

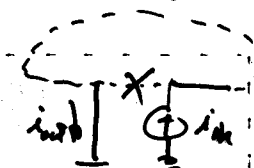
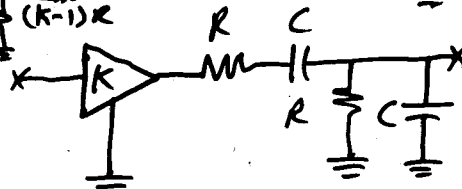
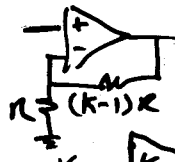


Wien Bridge Oscillator

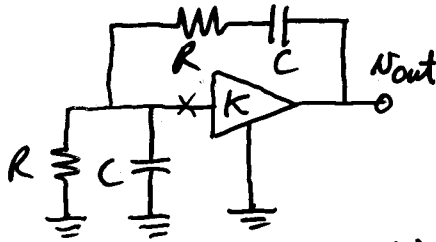
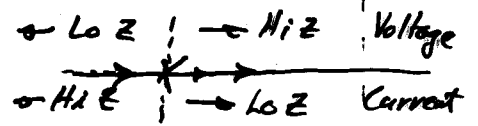
$$T(s) = \frac{K(R \parallel \frac{1}{sC})}{R + \frac{1}{sC} + R \parallel \frac{1}{sC}} = \frac{SKRC}{s^2 R^2 C^2 + 3RCs + 1}$$





$$T(j\omega) = \frac{j\omega KRC}{(1 - \omega^2 R^2 C^2) + j\omega 3RC} = 1 + j0 \Rightarrow \omega_{osc} = \frac{1}{RC} \quad K=3$$

Example: Let  $R=10k\Omega$  and  $C=0.1\mu F$


$$\omega_{osc} = \frac{1}{10^4 \cdot 10^{-7}} = 10^3 \rightarrow f_{osc} = \frac{1000}{2\pi} = 159 Hz$$

\* Amplitude Stabilization in Oscillators

Look at the amplifier transfer function.

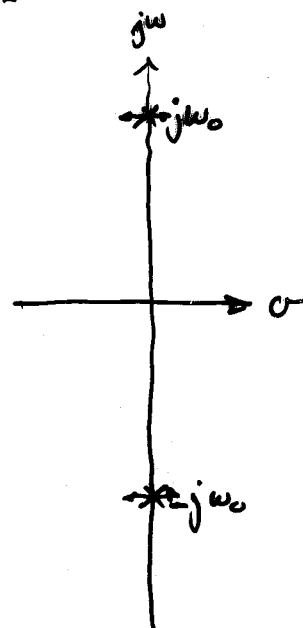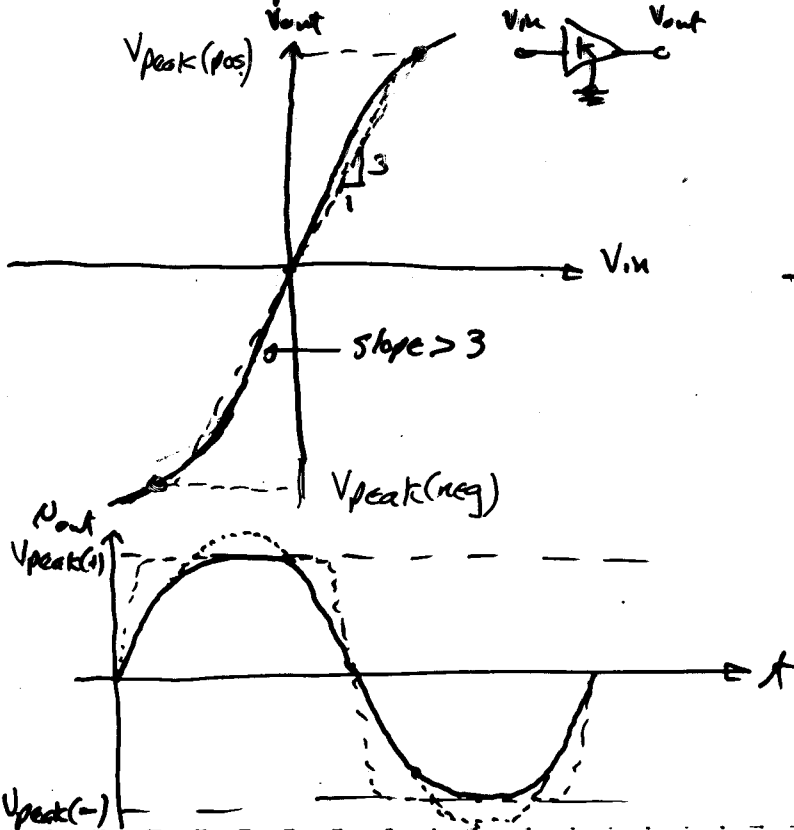

Modified Wien Bridge Oscillator -

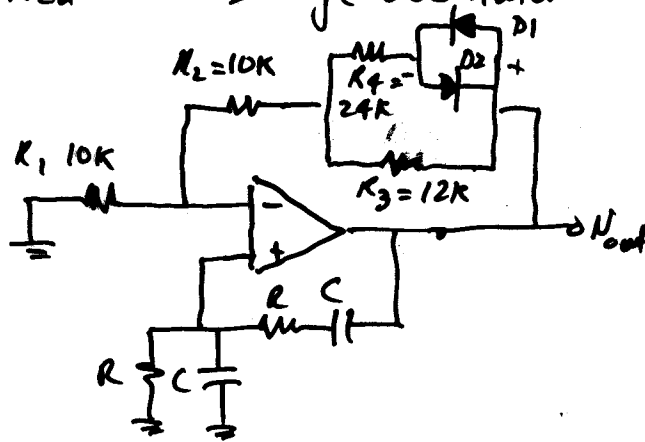


Gain with the diodes off:

$$\frac{R_1 + R_2 + R_3}{R_1} = \frac{32K}{10K} = 3.2$$

Gain with the diodes on:

$$\frac{R_1 + R_2 + R_3 \parallel R_4}{R_1} \approx \frac{25K}{10K} = 2.5$$

Hewlett-Packard

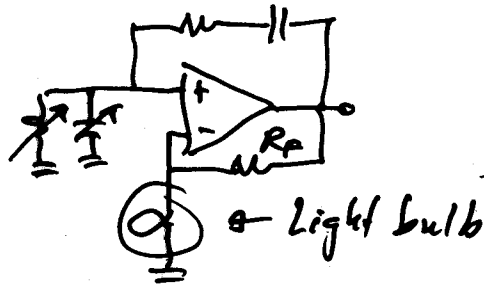

200 CD

