

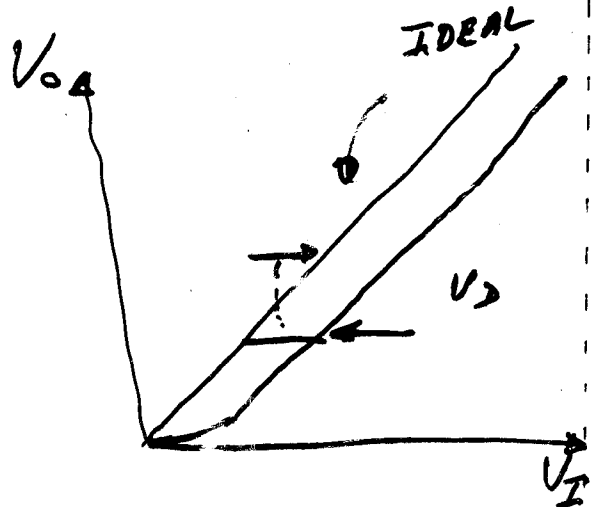


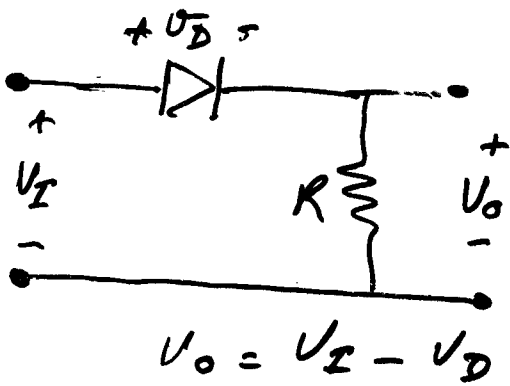EFFECT OF THE DIODE FORWARD VOLTAGE DROP:



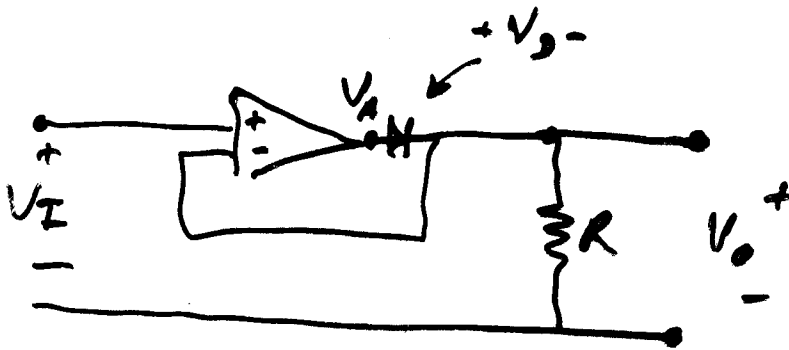THE USE OF OP-AMPS FOR RECTIFICATION - "THE SUPER-DIODE"



$\therefore A_V \neq \infty$

$V_O = V_A - V_D$


$\therefore V_A = A_V (V_I - V_O)$

$V_O = A_V (V_I - V_O) - V_D$


$$V_o(1 + A_v) = A_v V_I - V_D$$

$$\Rightarrow V_o = \frac{A_v}{1 + A_v} V_I - \frac{V_D}{1 + A_v}$$
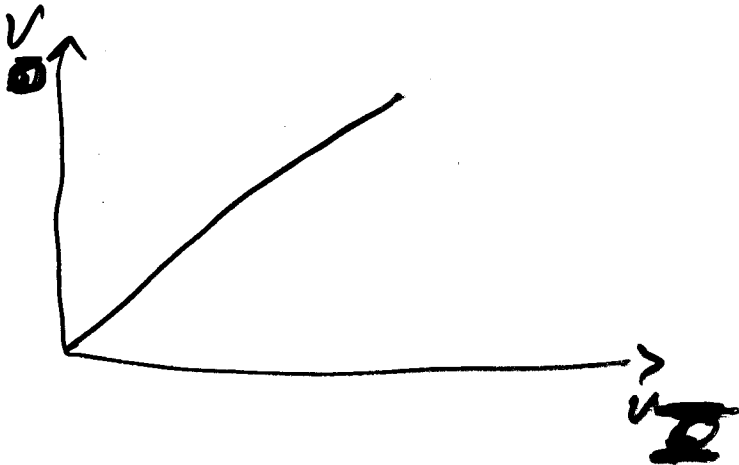
$$\text{As } A_v \rightarrow \infty, V_o = V_I$$



PRINCIPLE :

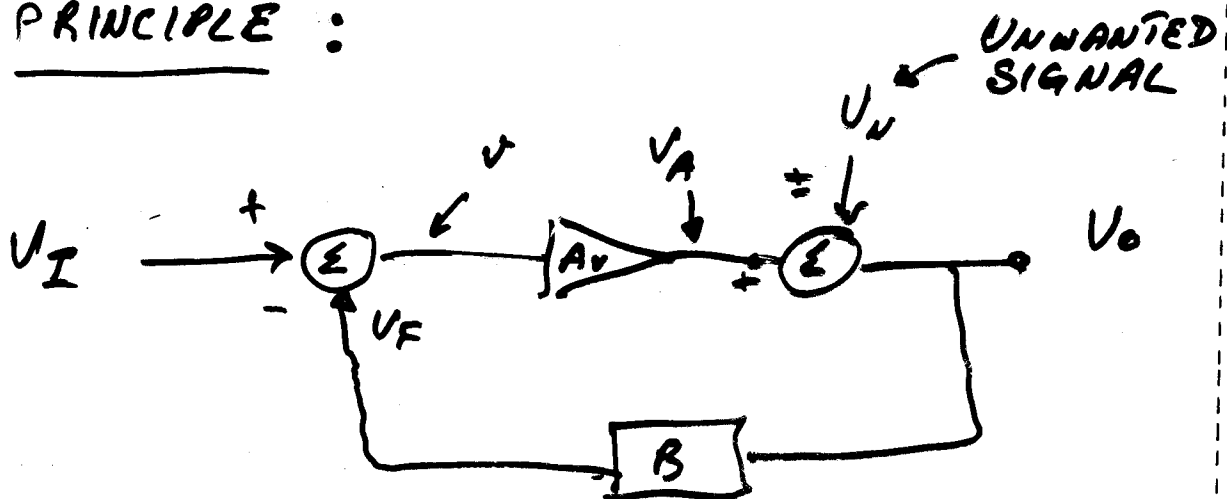

$$V_o = V_A \pm V_U = A_v V \pm V_U$$


$$V_o = A_v (V_I - V_F) \pm V_U$$

$$V_o = A_v (V_I - B V_o) \pm V_U$$

$$V_o = \left(\frac{A_v}{1 + B A_v} \right) V_I \pm \frac{V_U}{1 + B A_v}$$


"PRECISION DIODE" - PRACTICAL OP-AMP RECTIFIER :

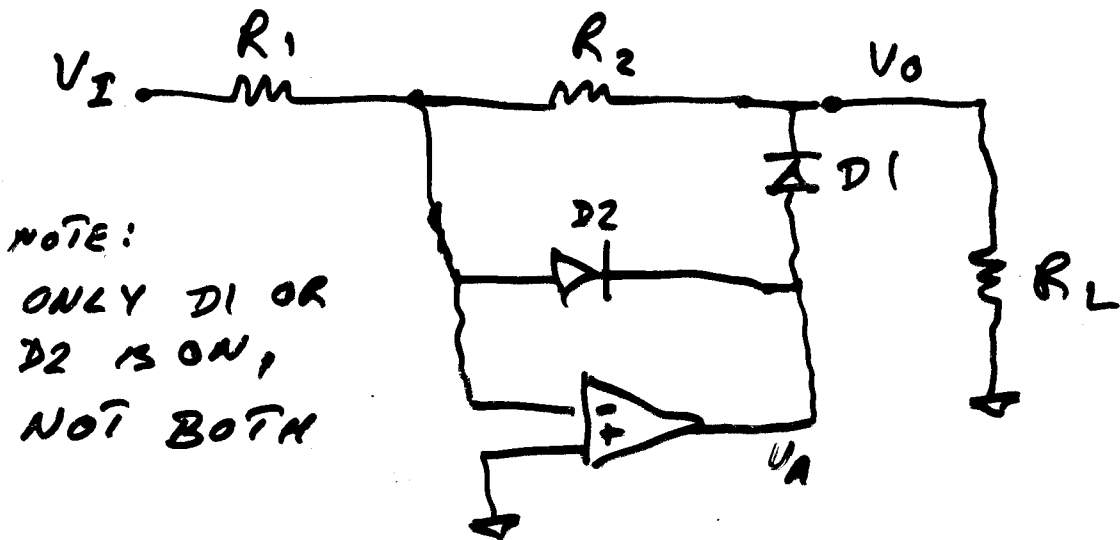IN THE PREVIOUS CRT the loop is open for $V_I < 0$.



NOTE:
ONLY D1 OR
D2 IS ON,
NOT BOTH

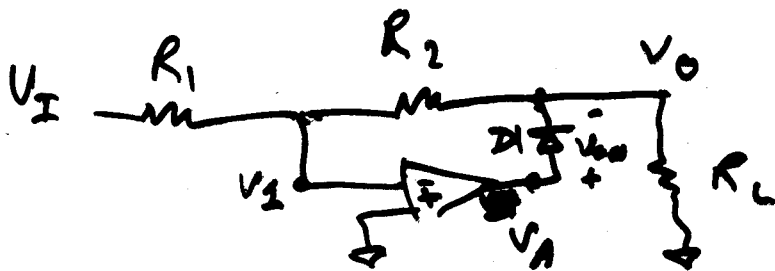$V_I < 0$ $V_A > 0 \Rightarrow D1 \text{ ON}, D2 \text{ OFF}$



$$V_O = V_A - V_{ON} = -A V_2 - V_{ON}$$

$$\therefore V_2 = \frac{R_2}{R_1 + R_2} V_I + \frac{R_1}{R_1 + R_2} V_O$$

$$V_o = -A_v \left(\frac{R_2}{R_1 + R_2} V_I + \frac{R_1}{R_1 + R_2} V_o \right) - V_{ON}$$

$$V_o \left[1 + \frac{A_v R_1}{R_1 + R_2} \right] = -A_v \frac{R_2}{R_1 + R_2} V_I - V_{ON}$$

$$V_o = \left(\frac{-A_v \frac{R_2}{R_1 + R_2}}{1 + A_v \frac{R_1}{R_1 + R_2}} \right) V_I - \frac{V_{ON}}{1 + A_v \frac{R_1}{R_1 + R_2}}$$

$$\lim_{A_v \rightarrow \infty} V_o = -\frac{R_2}{R_1} V_I$$

