
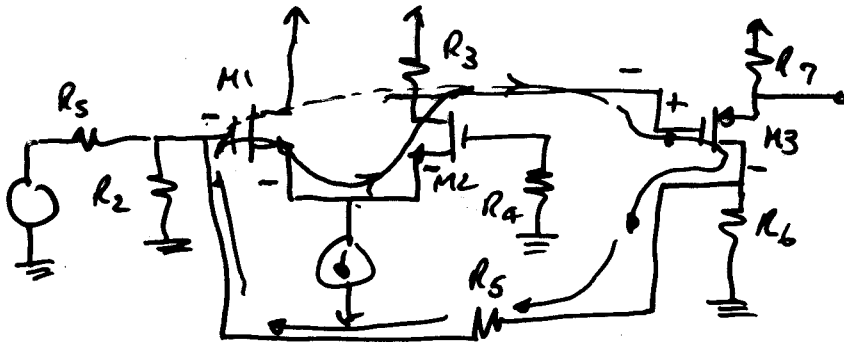


Final Exam Problem Session

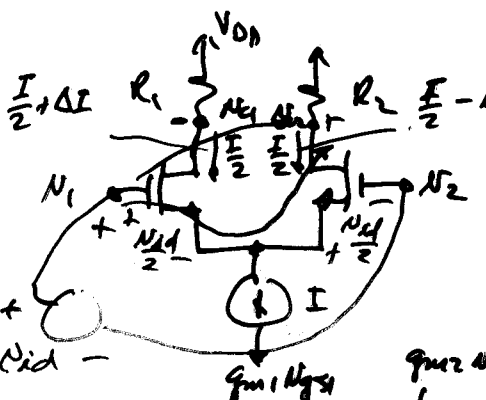Lecture 4/5/04 - Shunt-series fb. example



How is the feedback loop completed thru the diff. amp?





$R_1 = R_2 = R$

$$V_{O1} = V_{DD} - \left(\frac{I}{2} + \Delta I\right)R$$



$$V_{O2} = V_{DD} - \left(\frac{I}{2} - \Delta I\right)R$$

$$V_{O2} - V_{O1} = V_{DD} - \frac{I}{2}R + \Delta I \cdot R - V_{DD} + \frac{I}{2}R + \Delta I \cdot R$$

$$= 2 \Delta I R$$

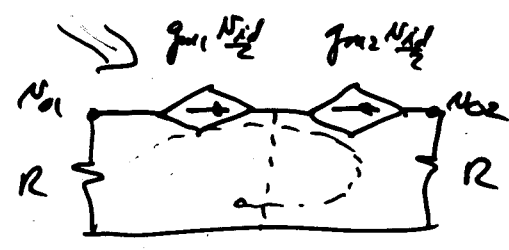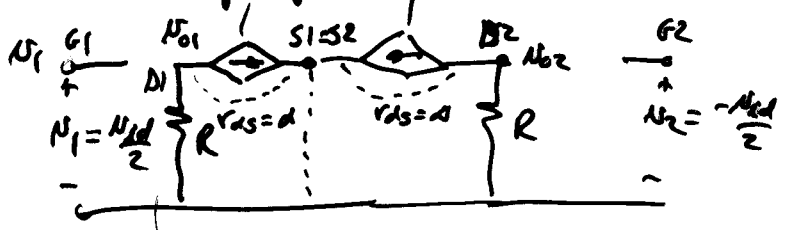

Fall 2002, Final, P2

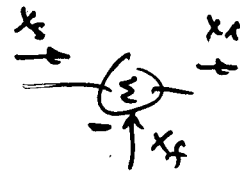
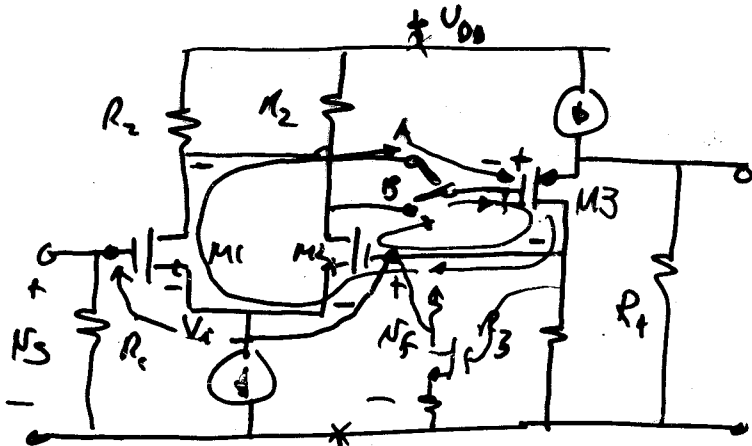


$$N_i = N_o - N_f$$




$$N = N_o \text{ or } i$$

$$N_i = N_o - N_f$$

$$i_i = i_o - i_f$$

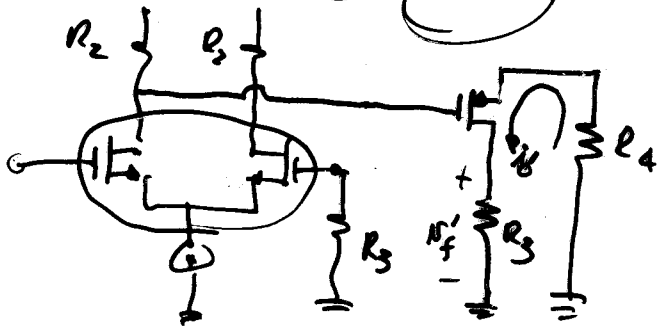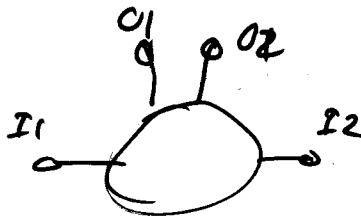

$$F = \frac{N_f'}{i_o} = R_3$$

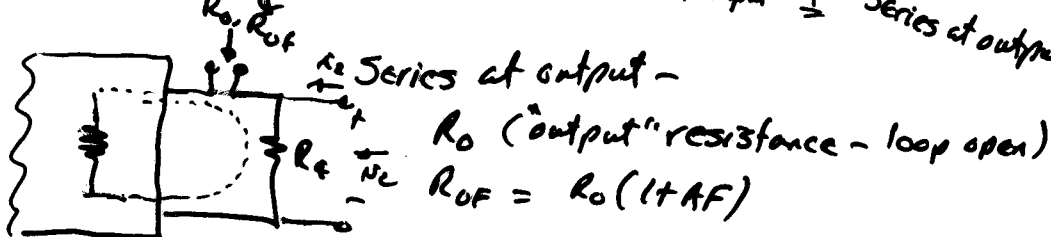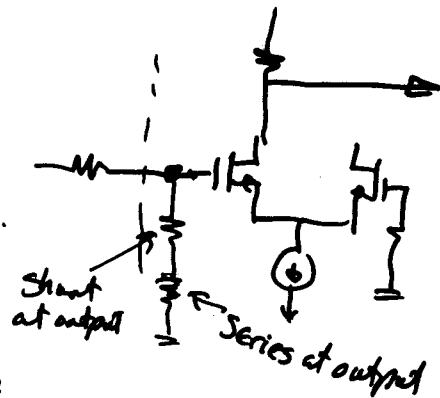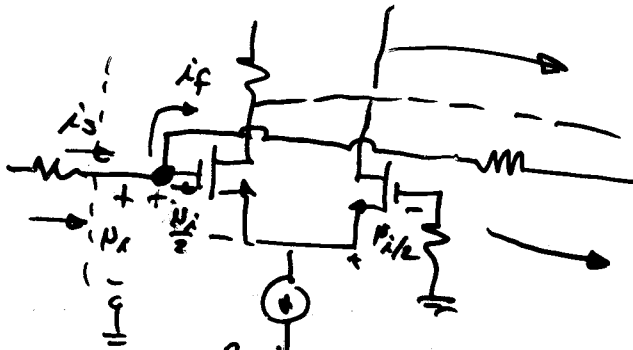


Series at output -


R_o ("output" resistance - loop open)

$$R_{oF} = R_o(1 + AF)$$
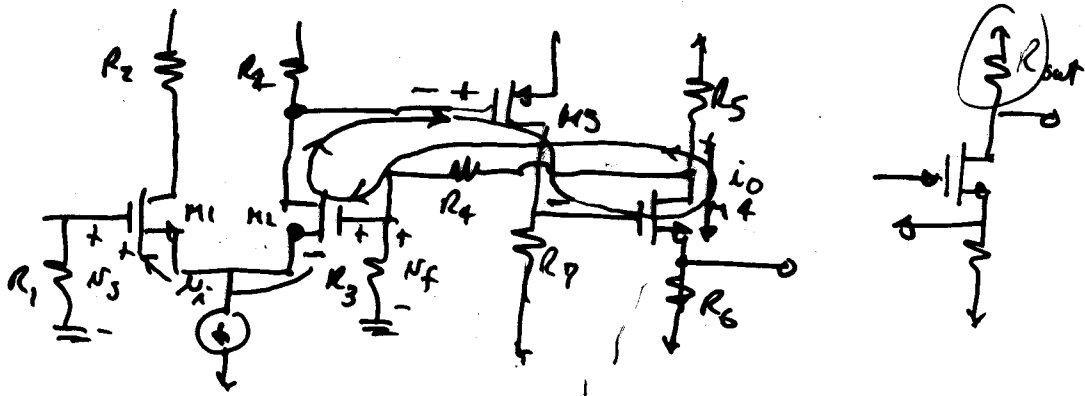
$$\frac{N_2}{i_2} = R_4 \parallel (R_{oF} - R_4)$$



Open-loop schematic - $1/g_{m4}R_6$

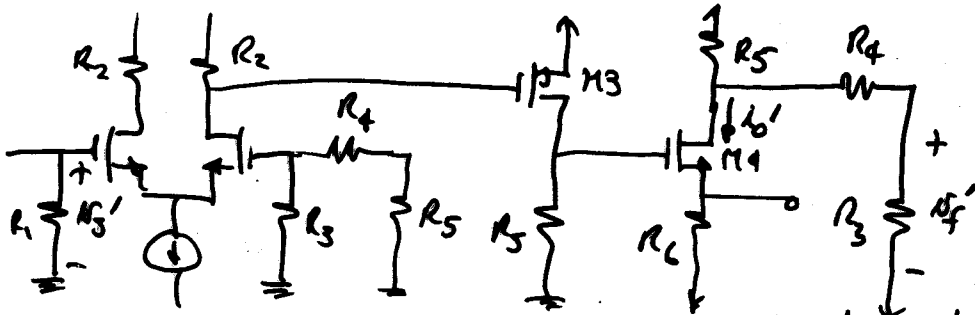

$$F = \frac{N_f'}{N_o'} = \frac{v_{gs4}'}{i_o'} = \frac{-R_5 R_3}{R_3 + R_4 + R_5}$$

$$A = \frac{i_o'}{v_{gs4}'}$$

~~$F = \frac{v_{gs4}'}{i_o'} = \frac{-R_5 R_3}{R_3 + R_4 + R_5}$~~

Fall 2002, Final, P1

Q. OK (b.)

$$T(j\omega) = \frac{-(g_m R)^3}{[1 - 3\omega^2 R^2 C^2] + j\omega RC [3 - \omega^2 R^2 C^2]} = 1 + j0$$

$$3 - \omega^2 R^2 C^2 = 0 \rightarrow \omega^2 = \frac{3}{R^2 C^2} \rightarrow \omega_{osc} = \frac{\sqrt{3}}{RC}$$

OK for $\omega = \omega_{osc}$ what is T?

$$\frac{-(g_m R)^3}{[1 + 3\omega_{osc}^2 R^2 C^2]} = \frac{-(g_m R)^3}{1 + 3R^2 C^2 \times \frac{3}{R^2 C^2}} = \frac{-(g_m R)^3}{1 - 9} = 1$$

$$(g_m R)^3 = 8$$

$$g_m R = 2$$

Suppose switch is connected to A.

$$T(s) = \frac{(g_m R)^3}{D(s)}$$

$$T(j\omega) = \frac{+(g_m R)^3}{[1 + 3\omega^2 R^2 C^2] + j\omega RC [3 - \omega^2 R^2 C^2]} = 1 + j0$$

$1 - 9 = -8$
 $\underbrace{\hspace{10em}}_{=0}$