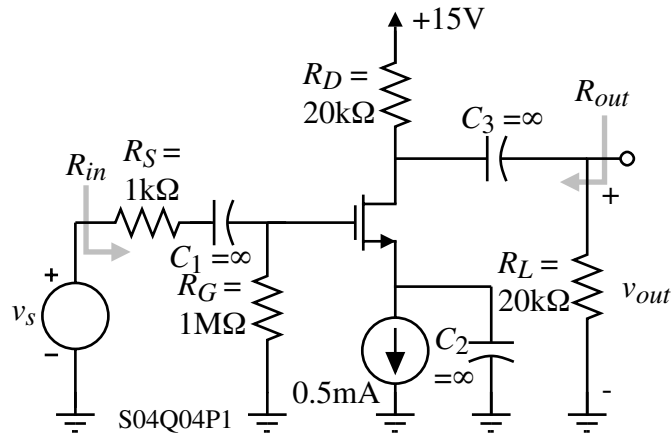



**QUIZ NO. 4 - SOLUTION**

(Average score = 8.2/10 of those taking the quiz.)

A NMOS common-source inverting amplifier is shown. Assume the parameters of the transistor are  $K_N = 1\text{mA/V}^2$ ,  $V_{TN} = 1\text{V}$ , and  $\lambda = 0$ . (a.) Find the small signal model parameter values for  $g_m$  and  $r_{ds}$ . (b.) Find an algebraic expression for the small signal input resistance,  $R_{in}$ , the output resistance,  $R_{out}$ , and the voltage gain,  $v_{out}/v_s$ . (c.) Numerically evaluate the small signal input resistance,  $R_{in}$ , the output resistance,  $R_{out}$ , and the voltage gain,  $v_{out}/v_{in}$ .

Solution

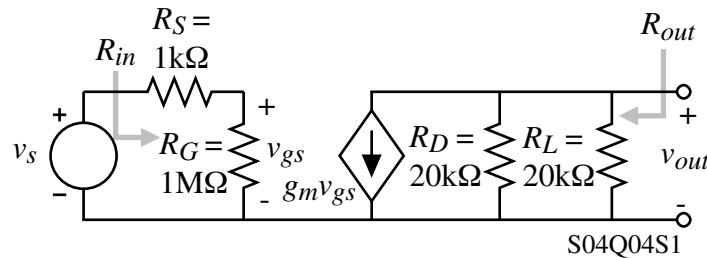(a.) Small-signal model (Note the dc current source is replaced by an infinite):



Find  $g_m$  and  $r_{ds}$ :  $g_m = \sqrt{2K_N I_D} = \sqrt{2 \cdot 1 \cdot 0.5} = \underline{1\text{mS}}$  and  $r_{ds} = \underline{\infty}$  (ignore  $V_{DS}$ )

(b.) Find  $R_{in}$ ,  $R_{out}$ , and  $v_{out}/v_s$ .

$$\boxed{R_{in} = R_S + R_G}$$

$$\boxed{R_{out} = R_D \parallel R_L}$$

$$\frac{v_{out}}{v_s} = \frac{v_{out}}{v_{gs}} \frac{v_{gs}}{v_s} = (-g_m R_{out}) \left( \frac{R_G}{R_G + R_S} \right) = -g_m \left( \frac{R_D R_L}{R_D + R_L} \right) \left( \frac{R_G}{R_G + R_S} \right)$$

$$\boxed{\frac{v_{out}}{v_s} = -g_m \left( \frac{R_D R_L}{R_D + R_L} \right) \left( \frac{R_G}{R_G + R_S} \right)}$$

(c.) Evaluate  $R_{in}$ ,  $R_{out}$ , and  $v_{out}/v_s$ .

$$R_{in} = 1\text{k}\Omega + 1\text{M}\Omega \approx \underline{1\text{M}\Omega}$$

$$R_{out} = R_D \parallel R_L = \underline{10\text{k}\Omega}$$

$$\frac{v_{out}}{v_s} = \frac{v_{out}}{v_{gs}} \frac{v_{gs}}{v_s} = -g_m \left( \frac{R_D R_L}{R_D + R_L} \right) \left( \frac{R_G}{R_G + R_S} \right) = (-1\text{mS})(10\text{k}\Omega)(1) = \underline{-10\text{V/V}}$$