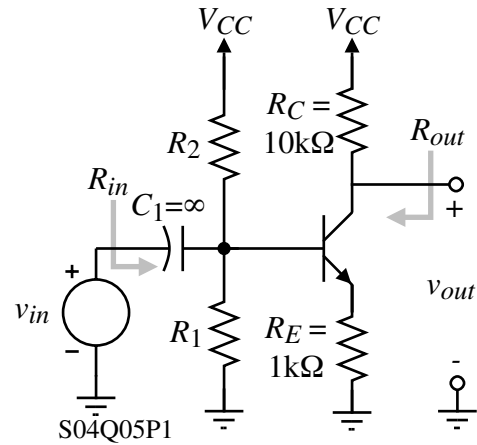


## QUIZ NO. 5

(Average score = 7.5/10 for those taking the quiz.)

An NPN BJT common-emitter inverting amplifier is shown. Assume the parameters of the transistor are  $\beta_o = 100$ ,  $V_T = 25\text{mV}$ , and  $V_A = 100\text{V}$ . (a.) If  $I_C = 0.5\text{mA}$  and  $V_{CE} = 3\text{V}$ , find the small signal model parameter values for  $g_m$ ,  $r_\pi$  and  $r_o$ . (b.) Find the numerical value for the small signal voltage gain,  $v_{out}/v_{in}$ , the input resistance,  $R_{in}$ , and the output resistance,  $R_{out}$ . Assume  $r_o = \infty$  in this part of the problem.

Solution

$$(a.) \quad g_m = \frac{I_C}{V_T} = \frac{0.5\text{mA}}{25\text{mV}} = \underline{20\text{mS}}$$

$$r_\pi = \beta_F \frac{V_T}{I_C} = \frac{100}{20\text{mS}} = \underline{5\text{k}\Omega}$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{102}{0.5\text{mA}} = \underline{204\text{k}\Omega}$$

(b.) The small signal model for this problem is shown (note a current controlled generator has been chosen for this problem).

Using the BE impedance reflection principle we get,

$$R_{in} = r_\pi + (1 + \beta_o)R_E \\ = 5\text{k}\Omega + (101)1\text{k}\Omega = \underline{106\text{k}\Omega}$$

( $R_B = R_1 \parallel R_2$  is not part of this because it is in parallel with  $v_{in}$  and is not a part of  $R_{in}$ .)

$$R_{out} = R_C = \underline{10\text{k}\Omega}$$

$$\frac{v_{out}}{v_{in}} = \left( \frac{v_{out}}{i_b} \right) \left( \frac{i_b}{v_{in}} \right) = (-\beta_o R_C) \left( \frac{1}{R_{in}} \right) = \frac{-100 \cdot 10\text{k}\Omega}{106\text{k}\Omega} = \underline{-9.434 \text{ V/V}}$$

