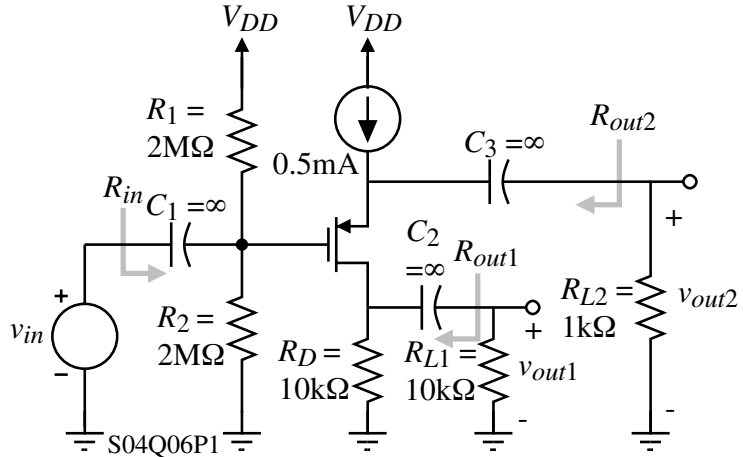


QUIZ NO. 6 - SOLUTION

(Average Score = 6.4/10 of those students taking the quiz)

A PMOS transistor amplifier with two outputs is shown. Assume the parameters of the transistor are $K_p = 1\text{mA/V}^2$, $V_{TP} = -1\text{V}$, and $\lambda = 0$. (a.) Find an algebraic expression for the small signal input resistance, R_{in} , the output resistances, R_{out1} and R_{out2} , the voltage gains, v_{out1}/v_{in} and, v_{out2}/v_{in} . (c.)



Numerically evaluate the small signal input resistance, R_{in} , the output resistances, R_{out1} and R_{out2} , the voltage gains, v_{out1}/v_{in} and, v_{out2}/v_{in} .

Solution

a.) Small-signal model:

We can write by inspection,



$$R_{in} = R_G$$

and

$$R_{out1} = R_D$$

The value of R_{out2} is equal to $1/g_m$ but will be proven as follows using the small-signal model shown,

$$R_{out2} = \frac{v_t}{i_t}$$

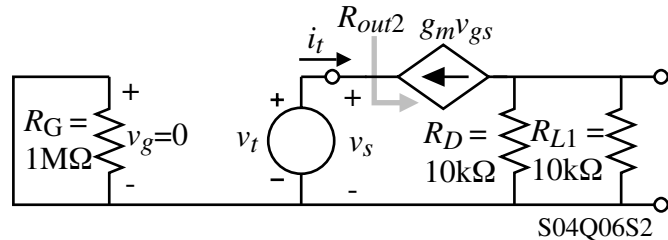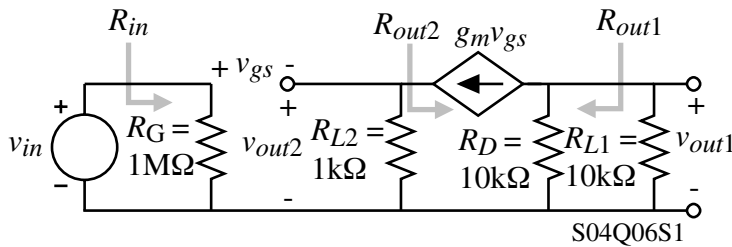

Now, $i_t = -g_m v_{gs} = -g_m(v_g - v_s) = -g_m(0 - v_t) = g_m v_t \rightarrow R_{out2} = \frac{v_t}{i_t} = \frac{1}{g_m} \rightarrow R_{out1} = \frac{1}{g_m}$

$$\frac{v_{out1}}{v_{in}} = \left(\frac{v_{out1}}{v_{gs}}\right)\left(\frac{v_{gs}}{v_{in}}\right) = [-g_m(R_D \parallel R_{L1})] \left(\frac{1}{1+g_m R_{L2}}\right) = \frac{-g_m(R_D \parallel R_{L1})}{1+g_m R_{L2}} \rightarrow \frac{v_{out1}}{v_{in}} = \frac{-g_m(R_D \parallel R_{L1})}{1+g_m R_{L2}}$$

$$\frac{v_{out2}}{v_{in}} = \left(\frac{v_{out2}}{v_{gs}}\right)\left(\frac{v_{gs}}{v_{in}}\right) = (g_m R_{L2}) \left(\frac{1}{1+g_m R_{L2}}\right) = \frac{g_m R_{L2}}{1+g_m R_{L2}} \rightarrow \frac{v_{out2}}{v_{in}} = \frac{g_m R_{L2}}{1+g_m R_{L2}}$$

b.) $R_{in} = 1\text{M}\Omega$, $R_{out1} = 10\text{k}\Omega$, $R_{out2} = \frac{1}{g_m} = \frac{1}{\sqrt{2K_p I_D}} = \frac{10^3}{\sqrt{2 \cdot 1 \cdot 0.5}} = 1\text{k}\Omega$,

$$\frac{v_{out1}}{v_{in}} = \frac{1\text{mS}(10\text{k}\Omega \parallel 10\text{k}\Omega)}{1+1 \cdot 1} = -2.5 \text{ V/V} \quad \text{and} \quad \frac{v_{out2}}{v_{in}} = \frac{1\text{mS}(1\text{k}\Omega)}{1+1 \cdot 1} = +0.5 \text{ V/V}$$