

## QUIZ NO. 6

NAME \_\_\_\_\_ Score \_\_\_\_\_ /10

A PMOS transistor amplifier with two outputs is shown.

Assume the parameters of the transistor are  $K_P = 1\text{mA/V}^2$ ,  $V_{TP} = -1\text{V}$ , and  $\lambda = 0$ . (a.)

Find an algebraic expression for the small signal input resistance,  $R_{in}$ , the output resistances,  $R_{out1}$  and  $R_{out2}$ , the voltage gains,  $v_{out1}/v_{in}$ , and,  $v_{out2}/v_{in}$ . (c.)

Numerically evaluate the small signal input resistance,  $R_{in}$ , the output resistances,  $R_{out1}$  and  $R_{out2}$ , the voltage gains,  $v_{out1}/v_{in}$ , and,  $v_{out2}/v_{in}$ .

