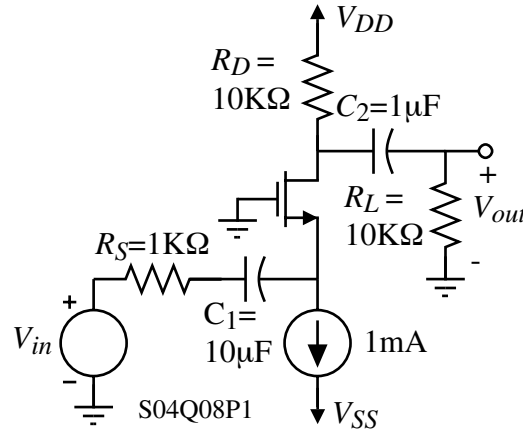


QUIZ NO. 8


(Average = 6.7/10 of those taking the quiz)

- a.) If the g_m of the MOSFET is 0.1mA/V, find the midband gain and the location of all zeros and poles of the circuit shown.
- b.) If the amplifier above has two zeros at the origin and a pole at -10 rads/sec and -40 rads/sec., what is the lower -3 dB frequency in Hz?



Solution

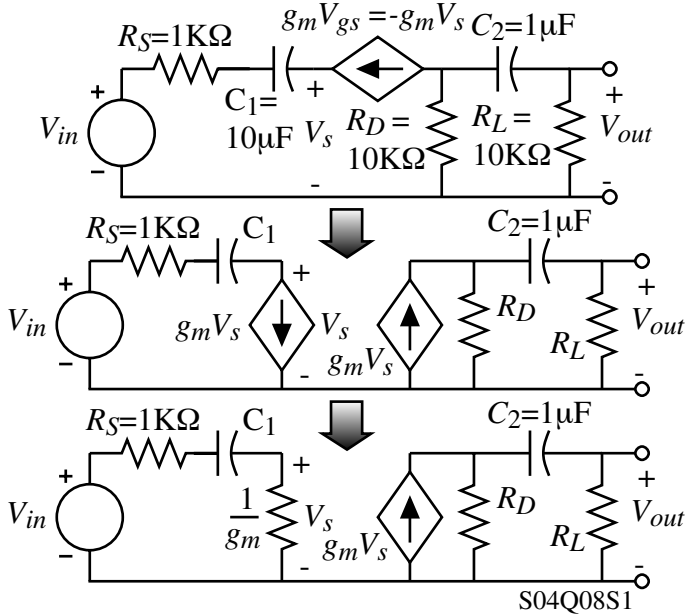a.) It is worthwhile to spend some effort in simplifying the small-signal model as follows:



$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_s} \frac{V_s}{V_{in}}$$

$$\frac{V_{out}}{V_s} = \frac{g_m R_D R_L}{R_D + R_L + \frac{1}{s C_1}}$$

$$= \left(\frac{g_m R_D R_L}{R_D + R_L} \right) \left(\frac{s}{s + \frac{1}{C_2 (R_D + R_L)}} \right)$$

$$\frac{V_s}{V_{in}} = \frac{1/g_m}{R_S + \frac{1}{g_m} + \frac{1}{s C_1}}$$

$$= \left(\frac{1}{1 + g_m R_S} \right) \left(\frac{s}{s + \frac{g_m}{C_2 (1 + g_m R_S)}} \right)$$

Thus, the MBG = $\left(\frac{g_m R_D R_L}{R_D + R_L} \right) \left(\frac{1}{1 + g_m R_S} \right) = (0.5)(1/1/1) = \underline{0.4545 V/V}$

There are two zeros at $s = 0$ and two poles:

$$p_2 = \frac{-1}{C_2 (R_D + R_L)} = \underline{-50 \text{ rads/sec.}} \text{ and}$$

$$p_1 = \frac{-g_m}{C_1 (1 + g_m R_S)} = \frac{-0.1 \times 10^{-3}}{10 \times 10^{-6} (1 + 0.1)} = \underline{-9.09 \text{ rads/sec.}}$$

b.) $\omega_L \approx \sqrt{p_1^2 + p_2^2 - 2(z_1^2 + z_2^2)} = \sqrt{10^2 + 40^2 - 2(0)} = \sqrt{1700} = 41.23 \text{ rads/sec.}$

$\therefore f_L = \frac{41.23}{6.28} = \underline{6.56 \text{ Hz}}$