



QUIZ NO. 10 - SOLUTIONS

(Average score = 6.4/10 of those taking the quiz.)

The FET in the amplifier shown has $g_m = 1\text{mA/V}$, $r_d = \infty$, $C_{gd} = 0.5\text{pF}$, and $C_{gs} = 10\text{pF}$. (a.) Find the midband gain, V_{out}/V_{in} . (b.) Find the upper -3dB frequency, f_H , in Hz.

Solution

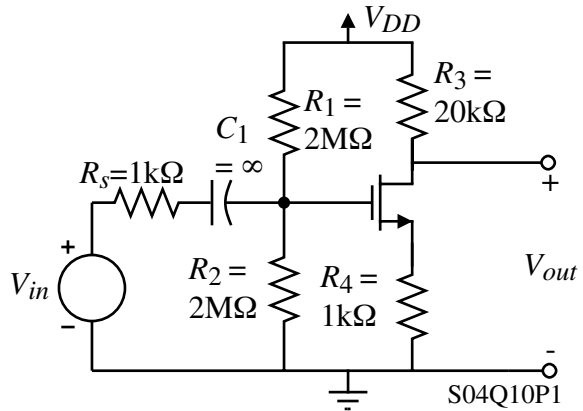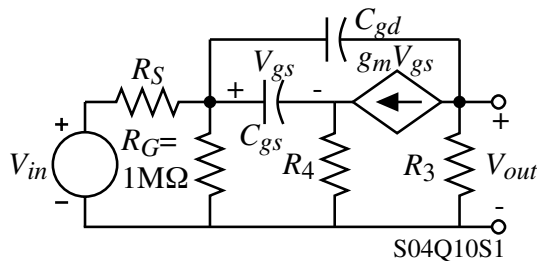(a.) The small-signal model for this problem is given below.



The MBG is given as


$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \left(\frac{V_{out}}{V_{gs}}\right) \left(\frac{V_{gs}}{V_g}\right) \left(\frac{V_g}{V_{in}}\right) \\ &= (-g_m R_3) \left(\frac{1}{1 + g_m R_4}\right) \left(\frac{R_G}{R_G + R_S}\right) \\ &= (-20)(0.5)(0.999) = \underline{-9.9\text{V/V}} \end{aligned}$$

(b.) Both the direct analysis and the Millers method are not attractive for this problem. The direct method is too complicated and because of R_4 , the Miller capacitance is not in parallel with C_{gs} . Therefore, we will use the OTC method.

R_{cgsO} : From the model shown to the right we write,

$$V_t = I_t(R_S \parallel R_G) + (I_t - g_m V_t)R_4$$
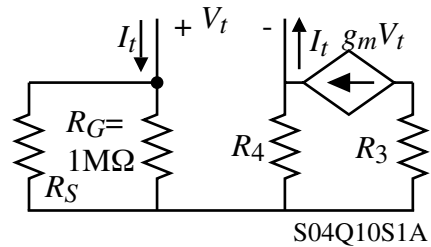
$$\therefore R_{cgsO} = \frac{R_S \parallel R_G + R_4}{1 + g_m R_4} = \frac{2.001\text{k}\Omega}{2} = 1\text{k}\Omega$$



R_{cgdO} : From the model shown to the right we write,

$$V_t = V_g + (I_t + g_m V_{gs})R_3$$

but $V_{gs} = V_g - V_s = V_g - g_m V_{gs} R_4$

or $V_{gs} = \left(\frac{1}{1 + g_m R_4}\right) V_g$

$$\therefore V_t = V_g + \left(\frac{g_m R_3}{1 + g_m R_4}\right) V_g + I_t R_3 = \left(\frac{1 + g_m R_3}{1 + g_m R_4}\right) V_g + I_t R_3 = I_t (R_S \parallel R_G) \left(\frac{1 + g_m R_3}{1 + g_m R_4}\right) + I_t R_3$$

or $R_{cgdO} = 20\text{k}\Omega + 0.999\text{k}\Omega \left(\frac{21}{2}\right) = 30.49\text{k}\Omega$ (this was a tough one)

Finally,

$$\omega_H \approx \frac{1}{R_{cgsO} C_{gs} + R_{cgsO} C_{gd}} = \frac{10^9}{1 \cdot 10 + 30.49 \cdot 0.5} = 39.61\text{Mrads/sec} \rightarrow \underline{6.30\text{MHz}}$$