



QUIZ NO. 11

(Average score = 8.1/10 of those taking the quiz)

A series-shunt feedback amplifier is shown. Use the methods of feedback analysis to find the numerical values of v_2/v_1 , v_1/i_1 , and v_2/i_2 . Assume that all transistors are matched and that $\beta = 100$, $r_\pi = 10\text{k}\Omega$ and $r_o = \infty$.

Solution

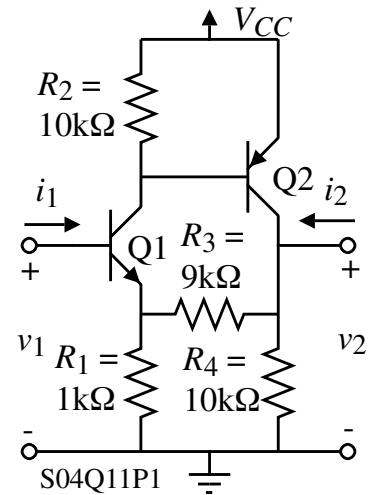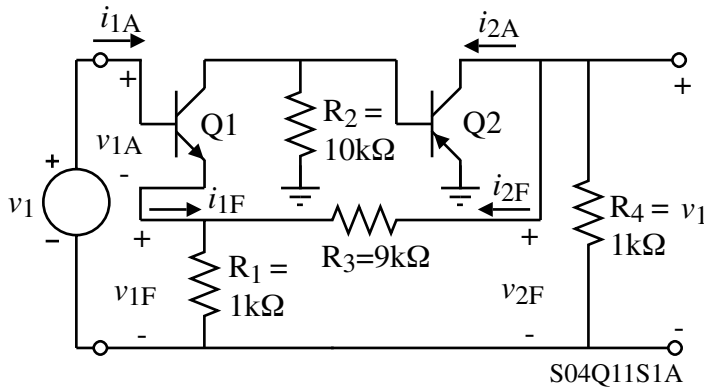
The circuit can be redrawn as shown to identify more clearly the A circuit and the feedback circuit.



$$F = h_{12F} = \frac{v_{1F}}{v_{2F}} \Big|_{i_{1F}=0} = 0.1 \text{ (V/V)}$$

We really don't need to calculate h_{11F} and h_{22F} if we correctly

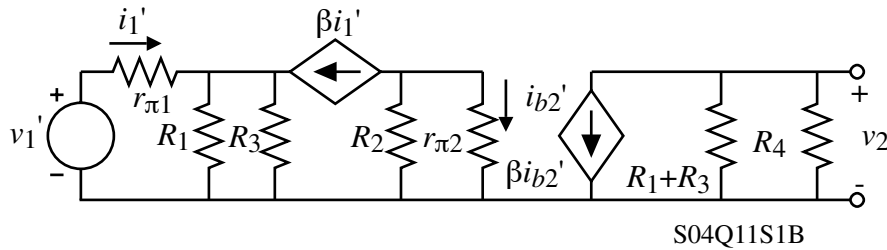open the loop as illustrated below. The small-signal model for the open-loop calculation of A is,



$$A = \frac{v_2'}{v_1'} = \left(\frac{v_2'}{i_{b2}'} \right) \left(\frac{i_{b2}'}{i_1'} \right) \left(\frac{i_1'}{v_1'} \right) = [-\beta(R_4 \parallel R_1 + R_3)] \left(\frac{-\beta R_2}{r_{\pi 2} + R_2} \right) \left(\frac{1}{r_{\pi 1} + (1 + \beta)(R_1 \parallel R_3)} \right)$$

$$= (-500\text{k}\Omega)(-50) \left(\frac{1}{10\text{k}\Omega + (101)(909)} \right) = 245.53 \text{ V/V}$$

$$\therefore A_F = \frac{v_2}{v_1} = \frac{A}{1 + AF} = \frac{245.53}{1 + 245.53(0.1)} = \frac{245.53}{25.553} = \underline{9.61 \text{ V/V}}$$

The open-loop input resistance is $R_i = r_{\pi 1} + (1 + \beta)(R_1 \parallel R_3) = 101.8\text{k}\Omega$

$$\therefore R_{in} = \frac{v_1}{i_1} = R_i(1 + AF) = 101.8\text{k}\Omega(25.553) = \underline{2.60\text{M}\Omega}$$

The open-loop output resistance is $R_o = R_4 \parallel (R_1 + R_3) = 5\text{k}\Omega$

$$\therefore R_{out} = \frac{v_2}{i_2} = \frac{R_o}{1 + AF} = \frac{5\text{k}\Omega}{25.553} = \underline{196 \Omega}$$