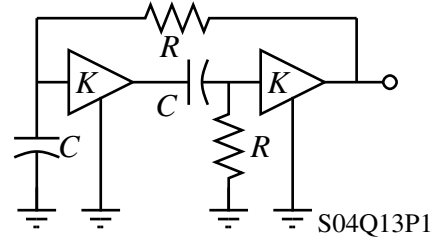


QUIZ NO. 13 - SOLUTION

(Average score = 6.8/10 of those taking the quiz)

This quiz deals with finding the open-loop gain and its application. The following questions are independent of each other.

(a.) Find the loop gain of the feedback circuit shown, $T(s)$, if the amplifier is an ideal voltage amplifier with a gain of K .



(b.) If $T(s) = \frac{sKRC}{s^2R^2C^2 + 2RCs + 1}$, find f_{osc} and the value of K necessary for oscillation.

(c.) If $T(s)$ has the following properties: $T(0) = 10$ and two poles at $s = -100$, what is the phase margin of this feedback circuit?


Solution

(a.) Opening the loop gives,

$$T(s) = \frac{V_{out}}{V_{in}} = \left(\frac{KR}{R + (1/sC)} \right) \left(\frac{K(1/sC)}{R + (1/sC)} \right)$$

$$= \frac{K^2RCs}{(sRC+1)(sRC+1)} = \frac{K^2RCs}{s^2R^2C^2 + s2RC + 1}$$
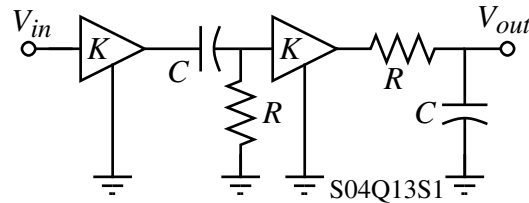
$$\therefore \boxed{T(s) = \frac{K^2RCs}{s^2R^2C^2 + s2RC + 1}}$$



$$(b.) T(s) = \frac{sKRC}{s^2R^2C^2 + 2RCs + 1} \quad \rightarrow \quad T(j\omega) = \frac{j\omega KRC}{-\omega^2R^2C^2 + j\omega 2RC + 1}$$

$$\text{or } T(j\omega) = \frac{j\omega KRC}{1 - \omega^2R^2C^2 + j\omega 2RC} = 1 + j0 \quad \Rightarrow \quad \boxed{f_{osc} = \frac{1}{2\pi RC}} \quad \text{and} \quad \boxed{K = 2}$$

(c.) We could plot a Bode plot and estimate the phase margin or do the following:

$$|T(j\omega)| = \frac{10}{1 + \left(\frac{\omega}{100}\right)^2}$$

$$\text{Find the unity-gain frequency from, } \frac{10}{1 + \left(\frac{\omega_c}{100}\right)^2} = 1 \quad \rightarrow \quad \omega_c^2 = 100^2(10-1) = 300^2$$

or $\omega_c = 300$ rads/sec. The phase margin can be expressed as,

$$PM = 180^\circ - 2 \tan^{-1} \left(\frac{300}{100} \right) = 180^\circ - 2(71.56^\circ) = \underline{\underline{36.87^\circ}}$$