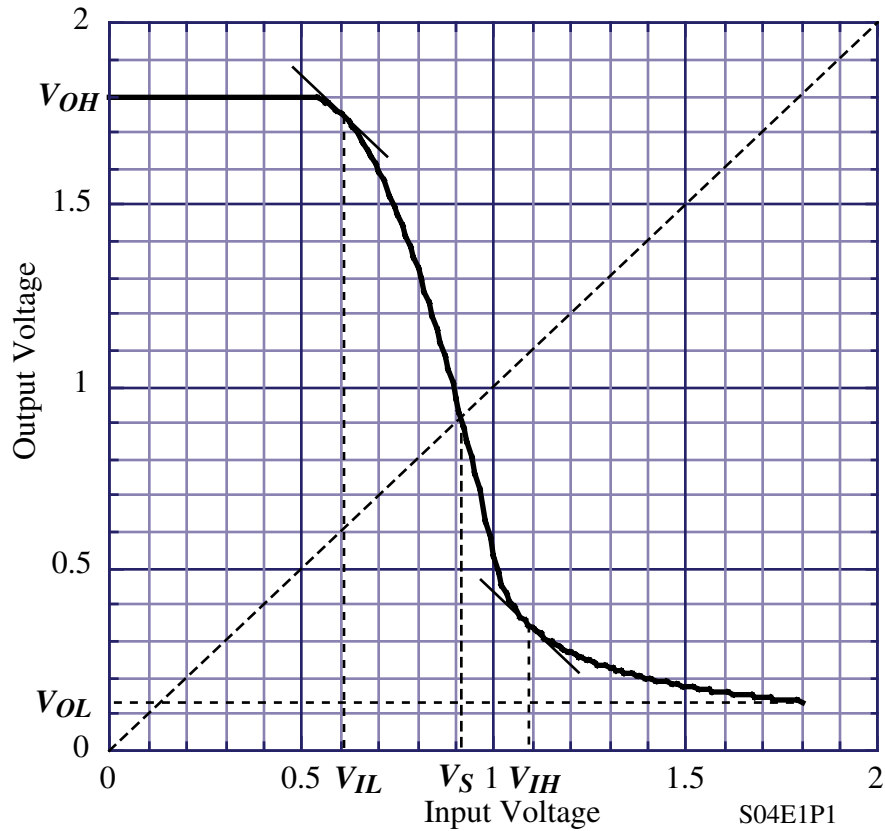


EXAMINATION NO. 1 - SOLUTIONS

(Average score = 78.4/100)

Problem 1 - (25 points)

From the voltage transfer function curve shown, numerically identify, V_{OH} , V_{OL} , V_{IL} , V_{IH} , and V_S . From these values, find the value of NM_H and NM_L .



From the curve we get the following numerical values.

$$V_{OH} = \underline{1.8V}, V_{OL} = \underline{0.13V}, V_{IL} = \underline{0.6V}, V_{IH} = \underline{1.08V}, \text{ and } V_S = \underline{0.92V}$$

The noise margins are,

$$NM_H = V_{OH} - V_{IH} = 1.80 - 1.08 = \underline{0.72V}$$

and

$$NM_L = V_{IL} - V_{OL} = 0.60 - 0.13 = \underline{0.47V}$$

Problem 2 – (25 points)

Solve for the dc value of the drain current, I_{DS} , for the NMOS transistor shown assuming $0.18\mu\text{m}$ CMOS technology. The W and L for this transistor are given in Problem 3.

Solution

Check for saturation.

$$V_{DS(\text{sat})} = \frac{(V_{GS} - V_T)E_c L}{(V_{GS} - V_T) + E_c L} = \frac{(1-0.5)(1.2)}{(1-0.5) + 1.2} = 0.353\text{V}$$

$$V_{DS} = 1.5\text{V} \Rightarrow \text{NMOS in saturation}$$


$$\therefore I_{DS} = Wv_{sat}C_{ox} \frac{(V_{GS} - V_T)^2}{(V_{GS} - V_T) + E_c L}$$

$$W = 0.6 \times 10^{-4} \text{ cm}$$

$$v_{sat} = \frac{\mu_e E_c}{2} = \frac{270 \text{ (cm}^2/\text{V}\cdot\text{s}) 6 \times 10^4 \text{ (V/cm)}}{2} = 8.1 \times 10^6 \text{ cm/sec}$$


$$C_{ox} = \frac{\epsilon_r(\epsilon_o)}{t_{ox}} = \frac{4 \cdot 8.85 \times 10^{-14} \text{ (F/cm)}}{35 \times 10^{-8} \text{ cm}} = 1.01 \times 10^{-6} \text{ F/cm}^2$$

$$\begin{aligned} \therefore I_{DS} &= (0.6 \times 10^{-4} \text{ cm})(8.1 \times 10^6 \text{ cm/sec})(1.01 \times 10^{-6} \text{ F/cm}^2) \left(\frac{0.5^2}{0.5 + 1.2} \right) \text{ (V)} \\ &= \underline{\underline{72.18 \mu\text{A}}} \end{aligned}$$

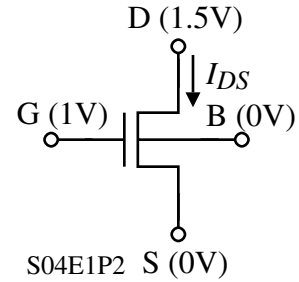

Problem 3 – (25 points)

Given the layout for the NMOS transistor of Problem 2, find the value of C_{gs} , C_{gd} , C_{gb} , C_{db} , and C_{sb} assuming that the junction depth of the source-drain diffusions is $x_j = 50$ nm, $m = 0.5$ and the lateral diffusion is 10nm.

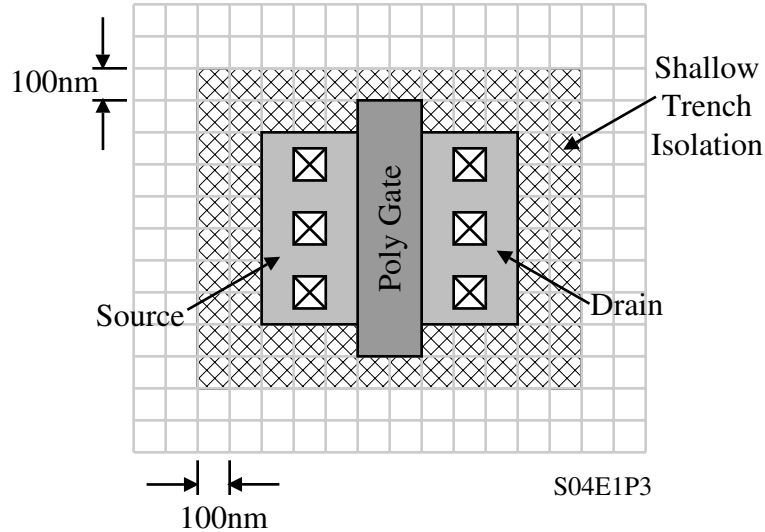**Solution**

From Problem 2, we know that the NMOS transistor is in saturation. To make the calculations, we will need C_g and C_{ov} . They are calculated as follows,

$$C_g = C_{ox} \cdot W \cdot L = 1.01 \times 10^{-6} \text{ (F/cm}^2\text{)} \cdot 0.6 \times 10^{-4} \text{ (cm)} \cdot 0.2 \times 10^{-4} \text{ (cm)} = 1.212 \times 10^{-15} \text{ F}$$

(C_{ox} was calculated in Problem 2)

$$C_{ol} = C_{ox} \cdot LD = 1.01 \times 10^{-6} \text{ (F/cm}^2\text{)} \cdot 10 \times 10^{-7} \text{ (cm)} = 1.01 \times 10^{-12} \text{ F/cm}$$

$$\therefore C_{gs} = C_{ol} \cdot W + 0.667 C_g = (1.01 \times 10^{-12}) \cdot (0.6 \times 10^{-4}) + (0.667)(1.212) = (0.061 + 0.808) \text{ fF}$$

$$= \underline{\underline{0.868 \text{ fF}}}$$

$$C_{gd} = 0.061 \text{ fF} \approx \underline{\underline{0}}$$

$$C_{gb} = \underline{\underline{0}}$$


$$C_J = \frac{C_{j0} (A_b + A_{sw})}{\left(1 - \frac{V_j}{\phi_B}\right)} = \frac{C_{j0} (A_b + A_{sw})}{\left(1 - \frac{V_j}{\phi_B}\right)}$$

$$C_{bd} = \frac{1.6 \text{ fF}/\mu\text{m}^2 [(0.3)(0.6) + (0.05)(0.6)]}{\sqrt{1 + \frac{1.5}{0.9}}} = \underline{\underline{0.206 \text{ fF}}}$$

$$C_{bs} = \frac{1.6 \text{ fF}/\mu\text{m}^2 [(0.3)(0.6) + (0.05)(0.6)]}{\sqrt{1 + 0}} = \underline{\underline{0.336 \text{ fF}}}$$

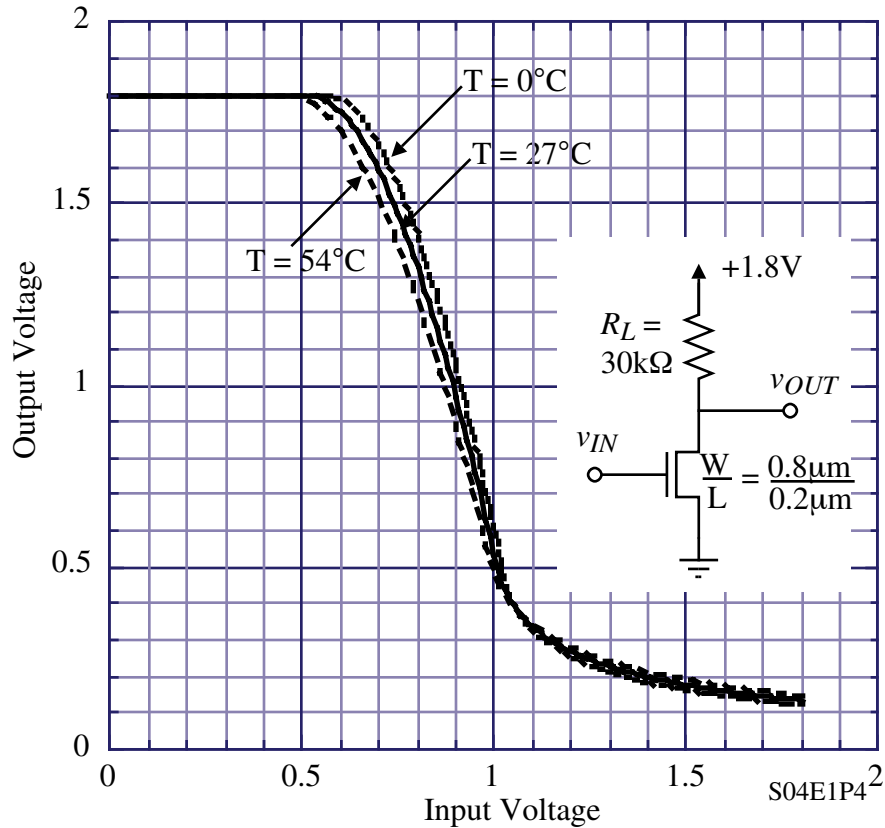Problem 4 – (25 points)

A voltage transfer curve of the circuit shown is given for $T = 0^\circ\text{C}$, 27°C , and 54°C . The solid curve corresponds to $T = 27^\circ\text{C}$. Identify which of the two dashed curves corresponds to $T = 0^\circ\text{C}$ and $T = 54^\circ\text{C}$? Justify your reason (for full credit) using the relationships for the temperature dependence of the mobility and threshold voltage given in the text. Assume that the resistor, R_L , has no temperature dependence and the technology is $0.18\mu\text{m}$ CMOS.



Assume the transistor is in saturation which might correspond for example to a value of $v_{IN} = 0.8\text{V}$. Therefore, assume that v_{IN} is fixed at a constant value such as 0.8V .

The output voltage can be found as

$$v_{OUT}(T) = 1.8 - I_D R_L = 1.8 - 30\text{k}\Omega \left[\frac{W\mu_e(T)E_C C_{ox} [V_{IN} - V_T(T)]^2}{2[(V_{IN} - V_T(T)) + E_C L]} \right]$$

$$\approx 1.8 - 30\text{k}\Omega \left[\frac{W\mu_e(T)C_{ox} [V_{IN} - V_T(T)]^2}{2L} \right], \text{ where } \frac{\mu_e(27^\circ\text{C})C_{ox}W}{2L} = 0.54\text{mA/V}^2$$

assuming $0.18\mu\text{m}$ CMOS technology. Assuming also that $V_{IN} = 0.8\text{V}$,

$$v_{OUT}(T) = 1.8 - 16.2 \left(\frac{T}{T_o} \right)^{-1.5} [0.8 - 0.5 + 0.002(T - T_o)]^2 = 1.8 - 16.2 \left(\frac{T}{T_o} \right)^{-1.5} [0.3 + 0.002(T - T_o)]^2$$

For $T = T_o = 27^\circ\text{C}$ we get, $v_{OUT}(27^\circ\text{C}) = 1.8 - 16.2(0.09) = 1.8 - 1.45 = 0.342\text{V}$

For $T = T_o = 0^\circ\text{C}$ we get, $v_{OUT}(0^\circ\text{C}) = 1.8 - 16.2(1.15)(0.3 - 0.054)^2 = 1.8 - 1.13 = 0.67\text{V}$

For $T = T_o = 54^\circ\text{C}$ we get, $v_{OUT}(54^\circ\text{C}) = 1.8 - 16.2(0.78)(0.3 + 0.054)^2 = 1.8 - 1.58 = 0.22\text{V}$

(Unfortunately I used the wrong mobility on the curves so that the values don't correspond but the trend is correct.)