

**Homework No. 4 – Solutions**Problem 1 – P4.2

Problem should refer to Figure P4.1

- a. Resistive load

$$V_{OH} = V_{DD}$$

$$\begin{aligned} V_{OL} &= \frac{V_{DD}}{1 + kR_L(V_{DD} - V_T)} = \frac{V_{DD}}{1 + \mu_N C_{OX} \frac{W}{L} R_L (V_{DD} - V_T)} \\ &= \frac{1.2}{1 + (260)(10^{-6})\left(\frac{1}{0.1}\right)(10 \times 10^3)(1.2 - 0.4)} = 0.055\text{V} \end{aligned}$$

- b. Saturated-enhancement load

$$\begin{aligned} V_{OH} &= V_{DD} - V_T = V_{DD} - \left( V_{T0} + \gamma \left( \sqrt{V_{SB} + 2|\phi_f|} - \sqrt{2|\phi_f|} \right) \right) \\ &= V_{DD} - V_{T0} - \gamma \sqrt{V_{OH} + 2|\phi_f|} + \gamma \sqrt{2|\phi_f|} \\ &= 1.2 - 0.4 - 0.2\sqrt{V_{OH} + 0.88} + 0.2\sqrt{0.88} \\ &= 0.988 - 0.2\sqrt{V_{OH} + 0.88} \end{aligned}$$

Iterate to produce:

$$V_{OH} = 0.733\text{V}$$

To compute  $V_{OL}$  we can ignore body effect and equate currents:

$$\begin{aligned} \therefore \frac{W_I}{L_I} \frac{\mu_N}{\left(1 + \frac{V_{OL}}{E_{CN} L_I}\right)} \left[ (V_{DD} - V_{TI}) V_{OL} - \frac{V_{OL}^2}{2} \right] &= \frac{W_L V_{sat} (V_{DD} - V_{OL} - V_{TL})^2}{(V_{DD} - V_{OL} - V_{TL}) + E_{CN} L_L} \\ \therefore \frac{1.2}{0.1} \frac{(270 \text{ cm}^2 / \text{V} \cdot \text{s})}{\left(1 + \frac{V_{OL}}{0.6}\right)} \left[ (1.2 - 0.4) V_{OL} - \frac{V_{OL}^2}{2} \right] &= \frac{(0.2 \mu\text{m})(8 \times 10^6 \text{ cm} / \text{s})(1.2 - V_{OL} - 0.4)^2}{(1.2 - V_{OL} - 0.4) + 0.6} \end{aligned}$$

Solve for  $V_{OL} \approx 0.03\text{V}$ 

- c. Linear-enhancement load

$$\begin{aligned}
 V_{OH} &= V_{GG} - V_T = V_{DD} - \left( V_{T0} + \gamma \left( \sqrt{V_{SB} + 2|\phi_f|} - \sqrt{2|\phi_f|} \right) \right) \\
 &= V_{GG} - V_{T0} - \gamma \sqrt{V_{OH} + 2|\phi_f|} + \gamma \sqrt{2|\phi_f|} \\
 &= 1.6 - 0.4 - 0.2 \sqrt{V_{OH} + 0.88} + 0.2 \sqrt{0.88} \\
 &= 1.388 - 0.2 \sqrt{V_{OH} + 0.88}
 \end{aligned}$$

Iterate to produce:

$$V_{OH} = 1.11\text{V}$$

This tells us that  $V_{GG}$  should have been above 1.6V (closer to 1.7 V).

To compute  $V_{OL}$  we can ignore body effect and equate currents. Note that the load is saturated even though we call it a linear-enhancement load. The driver is also saturated due to the device sizes used.

$$\begin{aligned}
 \therefore \frac{W_I V_{sat} (V_{DD} - V_{TI})^2}{(V_{DD} - V_{TI}) + E_{CN} L_I} &= \frac{W_L V_{sat} (V_{GG} - V_{OL} - V_{TL})^2}{(V_{GG} - V_{OL} - V_{TL}) + E_{CN} L_L} \\
 \therefore \frac{(0.1\mu\text{m})(8 \times 10^6 \text{ cm/s})(1.2 - 0.4)^2}{(1.2 - 0.4) + 0.6} &= \frac{(0.1\mu\text{m})(8 \times 10^6 \text{ cm/s})(1.6 - V_{OL} - 0.4)^2}{(1.6 - V_{OL} - 0.4) + 0.6}
 \end{aligned}$$

Solve for  $V_{OL} \approx 0.69\text{V}$

d. CMOS

$$V_{OH} = V_{DD} \quad V_{OL} = 0\text{V}$$

### Problem 2 – P4.3

For this problem, you are required to use the formulae:

$$V_{IL} = \frac{2V_{out} - V_{DD} - |V_{TP}| + (k_N / k_P)(V_{TN})}{1 + (k_N / k_P)} \quad V_{IH} = \frac{2V_{out} + V_{TN} + (k_P / k_N)(V_{DD} - |V_{TP}|)}{1 + (k_P / k_N)}$$

We already know that  $V_{OH}=1.2\text{ V}$  and  $V_{OL}=0\text{ V}$ . For  $V_S$  use:

$$W_N = 4\lambda, \quad W_P = 16\lambda:$$

$$X = \sqrt{\frac{\frac{W_N}{E_{CN}L_N}}{\frac{W_P}{E_{CP}L_P}}} = \sqrt{\frac{W_N E_{CP}}{W_P E_{CN}}} = \sqrt{\frac{(4)(24)}{(16)(6)}} = 1$$

$$V_S = \frac{0.8 + (0.4)1}{1+1} = 0.6V$$

Next  $V_{IL}$  and  $V_{IH}$  are estimated as follows:

$$V_{IL} = \frac{2V_{out} - V_{DD} - |V_{TP}| + (k_N/k_P)(V_{TN})}{1 + (k_N/k_P)} = \frac{2V_{out} - 1.2 - |-0.4| + (1)(0.4)}{1 + (1)} = \frac{2V_{out} - 1.2}{2} = 0.55V$$

$$V_{IH} = \frac{2V_{out} + V_{TN} + (k_P/k_N)(V_{DD} - |V_{TP}|)}{1 + (k_P/k_N)} = \frac{2V_{out} + 0.4 + (1)(1.2 - 0.4)}{1 + (1)} = \frac{2V_{out} + 1.2}{2} = 0.65V$$

Therefore

$$NM_L = 0.55 - 0 = 0.55V$$

$$NM_H = 1.2 - 0.65V = 0.55V$$

When we cut the size of the PMOS device in half, the VTC shifts to the left. So  $V_{IL}$ ,  $V_S$ , and  $V_{IH}$  will all shift to the left. The recalculation of the switching threshold produces  $V_S=0.566V$ .

We can compute  $V_{IL}$  to be roughly 0.533V and  $V_{IH}$  to be roughly 0.667V.

Therefore

$$NM_L = 0.533 - 0 = 0.533V$$

$$NM_H = 1.2 - 0.667V = 0.533V$$

### Problem 3 – P4.9

Resistive Load inverter:

$$\frac{V_{DD} - V_{OL}}{R_L} = \frac{W_N}{L_N} \frac{\mu_n C_{ox}}{\left(1 + \frac{V_{OL}}{E_C L}\right)} [2(V_{OH} - V_T)V_{OL} - V_{OL}^2]$$

$$\frac{1.2 - 0.1}{10k} = \frac{W_N (270)(1.6 \times 10^{-6})}{0.1 \left(1 + \frac{0.1}{0.6}\right)} [2(1.2 - 0.4)0.1 - 0.1^2]$$

$$\therefore W_N = 0.2 \mu m$$

Saturated Enhancement Load inverter (ignoring body-effect):

$$\frac{W_I}{L_I} \frac{\mu_N C_{ox}}{\left(1 + \frac{V_{out}}{E_{CN} L_I}\right)} \left[ (V_{in} - V_{TH}) V_{out} - \frac{V_{out}^2}{2} \right] = \frac{W_L V_{sat} C_{ox} (V_{DD} - V_{out} - V_{TL})^2}{(V_{DD} - V_{out} - V_{TL}) + E_{CN} L_L}$$

$$\frac{W_I (270)(1.6 \times 10^{-6})}{0.1 \left(1 + \frac{0.1}{0.6}\right)} [2(1.2 - 0.4)0.1 - 0.1^2] = \frac{0.1(10^{-4})(8)(1.6)(1.2 - 0.1 - 0.4)^2}{(1.2 - 0.1 - 0.4) + 0.6}$$

$$\therefore W_N = 0.1 \mu m$$

Linear Enhancement Load inverter (ignoring body-effect):

$$\frac{W_I}{L_I} \frac{\mu_N C_{ox}}{\left(1 + \frac{V_{out}}{E_{CN} L_I}\right)} \left[ (V_{in} - V_{TH}) V_{out} - \frac{V_{out}^2}{2} \right] = \frac{W_L V_{sat} C_{ox} (V_{DD} - V_{out} - V_{TL})^2}{(V_{DD} - V_{out} - V_{TL}) + E_{CN} L_L}$$

$$\frac{W_I (270)(1.6 \times 10^{-6})}{0.1 \left(1 + \frac{0.1}{0.6}\right)} [2(1.2 - 0.4)0.1 - 0.1^2] = \frac{0.1(10^{-4})(8)(1.6)(1.6 - 0.1 - 0.4)^2}{(1.6 - 0.1 - 0.4) + 0.6}$$

$$\therefore W_N = 0.6 \mu m$$

The linear enhancement load inverter requires the largest pull-down device since it has the strongest pull up device. The resistive load inverter is next and the saturated enhancement load requires the smallest pull-down device.