## **Homework Assignment No. 10**

Due on Wednesday, March 31, 2004

- 1.) Problem P7.6 (a) and (c) of the text.
- 2.) Problem P7.7 of the text.

[Ans. (a) 
$$LE = 2/3$$
 (b)  $LE_A = 1$ ,  $LE_B = 3$ , and  $LE_C = 1$ 

3.) Problem P7.10 of the text.

[Ans: Shortest path is 47.4ps and the longest path is 112.5ps]

4.) Problem P7.13 of the text.

[Ans: (a) Worst case charge sharing occurs when a = c = e = 1 and both b = d = 0.

(b)  $V^* = 1.34$ V and (c) Circuit is okay]