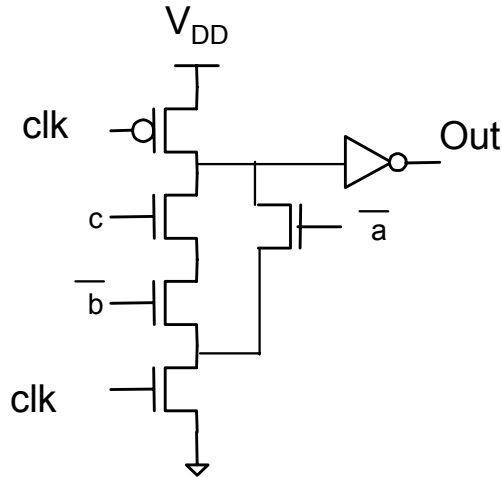



**Homework No. 10 – Solutions**

Problem 1 – P7.6(a) and (c)

(a.)  $Out = \bar{A} + \bar{B}C$



(c.)  $Out = \overline{(\bar{A} + \bar{B} + C)} + A\bar{B} = ABC\bar{C} + A\bar{B}$

 

Problem 2 – P7.7


P3.1. Assuming that one of the transistors in each transmission gate is being driven by a min-sized inverter:

(a.)  $LE = \frac{RC_{pass}}{RC_{inv}} = \frac{(R+R)(1)}{(R)(3)} = \frac{2\cancel{R}}{3\cancel{R}} = \frac{2}{3}$

(b.)  $LE_A = \frac{RC_A}{RC_{inv}} = \frac{(3R)(1)}{(R)(3)} = \frac{3\cancel{R}}{3\cancel{R}} = 1$   
 $LE_C = \frac{RC_C}{RC_{inv}} = \frac{(3R)(1)}{(R)(3)} = \frac{3\cancel{R}}{3\cancel{R}} = 1$   
 $LE_B = \frac{RC_B}{RC_{inv}} = \frac{(3R)(3)}{(R)(3)} = \frac{9\cancel{R}}{3\cancel{R}} = 3$

 Problem 3 – P7.10

P3.2. We will use 0.18um technology and the node names below:



For the two inverter inputs:

$$C_{inv} = C_g(3W) = 2(3)(0.2) = 1.2 \text{ fF}$$

For the pass gate inputs:

$$C_{pass} = C_g(W) = 0.4 \text{ fF}$$

At node x:

$$C_x = C_{eff}(3W) + C_{eff}(2W) + C_g(W) = 1.4 \text{ fF}$$

At node y:

$$C_y = 2(C_{eff}(2W) + C_g(W)) + C_{eff}(2W) = 2 \text{ fF}$$

At node Out:

$$C_{out} = (C_{eff}(2W) + C_g(W)) + C_{eff}(2W) = 1.2 \text{ fF}$$

The shortest path is through the one of the  $G_{ND}$  input nodes to the output:

$$t_{min} = RC_x + 2RC_{out} = (12.5k)(1.4 \text{ fF}) + 2(12.5k)(1.2 \text{ fF}) = 47.5 \text{ ps}$$

The longest path is through one of the inverters to the output.

$$t_{max} = RC_x + 2RC_y + 3RC_{out} = (12.5k)(1.4 \text{ fF}) + 2(12.5k)(2 \text{ fF}) + 3(12.5k)(1.2 \text{ fF}) = 112.5 \text{ ps}$$

Problem 4 – P7.13

(a.) The input settings that give you the worst-case charge sharing are any of  $a = c = e = 1$  and both of  $b = d = 0$ . Essentially, what you are doing is trying to create the greatest amount of parasitic capacitances without creating a path to  $G_{ND}$ .

(b.) Assuming that transistors share nodes to reduce capacitance.

$$C_1 = C_g(5W) + C_d(3W) + C_g(5W) = 5.2\text{fF}$$

$$C_2 = C_d(3W + 3W + 3W) = (1)(9)(0.2) = 1.8\text{fF}$$

$$V^* = \frac{C_1 V_1}{C_1 + C_2} = \frac{(5.2)(1.8)}{5.2 + 1.8} = 1.34\text{V}$$

The actual voltage would be larger than this since the internal node cannot rise above  $V_{DD} - V_T$ .

(c.) This circuit fails if the worst case voltage falls below the switching voltage which can be computed to be  $V_S = 0.92\text{V}$ . Therefore, the circuit will operate properly.