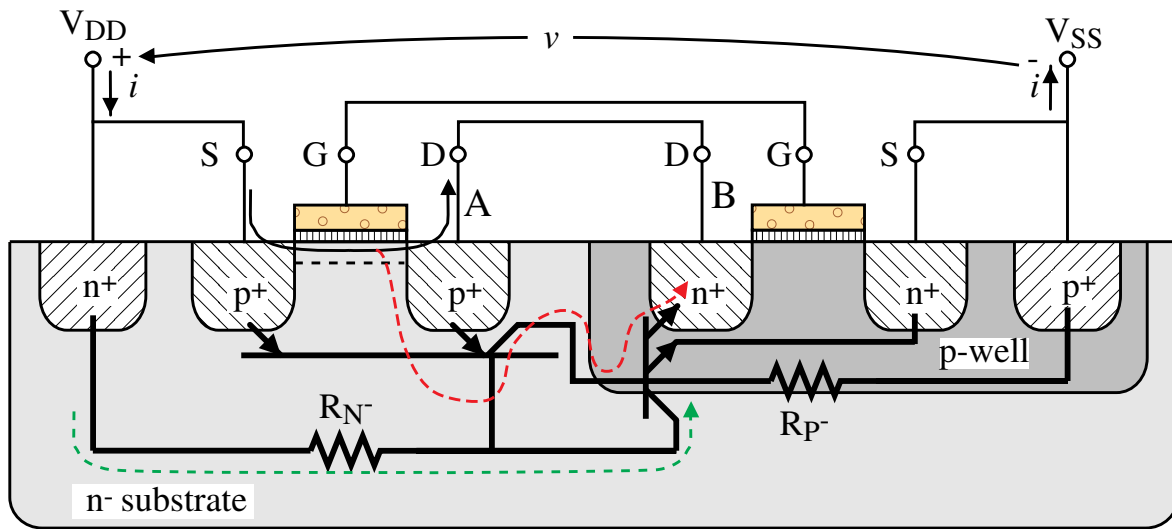


Latch-up in CMOS Technology

Latch-up Mechanisms:

1. SCR regenerative switching action.
2. Secondary breakdown.
3. Sustaining voltage breakdown.

Parasitic lateral PNP and vertical NPN BJTs in a p-well CMOS technology:



031223-01

Equivalent circuit of the SCR formed from the parasitic BJTs:

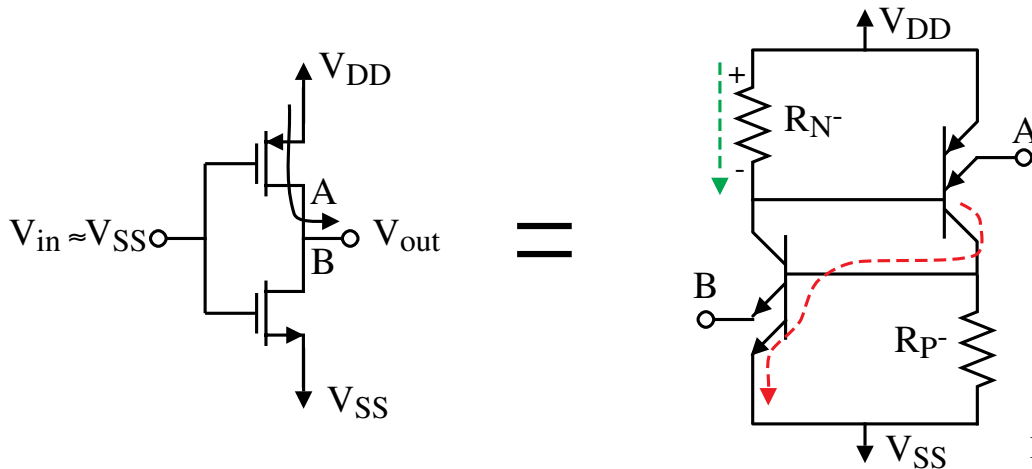


Fig. 190-09

Preventing Latch-Up in a P-Well Technology

- 1.) Keep the source/drain of the MOS device not in the well as far away from the well as possible. This will lower the value of the BJT betas.
- 2.) Reduce the values of R_{N^-} and R_{P^-} . This requires more **current** before latch-up can occur.
- 3.) Make a p^- diffusion around the p-well. This shorts the collector of Q1 to ground.

 


Figure 190-10

For more information see R. Troutman, “CMOS Latchup”, Kluwer Academic Publishers.