
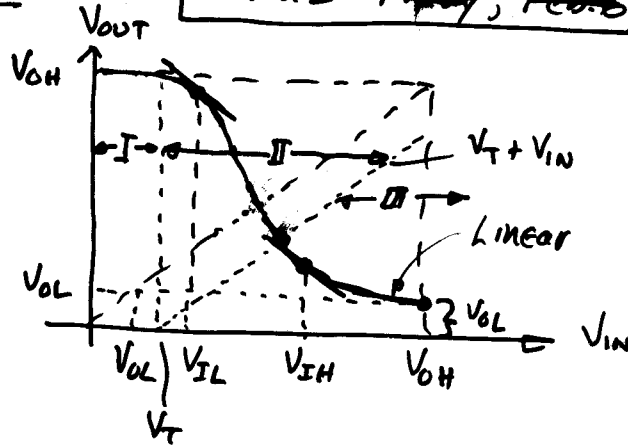
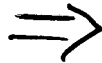


Resistor Load Inverter

Exam 1 ~~Friday, Feb. 6~~
Monday, Feb. 9

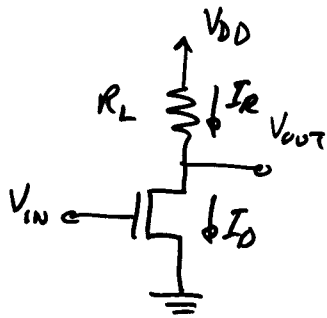

- I - Cutoff
- II - Saturation
- III - Linear

1.) $V_{OH} = V_{DD}$ if $V_{IN} < V_T$ (cutoff)

2.) $V_{OL} = ? \rightarrow$ MOSFET is linear

$$I_R = \frac{V_{DD} - V_{OL}}{R_L} \quad I_D(\text{linear}) = \frac{1}{2} \frac{W_N}{L_N} \left(\frac{\mu_n C_{ox}}{1 + \frac{V_{OL}}{E_c L_N}} \right) \left[2(V_{OH} - V_T)V_{OL} - V_{OL}^2 \right]$$

Assume that $\frac{V_{OL}}{E_c L_N} < 1 \rightarrow I_D(\text{linear}) = \frac{k}{2} \left[2(V_{OH} - V_T)V_{OL} - V_{OL}^2 \right]$

Quadratic -

$$V_{OL}^2 - 2 \left(\frac{1}{kR_L} + V_{DD} - V_T \right) V_{OL} + \frac{2V_{DD}}{kR_L} = 0$$

Or assume $V_{OL} < 1$ so that $V_{OL}^2 \approx 0$

$$\underline{\underline{V_{OL} \approx \frac{V_{DD}}{1 + kR_L(V_{DD} - V_T)}}}$$

3.) $V_{IL} = ?$ Assumptions: MOSFET in saturation and $N_{IN} - V_T$ small

$$I_R = I_D \rightarrow \frac{V_{DD} - N_{OUT}}{R_L} = \frac{W N_{sat} C_{ox} (N_{IN} - V_T)^2}{(N_{IN} - V_T) + E_c L} \approx \frac{W N_{sat} C_{ox} (N_{IN} - V_T)^2}{E_c L}$$

$$\text{Recall, } N_{sat} = \frac{\mu E_c}{2}$$

$$\frac{V_{DD} - N_{OUT}}{R_L} = \frac{\mu C_{ox} W}{2 L} (N_{IN} - V_T)^2 = \frac{k}{2} (N_{IN} - V_T)^2$$

$$\frac{d}{dN_{IN}} \rightarrow -\frac{1}{R_L} \frac{dN_{OUT}}{dN_{IN}} = k (N_{IN} - V_T)$$

$$\text{Setting } \frac{dN_{OUT}}{dN_{IN}} = -1 \rightarrow \frac{1}{R_L} = k (N_{IN} - V_T) = k (V_{IL} - V_T)$$

$$\underline{V_{IL} = V_T + \frac{1}{k R_L}}$$

$$\underline{NM_L = V_{IL} - V_{OL} = V_T + \frac{1}{k R_L} - \frac{V_{DD}}{1 + k R_L (V_{DD} - V_T)}}$$

4.) $V_{IH} = ?$ Assume: MOSFET is linear and $N_{OUT} < E_c L$

$$\frac{V_{DD} - N_{OUT}}{R_L} = \frac{W}{L} \frac{\mu C_{ox}}{1 + \frac{N_{OUT}}{E_c L}} \left[(N_{IN} - V_T) N_{OUT} - \frac{N_{OUT}^2}{2} \right]$$

$$\frac{V_{DD} - N_{OUT}}{R_L} = k \left[(N_{IN} - V_T) N_{OUT} - \frac{N_{OUT}^2}{2} \right]$$

Take the partial derivative w.r.t. N_{IN}

$$k \left[(N_{IN} - V_T) \frac{dN_{OUT}}{dN_{IN}} + N_{OUT} - N_{OUT} \frac{dN_{OUT}}{dN_{IN}} \right] = -\frac{dN_{OUT}}{dN_{IN}} \frac{1}{R_L}$$

$$\left. \begin{aligned}
 k \left[-(N_{IN} - V_T) + 2 N_{OUT} \right] &= \frac{1}{R_L} \\
 \frac{V_{DD} - N_{OUT}}{R_L} &= k \left[(N_{IN} - V_T) N_{OUT} - \frac{N_{OUT}^2}{2} \right]
 \end{aligned} \right\} \underline{V_{IH} = V_T + \sqrt{\frac{8V_{DD}}{3kR_L} - \frac{1}{kR_L}}}$$

$$\therefore \underline{NM_H = V_{OH} - V_{IH} = V_{DD} - V_T - \sqrt{\frac{8V_{DD}}{3kR_L} + \frac{1}{kR_L}}}$$

Example 4.2

Find N_{ML} and N_{MH} if $k' = 430 \frac{\mu A}{V^2}$, $V_T = 0.4V$, $\frac{W}{L} = 2$, $V_{DD} = 1.2V$ and $R_L = 20k\Omega$.

$$V_{OH} = V_{DD} = \underline{1.2V} \quad k = k' \frac{W}{L} = 430 \frac{\mu A}{V^2} \times 2 = 860 \frac{\mu A}{V^2}$$

$$V_{OL} \approx \frac{V_{DD}}{1 + kR_L(V_{DD} - V_T)} = \frac{1.2}{1 + (860)(20)(1.2 - 0.4)} = \underline{0.081V}$$

$$V_{IL} = V_T + \frac{1}{kR_L} = 0.4 + \frac{1}{(0.860)(20)} = \underline{0.46V}$$

$$V_{IH} = V_T + \sqrt{\frac{8V_{DD}}{3kR_L} + \frac{1}{kR_L}} = 0.4 + \sqrt{\frac{8(1.2)}{3(860)(20)} + \frac{1}{(0.860)(20)}}$$


$$\underline{V_{IH} = 0.773V}$$

$$NM_L = V_{IL} - V_{OL} = 0.46 - 0.081 = \underline{0.38V}$$

$$NM_H = V_{OH} - V_{IH} = 1.2 - 0.773 = \underline{0.43V}$$

ACTIVE LOAD INVERTERS

Saturated Enhancement Load Inverter


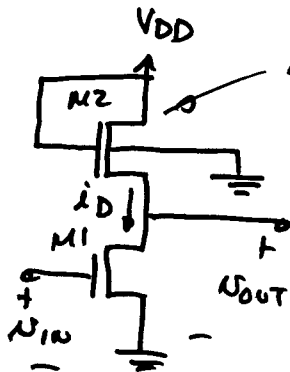


Always saturated ($V_{DS} \approx V_{GS} - V_T$)

$$V_D - V_S \approx V_G - V_S - V_T$$


$$(V_{DG} \approx -V_T)$$
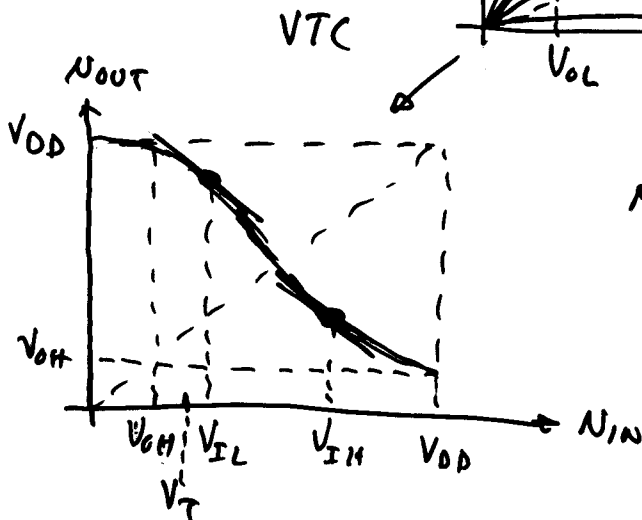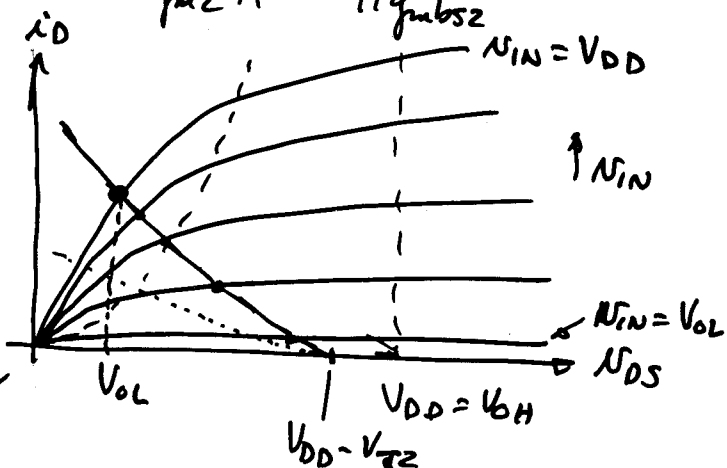
$$R_L = \frac{1}{g_{m2}} \parallel r_{ds2} \parallel \frac{1}{g_{mbs2}}$$




Problem: $V_{T2} = f(V_{OUT})$

"CMOS Equivalent"

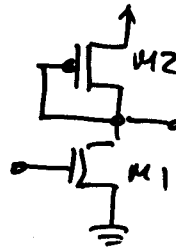

Linear Enhancement Load Inverter

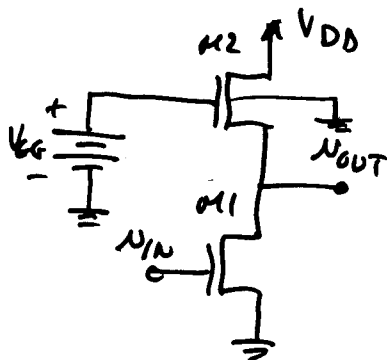

More gain

Disadvantages:

1. Must provide V_{GG} .
2. More chip area reqd.
3. More power dissipation

