
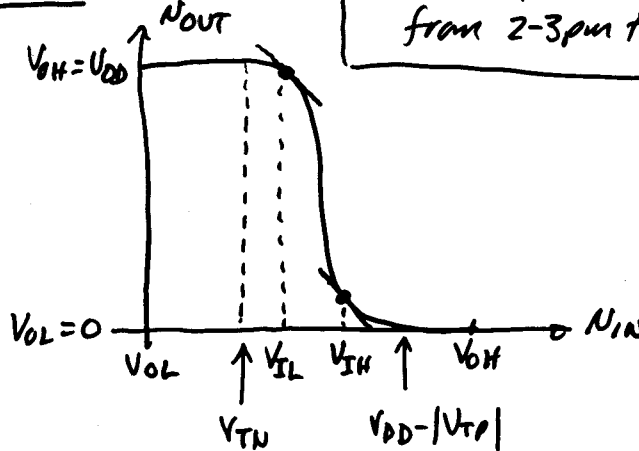


Exam No. 1 - Monday, Feb. 9, 2004, 12:05-12:55pm, C341
 Problem Session - Sunday, Feb. 8, 2004, 4-5pm, C341?

CMOS Inverters

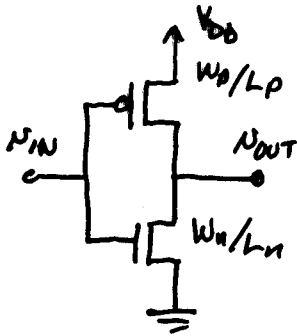

Wednesday off are moved from 2-3pm to 3-4pm

$V_{IL} = ?$ (NMOS sat., PMOS lin.)

$$\frac{W_n \mu_{sat} C_{ox} (N_{IN} - V_{TN})^2}{(N_{IN} - V_{TN}) + E_{CN} L_n} = \frac{W_p}{L_p} \left(\frac{\mu_p C_{ox}}{1 + \frac{V_{DD} - N_{OUT}}{E_{CP} L_p}} \right) \left[(V_{DD} - N_{IN} - |V_{TP}|)(V_{DD} - N_{OUT}) - \frac{(V_{DD} - N_{OUT})^2}{2} \right]$$

Assumptions: $N_{IN} - V_{TN} \approx 0$ and $N_{OUT} \approx V_{DD} \rightarrow \frac{V_{DD} - N_{OUT}}{E_{CP} L_p} \approx 0$

$$\text{Eq. (1)} \quad \frac{W_n \mu_n}{L_n} \frac{(N_{IN} - V_{TN})^2}{2} = \frac{W_p \mu_p}{L_p} \left[(V_{DD} - N_{IN} - |V_{TP}|)(V_{DD} - N_{OUT}) - \frac{(V_{DD} - N_{OUT})^2}{2} \right]$$

$$\frac{\partial}{\partial N_{IN}} \rightarrow \frac{W_n \mu_n}{L_n} (N_{IN} - V_{TN}) = \frac{W_p \mu_p}{L_p} \left[(V_{DD} - N_{IN} - |V_{TP}|) \left(-\frac{\partial N_{OUT}}{\partial N_{IN}} \right) + (V_{DD} - N_{OUT})(-1) - (V_{DD} - N_{OUT}) \left(-\frac{\partial N_{OUT}}{\partial N_{IN}} \right) \right]$$

If $k_n \equiv \mu_n \frac{W_n}{L_n}$ and $k_p \equiv \mu_p \frac{W_p}{L_p}$ ($N_{OUT} = \bar{V}_{OUT}$)

and $N_{IN} = V_{IL}$, then

$$\text{Eq. (2)} \quad V_{IL} = \frac{2V_{OUT} - V_{DD} - |V_{TP}| + (k_n/k_p) V_{TN}}{1 + \frac{k_n}{k_p}} \quad \begin{array}{l} \text{Use Eqs. (1)} \\ \text{and (2)} \\ \text{to solve} \\ \text{for } V_{IL} \\ \text{or} \end{array}$$

If $V_{OUT} \approx V_{DD}$, $V_{IL} \approx \frac{V_{DD} - |V_{TP}| + (k_n/k_p) V_{TN}}{1 + (k_n/k_p)}$

$$\underline{V_{IH} = ?}$$

$$i_{DN}(\text{lin}) = i_{DP}(\text{sat.})$$

$$\frac{W_n}{L_n} \left(\frac{\mu_n C_{ox}}{1 + \frac{N_{OUT}}{E_{cn} L_n}} \right) \left[(N_{IN} - V_{TN}) N_{OUT} - \frac{N_{OUT}^2}{2} \right] = \frac{W_p N_{sat} C_{ox} (V_{DD} - N_{IN} - |V_{TP}|)^2}{(V_{DD} - N_{IN} - |V_{TP}|) + E_{cp} L_p}$$

Assumptions: $\frac{N_{OUT}}{E_{cn} L_n} < 1$ and $(V_{DD} - N_{IN} - |V_{TP}|) < E_{cp} L_p$

$$\mu_n C_{ox} \frac{W_n}{L_n} \left[(N_{IN} - V_{TN}) N_{OUT} - \frac{N_{OUT}^2}{2} \right] = \frac{\mu_p C_{ox} W_p}{2 L_p} (V_{DD} - N_{IN} - |V_{TP}|)^2 \quad \text{Eq. (1)}$$

$$k_n = \mu_n C_{ox} \frac{W_n}{L_n} \quad \text{and} \quad k_p = \mu_p C_{ox} \frac{W_p}{L_p}$$

$$\text{Eq. (1) - } k_n \left[(N_{IN} - V_{TN}) N_{OUT} - \frac{N_{OUT}^2}{2} \right] = \frac{k_p}{2} (V_{DD} - N_{IN} - |V_{TP}|)^2$$

$$\frac{\partial}{\partial N_{IN}} \left[\dots \right] = 0$$

$$\text{Eq. (2) } N_{IN} = V_{IH} \quad \text{and} \quad N_{OUT} = V_{OUT}$$

$$V_{IH} = \frac{2V_{OUT} + V_{TN} + \left(\frac{k_p}{k_n}\right)(V_{DD} - |V_{TP}|)}{1 + \left(\frac{k_p}{k_n}\right)}$$

Solve Eqs. (1) and (2) for V_{IH} .

An approx. $V_{OUT} \approx 0 \rightarrow V_{IH} \approx \frac{V_{TN} + \left(\frac{k_p}{k_n}\right)(V_{DD} - |V_{TP}|)}{1 + \frac{k_p}{k_n}}$

Example

Find NM_H and NM_L for a CMOS inverter if

$$W_n = 400\text{nm}, W_p = 800\text{nm}, \mu_n = 270 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}, \mu_p = 70 \frac{\text{cm}^2}{\text{V}\cdot\text{s}},$$

$$C_{ox} = 1\text{mF}/\text{cm}^2, V_{TN} = 0.5\text{V}, V_{TP} = -0.5\text{V}, E_{cn}L_n = 1.2\text{V},$$

$$E_{cp}L_p = 4.8\text{V}, N_{sat} = 8 \times 10^6 \frac{\text{cm}}{\text{s}}, V_{DD} = 1.8\text{V} \text{ and } L_p = L_n = 200\text{nm}.$$

Solution:

$$V_{OH} = V_{DD} = 1.8\text{V} \text{ and } V_{OL} = 0\text{V}$$

$$k_n = \mu_n C_{ox} \frac{W_n}{L_n} = 540 \frac{\mu\text{A}}{\text{V}^2} \text{ and } k_p = \mu_p C_{ox} \frac{W_p}{L_p} = 280 \mu\text{A}/\text{V}^2$$

$$V_{IL} = ?$$

$$\text{Eq. (2)} \rightarrow V_{IL} = \frac{2V_{OUT} - 1.8 - 0.5 + \left(\frac{540}{280}\right)0.5}{1 + \frac{540}{280}}$$

$$V_{OUT} = 0.7593 V_{IL} - 0.5875$$

$$\text{Eq. (1)} \quad \frac{540}{2} (V_{IL} - 0.5)^2 = 280 \left[(1.8 - V_{IL} - 0.5)(1.8 - V_{OUT}) - \frac{(1.8 - V_{OUT})^2}{2} \right]$$

Too simplify, assume that $V_{OUT} \approx 1.8 \rightarrow (1.8 - V_{OUT})^2 \approx 0$

$$(V_{IL} - 0.5)^2 = 1.037 \left[(1.3 - V_{IL})(1.8 - V_{OUT}) \right]$$

$$\text{Quadratic} \rightarrow V_{IL}^2 - 4.14V_{IL} + 2.46 = 0 \rightarrow \underline{V_{IL} = 0.719\text{V}}$$

$$\underline{V_{IH} = ?}$$

$$\text{Eq. (2)} \quad V_{IH} = \frac{2V_{OUT} + 0.5 + \frac{280}{540}(1.8 - 0.5)}{1 + \frac{280}{540}}$$

(SPICE:
0.622V)

$$V_{OUT} = 0.7593 V_{IH} - 0.5875$$

$$\text{Eq. (1)} \quad 540 \left[(V_{IH} - 0.5)V_{OUT} - \frac{V_{OUT}^2}{2} \right] = \frac{280}{2} \left[1.8 - V_{IH} - 0.5 \right]^2$$

Assume that $V_{OUT} \approx 0$ so that $V_{OUT}^2 \approx 0$

$$\circ (V_{IH} - 0.5)V_{OUT} \approx \frac{280}{2.540} [1.3 - V_{IH}]^2$$

↑
Eq. (2)

(SPICE:
0.909)

$$V_{IH}^2 - 0.699V_{IH} - 0.3088 = 0 \rightarrow \underline{\underline{V_{IH} = 0.954}}$$

Finally,

$$NM_H = V_{OH} - V_{IH} = 1.8 - 0.954 = 0.846V \quad (0.891)$$

$$NM_L = V_{IL} - V_{OL} = 0.719 - 0 = 0.719V \quad (0.676)$$