
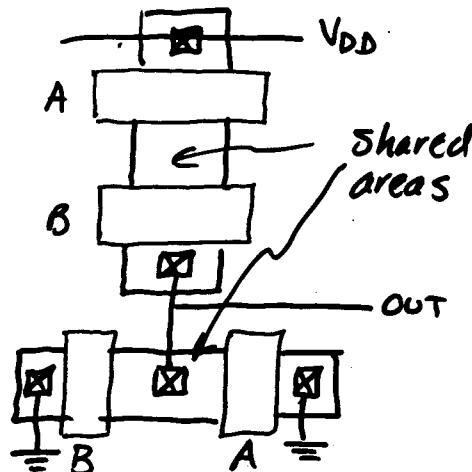


Capacitance of NOR2

(Problem session - Thurs. 3/4 at 7pm)

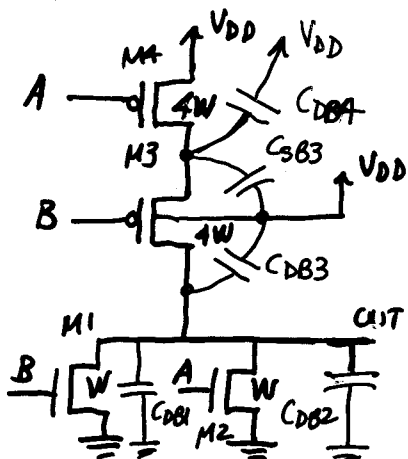

$$C_{load} = C_{self} = \underbrace{C_{DB1} + C_{DB2}}_{\text{shared}} + C_{DB3} + \underbrace{C_{SB3} + C_{DB4}}_{\text{shared}}$$



$$C_{load} = C_{eff}(W_n) + C_{eff}(W_p) + C_{eff}(W_p)$$

$$= C_{eff}[W_n + 2W_p] = 9W C_{eff} = 9W (1fF/\mu m)$$

$$C_{in}(\text{worst case}) = C_g(W_n + W_p) = 5W C_g = 5W (2fF/\mu m)$$

NAND3 Example

  Find  $C_{in}$  (worst case) and  $C_{load}$  if  $W = 0.4\mu m$ .



$$C_{in}(\text{worst case}) = C_g(W_n + W_p) = 5W C_g = 5(0.4)(2) = \underline{\underline{4fF}}$$


$$C_{load} = C_{self}[2W_p + 3W_n] = (1fF/\mu m)[4W + 9W] = 13(0.4)(1) = \underline{\underline{52fF}}$$

## Switching Implications on Gates from a Speed Viewpoint

In a series logic stack, the delay from the input to the output increases the further away a transistor is from the output.

Suppose the following circumstances:

 
- 1.) A is late, only  $C_L$  needs to be charged
- 2.) If B is late, both  $C_x$  and  $C_L$  must be charged.
- 3.) If C is late, the  $C_L + C_x + C_y$  must be charged.



- o. Move a transistor with a delayed input closest to the output.

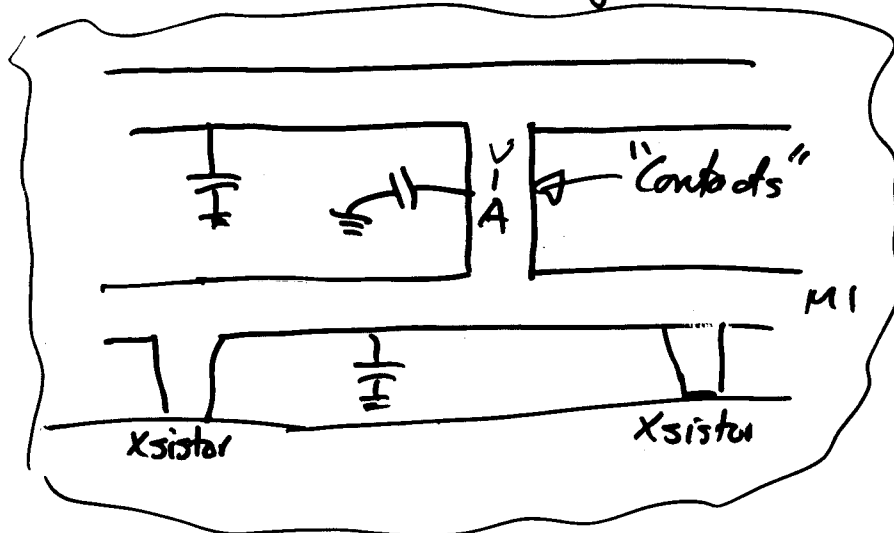
## Wiring Capacitance

$$C_{\text{wire}} = (0.2 \text{ fF}/\mu\text{m}) \times (\text{Length of the conductor})$$




So far, all inputs have been step inputs

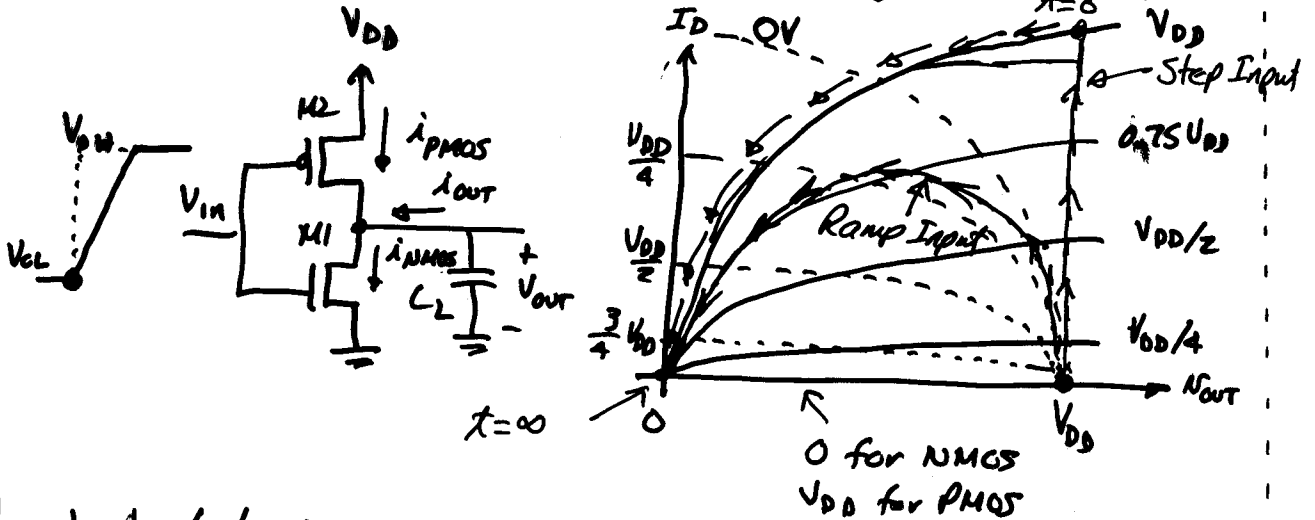Improving the Delay Calculations including the input stage



 1.) Analytical Expression for a Delay with a Step Input




$$i_{out} \approx i_{max} = C_L \frac{dV_{out}}{dt}$$

$$i_{out} = C_L \frac{\Delta V}{\Delta t} = C_L \frac{0.5V_{DD}}{t_{PHL(step)}}$$

$$t_{PHL(step)} = C_L \frac{V_{DD}}{2 i_{max}}$$

 2.) Analytical Expression for a Delay with a Ramp Input



$$t_{PHL(ramp)} = \frac{t_r}{4} + t_{PHL(step)}$$