


Improving the Delay Calculations including the Input Stage

1.) Step input

$$t_{PHL}(\text{step}) = C_L \frac{V_{DD}}{2 I_{max}}$$

Problem Session
on 3/4 at 7pm

2.) Ramp input

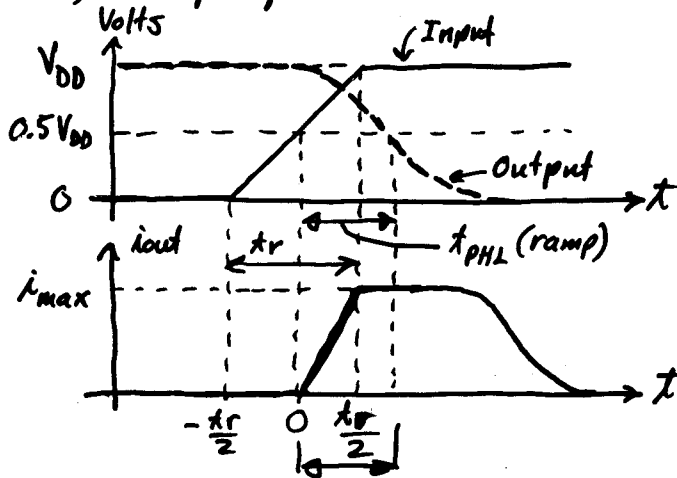

$$i_{out} = C_L \frac{dV_{out}}{dt} \quad V_{DD}/2$$

$$t_{PHL} \int_0^{t_{PHL}} i_{out} dt = C_L \int_0^{t_{PHL}} dV_{out}$$

$$\int_0^{t_{PHL}} i_{max} \left(\frac{t}{t_r/2} \right) dt + \int_{t_r/2}^{t_{PHL}} I_{max} dt$$

$$= C_L \frac{V_{DD}}{2}$$

$$\frac{I_{max}}{0.5 k_r} \left. \frac{t^2}{2} \right|_0^{t_r/2} + I_{max} t \left. \right|_{t_r/2}^{t_{PHL}(\text{ramp})} = C_L \frac{V_{DD}}{2} \quad t_{PHL}(\text{step})$$

$$I_{max} \left(\frac{t_r}{4} \right) + I_{max} \left[t_{PHL}(\text{ramp}) - \frac{t_r}{2} \right] = \frac{C_L V_{DD}}{2} = \frac{C_L V_{DD}}{2 I_{max}}$$


$$\frac{t_r}{4} + t_{PHL}(\text{ramp}) - \frac{t_r}{2} = t_{PHL}(\text{step})$$

$$\therefore \boxed{t_{PHL}(\text{ramp}) = \frac{t_r}{4} + t_{PHL}(\text{step})}$$

If t_{in} is the input rise or fall time, then

$$t_{ramp} \approx \frac{t_{in}}{2} + t_{step} = \frac{t_{in}}{2} + 0.7RC$$

Inverter Chain Delay

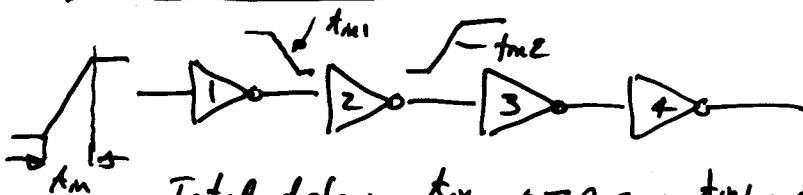


$$\text{Total delay} = \frac{t_{in}}{2} + 0.7R_1C_1 + \frac{t_{m1}}{2} + 0.7R_2C_2 + \frac{t_{m2}}{2} + 0.7R_3C_3 + \frac{t_{m3}}{2} + 0.7R_4C_4$$

$$\text{Total delay} = \frac{t_{in}}{2} + 0.7R_1C_1 + 0.7\frac{R_1C_1}{2} + 0.7R_2C_2 + \frac{0.7R_2C_2}{2} + 0.7R_3C_3 + \frac{0.7R_3C_3}{2} + 0.7R_4C_4$$


$$\text{Total delay} \approx \frac{t_{in}}{2} + R_1C_1 + R_2C_2 + R_3C_3 + 0.7R_4C_4 = \sum_{i=1}^n R_i C_i \approx R_4 C_4$$

Gate Sizing for Optimal Delay

The problem: Minimize the global delay.

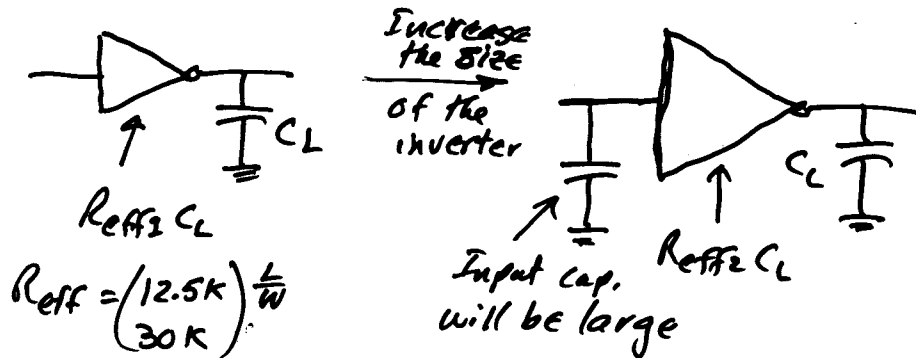

Inverter Delay

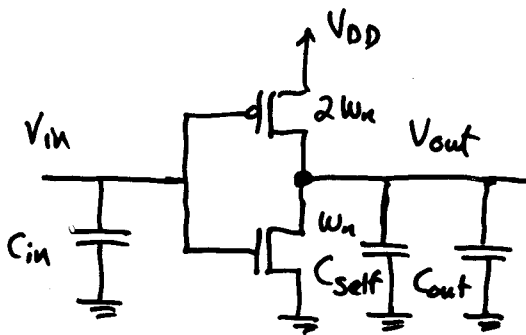

Define the gate time constant of an inverter as,

$$\tau_{inv} = R_{eff} C_{in}$$

$$\tau_{inv} = R_{eqn} \left(\frac{L_n}{W_n} \right) C_g (3W_n) = 3R_{eqn} C_g L_n$$

$$t_{delay} = R_{eff} [C_{self} + C_{out}] \times \frac{C_{in}}{C_{in}} = R_{eff} C_{in} \left[\frac{C_{self}}{C_{in}} + \frac{C_{out}}{C_{in}} \right]$$

$$t_{delay} = \tau_{inv} \left[\frac{C_{out}}{C_{in}} + \gamma_{inv} \right] \quad \text{where} \quad \gamma_{inv} = \frac{C_{self}}{C_{in}}$$

Note: $\frac{C_{out}}{C_{in}} = f_{out} = f$ and C_{self} is strongly dependent on layout


Exercise 6.3

Find τ_{inv} and δ_{inv} for an inverter in 0.12 μm technology

$$\tau_{inv} = 3R_{eq} C_g L_n = 3(12.5 \text{ k}\Omega)(2 \text{ fF}/\mu\text{m})(0.2 \mu\text{m}) = 15 \text{ ps}$$

$$\delta_{inv} = \frac{C_{self}}{C_{in}} = \frac{C_{eff}(3W)}{C_g(3W)} = \frac{1 \text{ fF}/\mu\text{m}}{2 \text{ fF}/\mu\text{m}} = \frac{1}{2}$$

$$0 < \delta_{inv} < 2$$

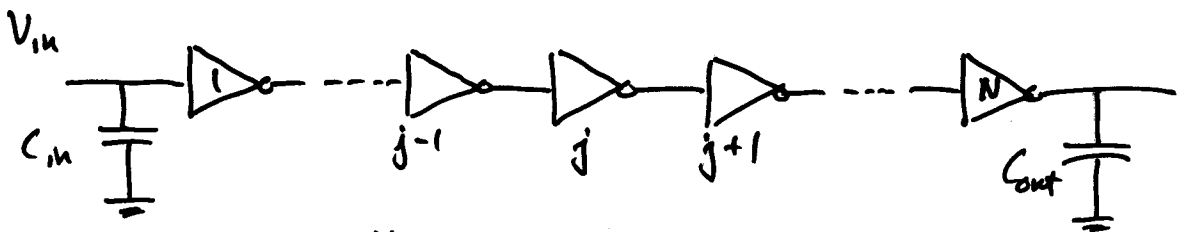Optimal Sizing on An Inverter Chain

$$\text{Total Delay} = \sum_{j=1}^N \tau_{inv} \left(\frac{C_{j+1}}{C_j} + \delta_{inv} \right) = \sum_{j=1}^N \tau_{inv} \left(\frac{C_j W_{j+1}}{C_j W_j} + \delta_{inv} \right)$$

Define the consecutive delay as

$$D_j = \tau_{inv} \left(\frac{W_j}{W_{j-1}} + \delta_{inv} \right) + \tau_{inv} \left(\frac{W_{j+1}}{W_j} + \delta_{inv} \right)$$

$$\frac{\partial D_j}{\partial W_j} = 0 \rightarrow \frac{\partial D_j}{\partial W_j} = \tau_{inv} \frac{1}{W_{j-1}} - \tau_{inv} \left(\frac{W_{j+1}}{W_j^2} \right) = 0$$

$$\frac{W_j}{W_{j-1}} = \frac{W_{j+1}}{W_j} \rightarrow \underline{\underline{W_j = \sqrt{W_{j+1} W_{j-1}}}}$$


In general,

$$W_j = (W_1 W_2 \cdots W_{j-1} W_{j+1} \cdots W_{N-1} W_N)^{1/N}$$

Q. How do we achieve geometrical sizing?

A. We will increase size of each inverter by the fanout = $\frac{W_{j+1}}{W_j}$

$$f_j \equiv \frac{W_{j+1}}{W_j}$$

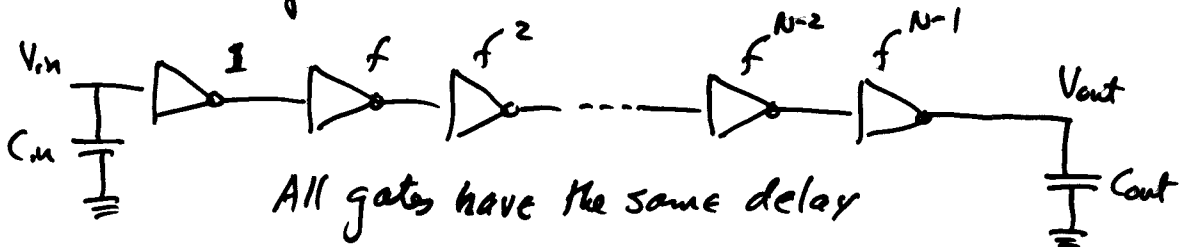

Note that: $C_{out} = f^N C_{in} \rightarrow N = \frac{\ln(C_{out}/C_{in})}{\ln f}$

What optimizes the problem is knowing f and N given C_{in} and C_{out} .

$$\text{Total Delay} = N \times \text{Gate Delay} = N \times \tau_{inv} \left(\frac{C_{j+1}}{C_j} + \tau_{inv} \right)$$

$$\text{Total Delay} = \frac{\ln(C_{out}/C_{in})}{\ln f} \times \tau_{inv} (f + \tau_{inv})$$

For $\tau_{inv} = 0 \rightarrow f = e = 2.72$

$0.5 < \tau_{inv} < 2 \rightarrow 2.5 < f < 4$

Ex. 6.9

a.) Find the optimal fanout for $N=3$ and total delay if

$C_{out} = 200\text{fF}$ and $C_{in} = 1\text{fF}$. Assume $\tau_{inv} = 7.5\text{ps}$ & $\tau_{in0} = 0.5$

$$\ln f = \frac{\ln(C_{out}/C_{in})}{N} = \frac{\ln 200}{3} = 1.766 \rightarrow f = \underline{\underline{5.85}}$$

$$\text{Total delay} = 3(7.5\text{ps})(5.85 + 0.5) = \underline{\underline{143\text{ps}}}$$

b.)