
 



Transmission Gate

 


Multiplexers Using CMOS Transfer Gates





XOR Gate

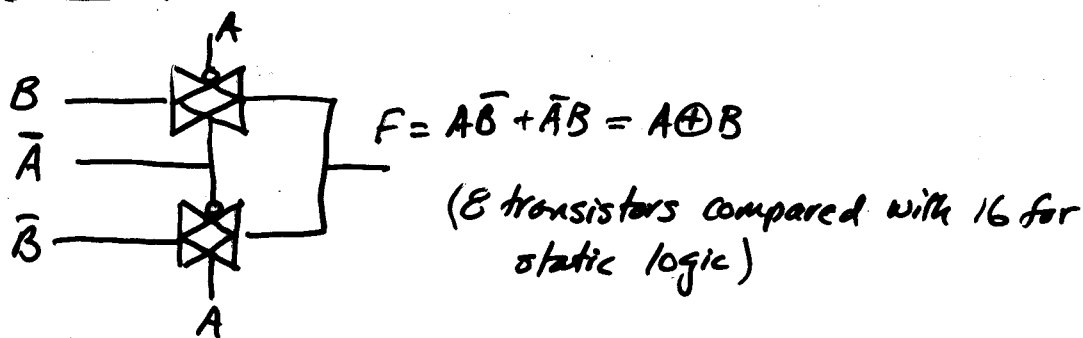

XNOR Gate

 

Multiplexer -

 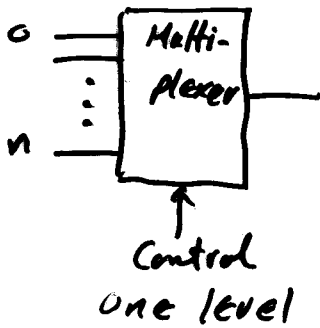


Tradeoffs between single and multiple-level MUXs

Single has less control signals, quicker

Multiple has less inverter (logic) → Less area  
Slower


Output conflicts for MUXs

1.) Two defined paths conflict

 


2.) No defined paths

Hi Z state

 

3.) Charge sharing

 

## Implementation of Logic Functions

- 1.) Identify the control signals
- 2.) Build truth table
- 3.) Convert the truth table to a multiplexer-style design by creating a path for each row to the output.
- 4.) The desired outputs are routed from input to the output.

### Example 1


$$F = AB + A\bar{B}C + \bar{A}\bar{C}$$

- 1.) Let  $A$  &  $B$  be the control signals.

- 3.) Use a two-level MUX

2.)

A	B	F
0	0	$\bar{C}$
0	1	$\bar{C}$
1	0	C
1	1	1

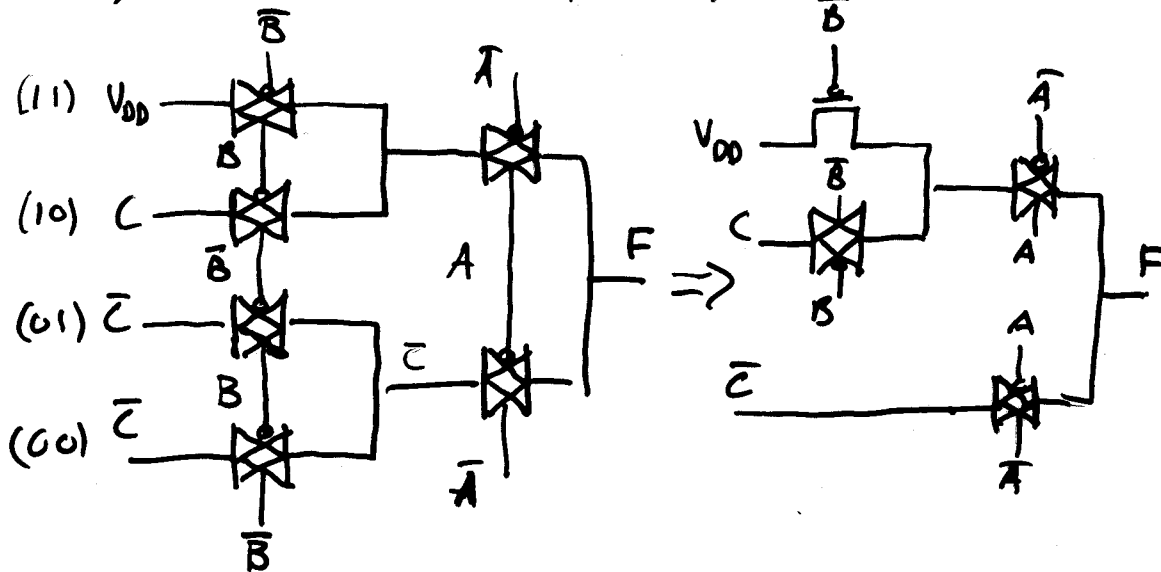

Note that you can also combine TEs and static logic gates for efficient implementation of logic functions


## Problem 7.4 (c)

$$Out = \overline{(A+B+C)} + \bar{A}B = \bar{A}\bar{B}\bar{C} + \bar{A}B$$

Let A and B be the control signals

A	B	C	Out
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

A	B	Out
0	0	1
0	1	1
1	0	0
1	1	0

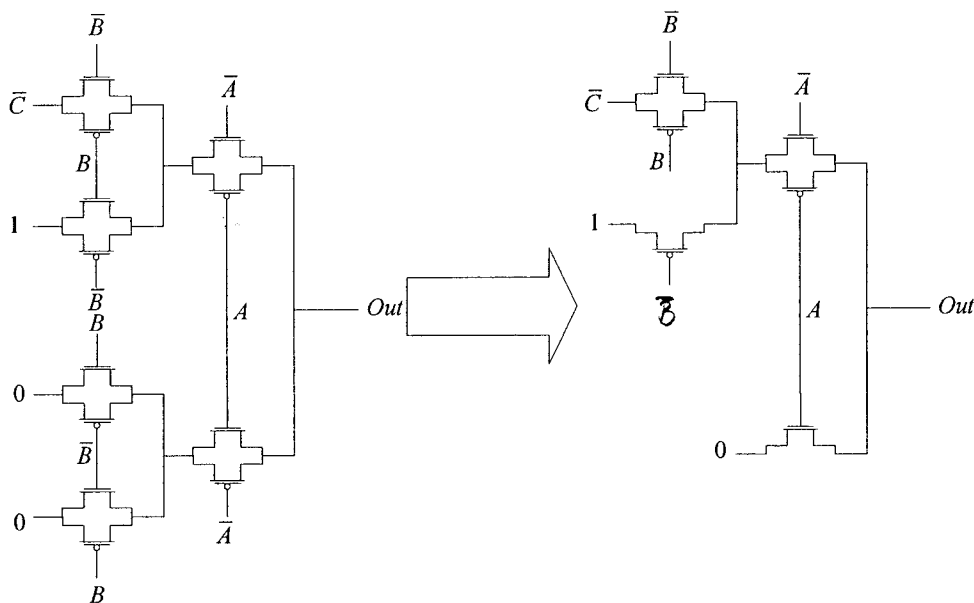


## Problem 7.4(b)


$$Out = \overline{\overline{(A+B+C)}} + \overline{AB} = \overline{ABC} + \overline{AB} = \overline{AB}(C+1) = \overline{AB} = A+B$$

A	B	C	Out
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

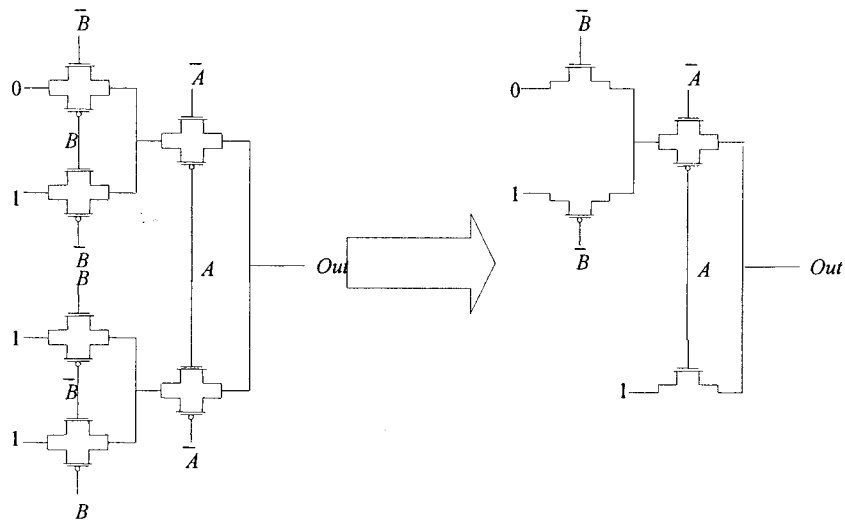

CMOS TG Delays

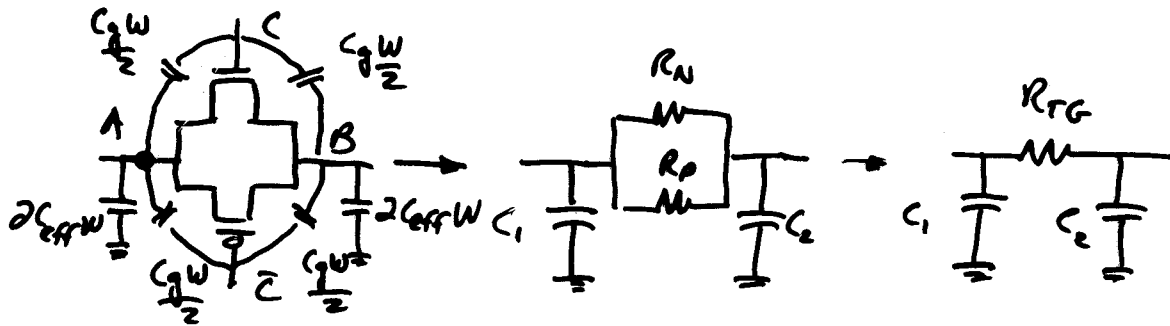

Delay = RC

R = ?

1.) For the propagation of a  $V_{DD}$ ,

$R_{TG} = R_N || R_P = 2R_{eqn} || R_{eqp} = 2R_{eqn} || 2.4R_{eqn} \approx 1.1R_{eqn} \approx R_{eqn}$

$\frac{30K}{12.5K}$

2.) For the propagation of a 0, Approx. PMOS as twice the normal resistance  
 $R_{TG} = R_N || R_P \approx R_{eqn} || 4.8R_{eqn} = 0.83 \approx R_{eqn}$


Bottom line:  $R \approx R_{eqn}$ .

C = ?


1.) Off state:  $C_1 = C_2 = C_{in} = C_{out} = C_{eff}(W_n + W_p) = 2WC_{eff}$

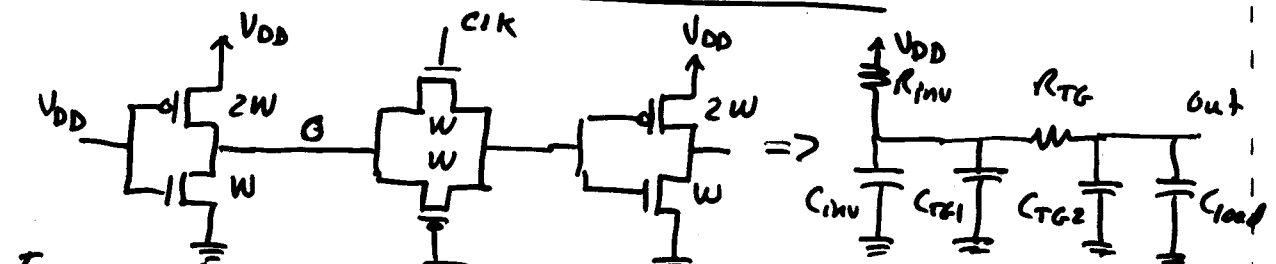2.) ON state:  $C_1 = C_2 = C_{eff}(W_n + W_p) + \frac{1}{2}(C_g W_n + C_g W_p)$   
 $= 2C_{eff}W + WC_g$

Transmission Gate with a Driver and a Load



In general,

 

Elmore's Delay -

$t_{Elmore} = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 + \dots$