 


Exam #3 scheduled for 4/16/04 has been moved to 4/14/04.  
 Conflicts: Contact Dr. Allen by e-mail before 4/14.

Transmission Gates combined with Inverter (Driver) —


Elmore Delay:



$$\text{Delay at input} = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 + \dots$$

Ex. 7.4

 Find the Elmore delay for the path shown where the fanout of 1X inverter at the output of the MUX is f.



$$t_1 = R_{inv} C_1 + (R_{inv} + R_{TG}) C_2 + (R_{inv} + 2R_{TG}) C_3$$

$$R_{inv} = R \quad R_{TG} = R$$

$$C_1 = 3WC_{eff} + 2WC_{eff} + WC_g$$

$$C_2 = 5WC_{eff} + WC_g$$

$$C_3 = 2(2WC_{eff} + WC_g) + 2WC_{eff} = 6WC_{eff} + 2WC_g$$


$$C_3 = 3WfC_g + 2WC_{eff} + WC_g + 2WC_{eff}$$

$$C_3 = 4WC_{eff} + WC_g (1 + 3f)$$

Review:

OFF TG:  $C_{in} = 2WC_{eff}$

 ON TG:  $C_m = 2WC_{eff} + \frac{1}{2}C_g W + \frac{1}{2}C_g W = 2WC_{eff} + WC_g$



$$t_1 = RW [5C_{eff} + 2C_g] + 2RW [C_{eff} + 2C_g]$$

$$+ 3RW [4C_{eff} + C_g + 3fC_g]$$


$$t_1 = RW [29C_{eff} + 8C_g + 9fC_g]$$

Logical Effort for CMOS TG's

Recall that  $LE = \frac{\tau_{gate}}{\tau_{inv}} = \frac{\tau_{gate}}{3WR C_g}$   $\tau = (\text{Pullup } R)(\text{Input } C)$

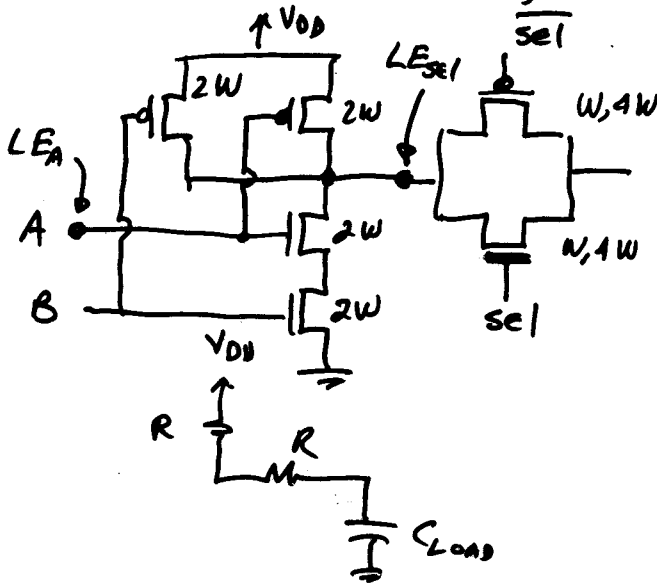Example 7.5

Compute the  $LE_A$  and  $LE_{sel}$  for the NAND gate shown which drives a TG with a.) Width of TG =  $W$  b.) Width of TG =  $4W$ .



$W:$   
 $LE_A = \frac{\tau_{gate}}{3WR C_g} = \frac{2R(4WC_g)}{3WR C_g} = \frac{8}{3}$


$LE_{sel} = \frac{2R(WC_g)}{3WR C_g} = \frac{2}{3}$

$4W:$   
 $LE_A = \frac{4WC_g(R + \frac{R}{4})}{3WR C_g} = \frac{5}{3}$

$LE_{sel} = \frac{WC_g(R + \frac{R}{4})}{3WR C_g} = \frac{5}{3}$


DYNAMIC D-LATCHES AND D FLIP-FLOPS

Evolution of Simple D-Latches using TG's

 


 
Problems:

- Propagation of  $V_{DD}$
- Clock feed thru
- No  $\bar{Q}$  available
- Output is hi-Z when clk goes low



Solves:

  - Propagation of  $V_{DD}$
- Somewhat solves the clock feed thru



New problem:

When CLK goes high, the delay before  $\overline{CLK}$  goes low can cause a conflict at Q between TG1 and TG2

Solution 1: Size the gates so that the forward path is stronger than the feedback path.

Solution 2:

