 


Solution to the internal node conflict for the simple D-latch -



CLK = 1: Transparent mode (has a delay of  $TG + 2 \cdot INV$ )

D = 0:  $\rightarrow \bar{Q} = 1$  (M1 ON, M2 OFF, M3 OFF, M4 OFF)

D = 1:  $\rightarrow \bar{Q} = 0$  (M1 OFF, M2 OFF, M3 OFF, M4 ON)

CLK = 0: Hold mode (latch mode)

D = 0:  $\rightarrow \bar{Q} = 1$  (M1 ON, M2 ON, M3 ON, M4 OFF)


D = 1:  $\rightarrow \bar{Q} = 0$  (M1 OFF, M2 ON, M3 ON, M4 ON)

Master-Slave D Flip-Flop


(see next page)

Dynamic Logic


Evolution -

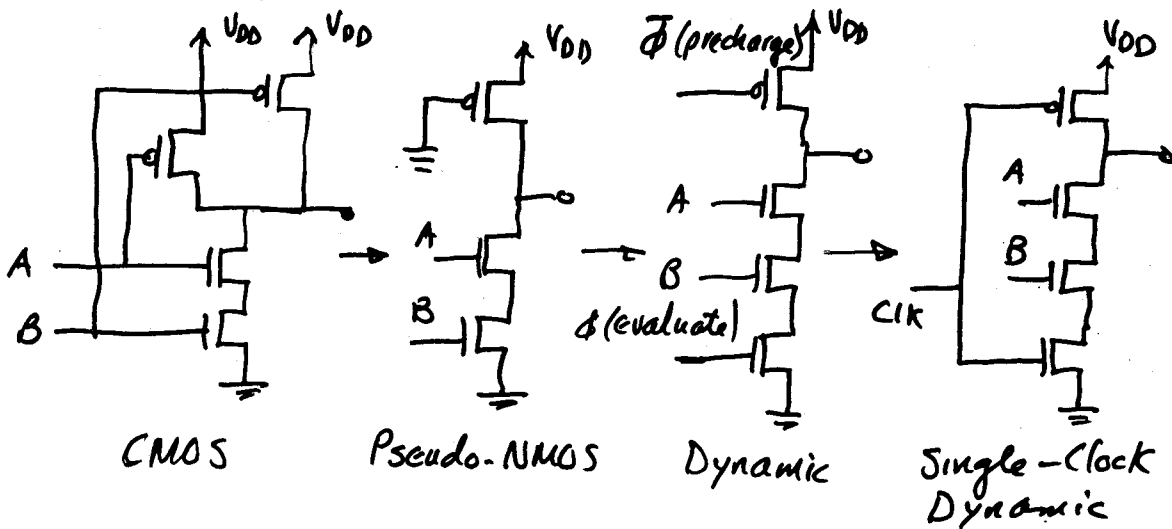

**Figure 7.24 – Positive edge-triggered D-type flip-flop**

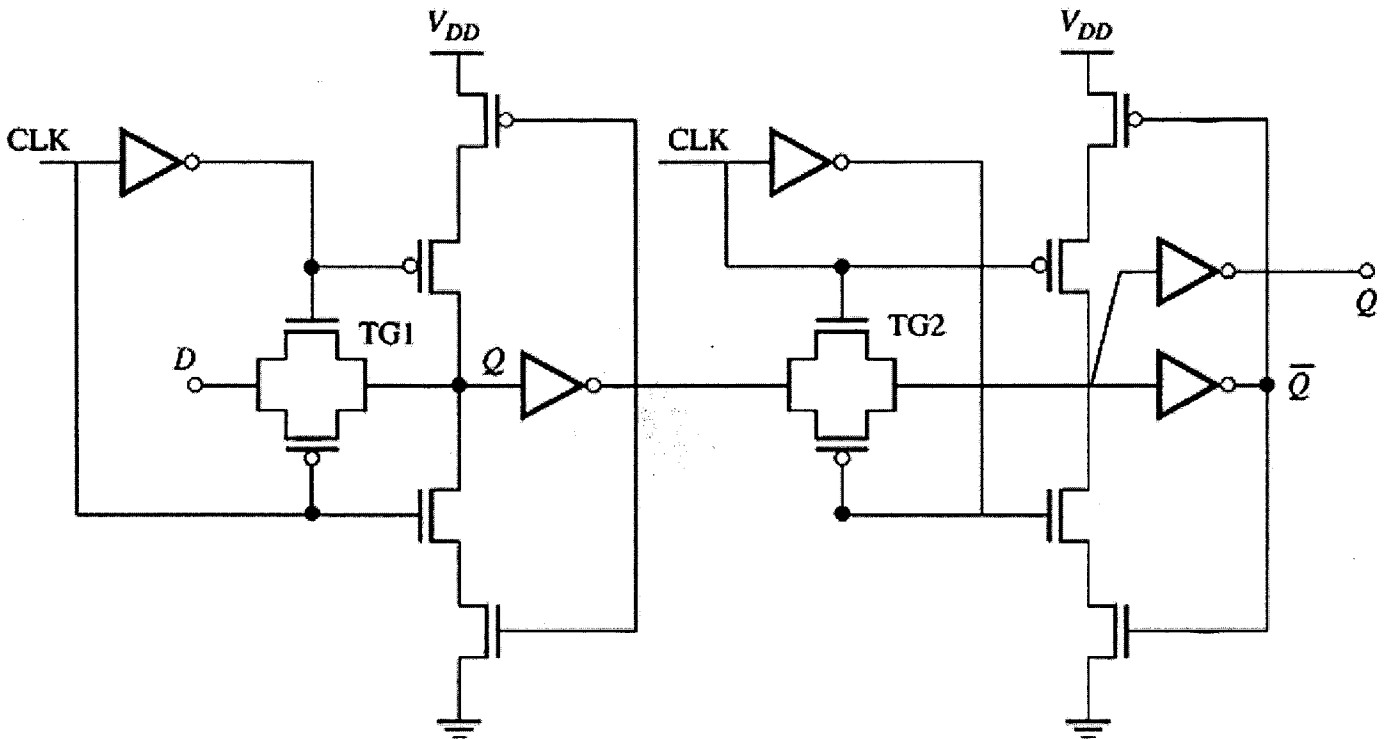

 Positive edge of the CLK shuts off the first latch and enables the second.




CLK=0: 1st latch is transparent  
2nd latch is disabled

CLK=1: TG1 shuts off and holds D at its output (of 1st latch)  
TG2 allows Q to flow to the output.


Since D is only transmitted to the output on the rising edge of the clock, this ff is positive edge triggered.

3-input Dynamic NOR gate

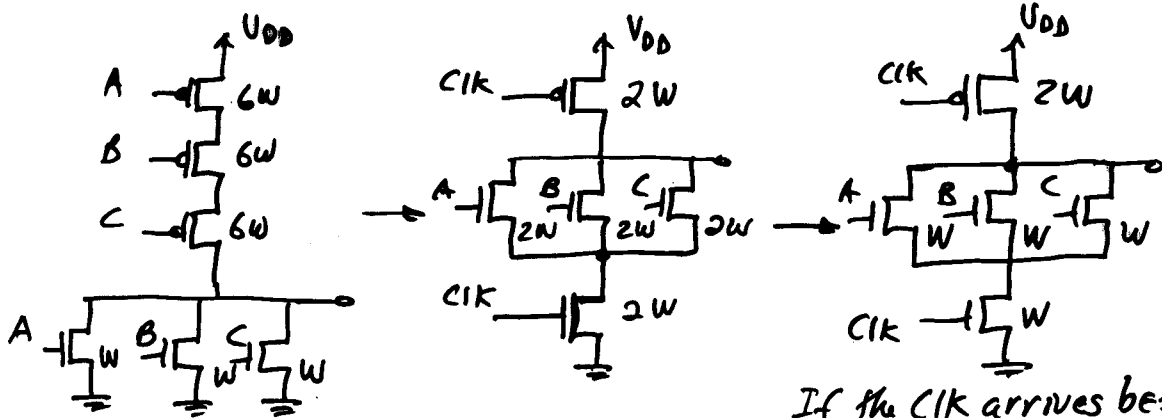

If the CLK arrives before A, B, or C.

General structure of a dynamic gate

 

All stages are precharged to  $V_{DD}$  when  $\phi = 0$

When  $\phi = 1$ , the internal nodes will charge from left to right assuming that there is a path to ground thru the various NMOS complexes


Domino Logic - Some Observations

- 1.) Since the output is already high, we can speed up the gate by increasing the sizes of the NMOS transistors
- 2.) Since there is no pull-up fighting the pull down a domino stage will actually switch faster than a regular gate.

 - 3.) Power savings - only those gates that discharge the output node to ground will dissipate power.
- 4.) Domino logic can only be used to create a non-inverting logic function.

Logic Effort for Domino Gates

Static NOR2 with a dynamic (domino) NOR2 -




$L = 2λ$

Static NOR2

$$LE_{NOR} = \frac{NOR\ input\ C}{INV\ input\ C}$$
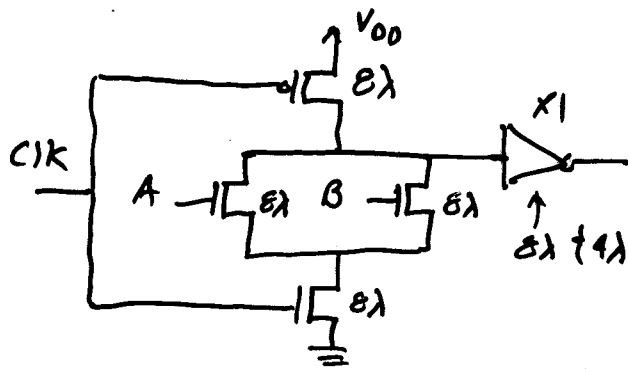
$$= \frac{20λ}{12λ} = \frac{5}{3} = 1.67$$



Dynamic NOR2


$$LE_{Dyn\ NOR} = \frac{Dynamic\ Input\ C}{INV\ input\ C} = \frac{8λ}{12λ} = \frac{2}{3}$$

$LE_{INV} = 1$

$\therefore LE_{Domino} = \sqrt{LE_{Dyn\ NOR} \cdot LE_{INV}} = 0.8$

Limitations of Domino Logic

1.) Charge sharing

 

AS IN goes from 0 to 1,

$$V_{out} = V_{DD} - \frac{C_{out}}{C_x + C_{out}} V_{DD}$$

$$0 C_x + C_{out} V_{DD} = V_p (C_x + C_{out})$$

If  $C_x = C_{out}$ , then  $V_{out} = \frac{V_{DD}}{2}$

Solutions:

- 1.) Increase  $C_{out}$  ???
  - 2.) Precharge node X to  $V_{DD}$
  - 3.) Use keepers
- 2.) Leakage

