

Memory Organization

(See Fig. 8.2)


MOS Decoders

Two-stage decoder =


An  $n$ -bit decoder require  $2^n$  logic gates each with  $n$ -inputs

For example if  $n=6 \rightarrow 64$  gates driving 64 inverters

First-stage (predecoder)

 

Second-stage -

 

Two level Decoder for a 6-bit address -  
(Fig. 8.6)

Example 8.1 - Decoder Sizing use LE Techniques

Size the decoder for  $n=6$  case using FO4 rules assuming that the normalized output loading is 1.

For each stage,  $C_{in} = \frac{LE \times BE \times C_{out}}{4}$



 


Figure 8.6 – Structure of two-level decoder for 6-bit address

 


Static RAM Cell Design


6 Transistor (6T) -

 

4 Transistor (4T)

 


Wordline and Double Bitline Architecture

 

$$C_{word} = [(2 \times \text{gate capacitance}) + \text{wire capacitance}] \times \text{no. of cells in a row}$$


$$C_{bit} = (\text{Source/drain capacitance} + \text{wire capacitance}) \times \text{no. of cells in a column}$$

Read Operation of the SRAM Cell

 

- 1.) Assume  $q=0$  &  $\bar{q}=1$
- 2.) Bit lines are precharged to  $V_{DD}$
- 3.) M1 is ON and M2 off
- 4.)  $b$  drops,  $\bar{b}$  stays at  $V_{DD}$
- 5.) Difference between  $b$  and  $\bar{b}$  is applied to the sense amplifier.

Wave forms

 

$$I_{cell} = C_{bit} \frac{\Delta V}{\Delta T}$$

Example 3.2 - Read Cycle Design Guidelines

Compute  $W_1$  and  $W_3$  given that the  $q$ -node can change 0.1V during a read operation. Assume  $C_{bit} = 2pF$  and that the sense amplifier requires a transition of 200mV on the bit line in 2ns. Use 0.13um technology

$$I_{cell} = C_{bit} \times \frac{\Delta V}{\Delta T} = 2pF \times \frac{0.2V}{2ns} = 200nA$$