 


Example 8.2 - Read Cycle Design Guidelines

Compute W_1 and W_3 given that the q -node can change 0.1V during a read operation. Assume $C_{bit} = 2pF$ and that the sense amp. requires a 200mV transition of the bitline in 2ns. Use 0.13 μm technology.

Solution

$$\textcircled{1} I_3 = I_1 \quad (I_1 = I_3)$$

$$\textcircled{2} I_{cell} = C_{bit} \frac{\Delta V}{\Delta T} = 200 \mu A$$

$$\frac{W_1}{L_1} \frac{M_n C_{ox}}{\left(1 + \frac{V_g}{E_{cn} L_1}\right)} \left[(V_{DD} - V_{T1}) V_g - \frac{V_g^2}{2} \right] = \frac{W_3 N_{sat} C_{ox} (V_{DD} - V_g - V_{T3})^2}{(V_{DD} - V_g - V_{T3}) + E_{cn} L_3}$$

$$\frac{W_1}{10^{-5} \text{ cm}} \frac{270 \text{ cm}^2/\text{V} \cdot 5}{\left(1 + \frac{0.1}{0.6}\right)} \left[(4.2 - 0.4)(0.1) - \frac{0.1^2}{2} \right] = \frac{W_3 (8 \times 10^6 \frac{\text{cm}}{\text{V}}) (1.2 - 0.1 - 0.4)^2}{(1.2 - 0.1 - 0.4) + 0.6}$$


$$\rightarrow \frac{W_1}{W_3} = 1.73$$

$$I_{cell} = I_3 = \frac{W_3 (8 \times 10^6) (1.6 \times 10^{-6}) (1.2 - 0.1 - 0.4)^2}{1.3} \rightarrow W_3 = 0.41 \mu m$$


$$\therefore W_1 \approx 1.7 W_3 = 0.7 \mu m$$

Normal practice gives $\frac{W_1}{W_3} \approx 1.5$


Write Operation for a 6T SRAM Cell

 

 - Operation to write a "1"
- 1.) $b = V_{DD}$ and $\bar{b} = 0$
 - 2.) When WL comes up, both M3 and M4 are on
 - 3.) Drain of M1 is pulled to V_{DD} and the drain of M2 is pulled to ground.
 - 4.) When the drains of M1 and M2 pass V_S , regeneration occurs and completes the switching.



How do we size M6 and M4?

 

Typically $\frac{W_4}{W_6} \approx 1.5$

$$W_6 = \frac{W_4}{1.5} = \frac{W_3}{1.5} = \frac{W_1}{(1.5)^2} = \frac{W_1}{2.25} \rightarrow W_6 = \frac{W_1}{2.25}$$

6T SRAM Layout (See transparency)

Ex. 8.3


Find C_{word} and C_{bit} for the 64K RAM shown previously. Assume that $\frac{W_3}{L_3} = \frac{W_4}{L_4} = \frac{0.5 \mu m}{0.1 \mu m}$, the contacts on the bit lines are shared between pairs of cells and have a cap. of 0.5 fF each. Also assume wire capacitance is 0.2 fF/ μm and the cell layout is 40 λ by 30 λ (where 30 λ = 1 μm). Use 0.13 μm technology.

Solution

$$C_{\text{word}} = \underbrace{256 \times (2C_g)}_{C_g \text{ of } M3 \text{ \& } M4} \times W + \underbrace{256 \times (0.2 \frac{\text{fF}}{\mu\text{m}})}_{\text{Bit line cap. / cell}} (30\lambda) \left(\frac{1}{20} \frac{\mu\text{m}}{\lambda}\right)$$

$$= 512 \text{ fF} + 77 \text{ fF} = 589 \text{ fF}$$
 
$$C_{\text{bit}} = \underbrace{\text{S/D - Bulk capacitance + Contact Cap + Wire Cap}}_{\text{of } M3 \text{ and } M4}$$



Normally we would use C_{eff} (no rev. bias)

In this problem, assume $C_{\text{eff}} = 0.5 \text{ fF}$ because of a reverse bias of V_{DD} .

$$C_{\text{bit}} = (0.5 \text{ fF}/\mu\text{m}) 256 (0.5 \mu\text{m}) + \frac{1}{2} 256 (0.5 \text{ fF}) + 256 \times 46\lambda (0.2 \text{ fF}/\mu\text{m}) \frac{1}{20}$$

$$= 64 \text{ fF} + 64 \text{ fF} + 102.4 \text{ fF} = 230 \text{ fF}$$

Contact capacitance?

