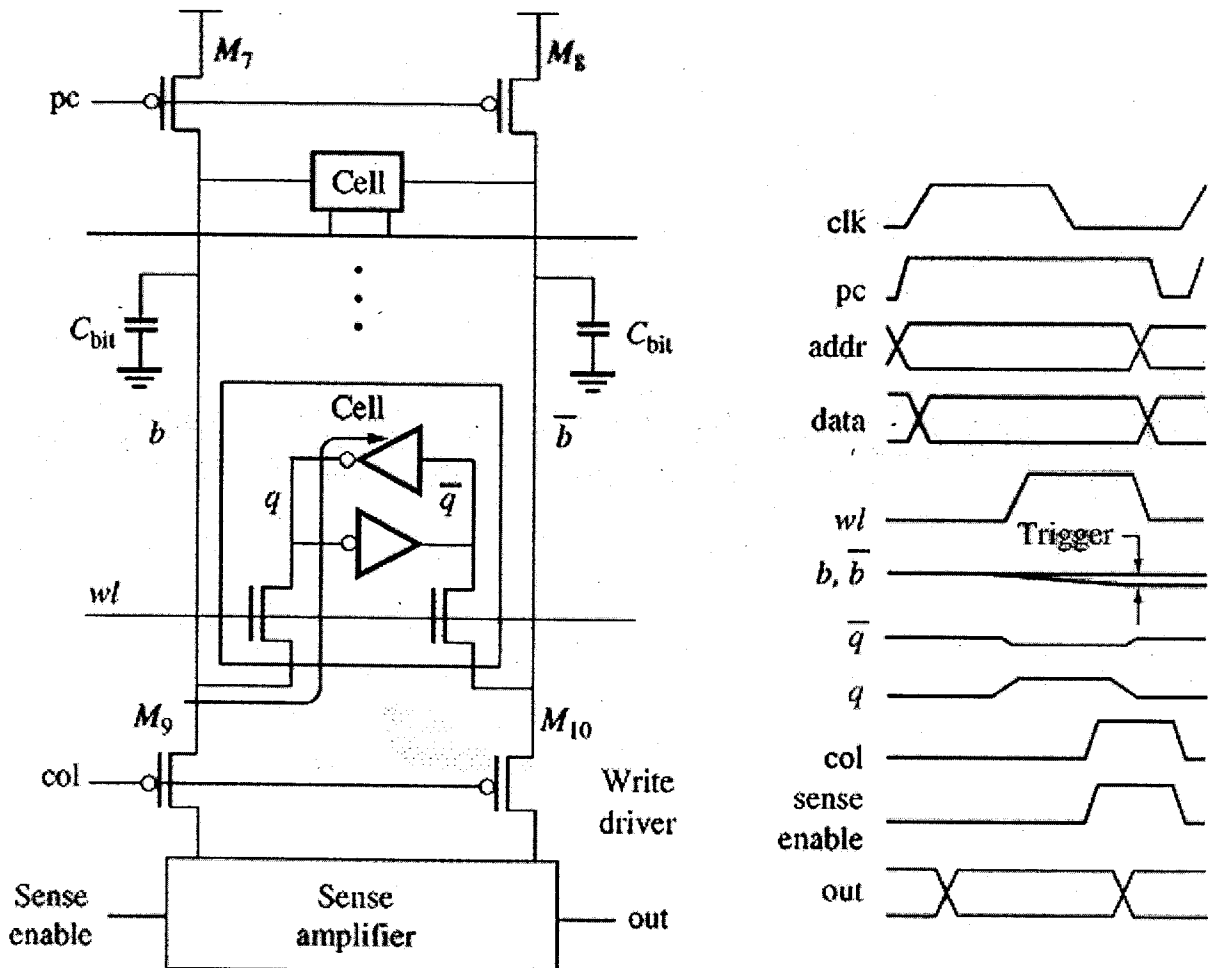


Read Circuitry


Figure 8.19 – Basic read circuit.

Operation

- 1.) Precharge circuits pull the column lines to V_{DD}
- 2.) The address, data and clock are applied
- 3.) The address signals translate into column enable and wordline activation signals.
- 4.) The bitline with the initial 0 begins to fall
- 5.) Sense enable signal reads the difference and amplifies it.

Sense Amplifiers


Figure 8.21 – Differential sense amplifier.

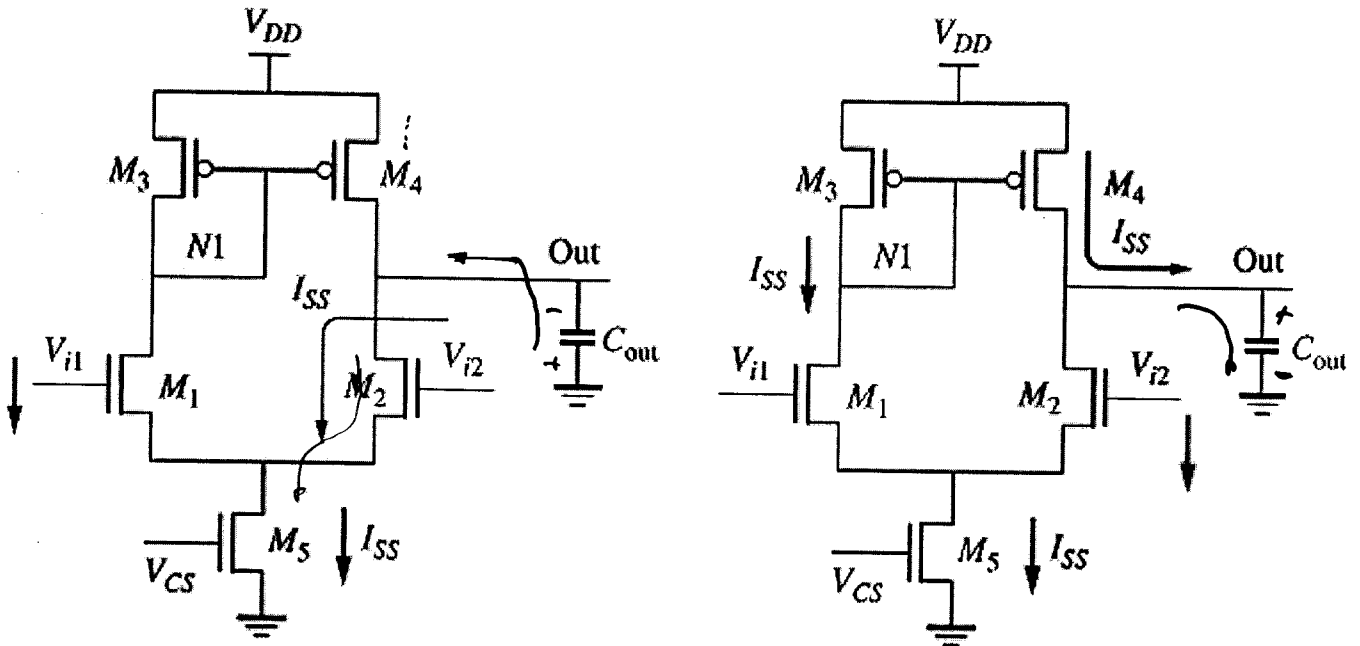

(a) Discharging output

 
(b) Charging output

$$\text{Max. } \frac{dV_{out}}{dt} = \frac{I_{SS}}{C_{out}}$$



Maximum input common-mode range:
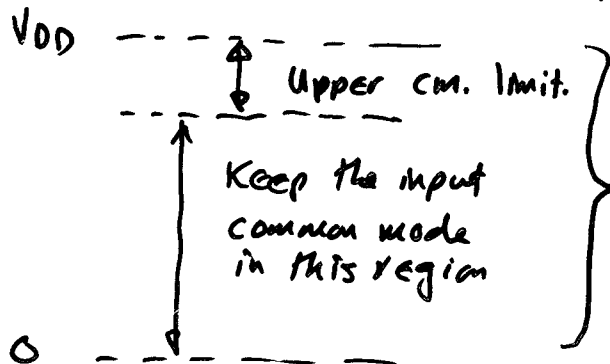
$$V_{icm}^+ = V_{DD} - V_{SGP} + V_{TN} \leftarrow \text{The max. common mode voltage the sense amp. can have.}$$




Makes Fig 8.13c much more attractive

$$V_{bit}(\text{max}) = V_{DD} - V_T$$


Assume $\Delta V = 0.1V$ if $A_v(\text{sense amp}) = 50 \rightarrow V_{out} = 5V !!!$

Figure 8.22 – Latch-based sense amplifier.

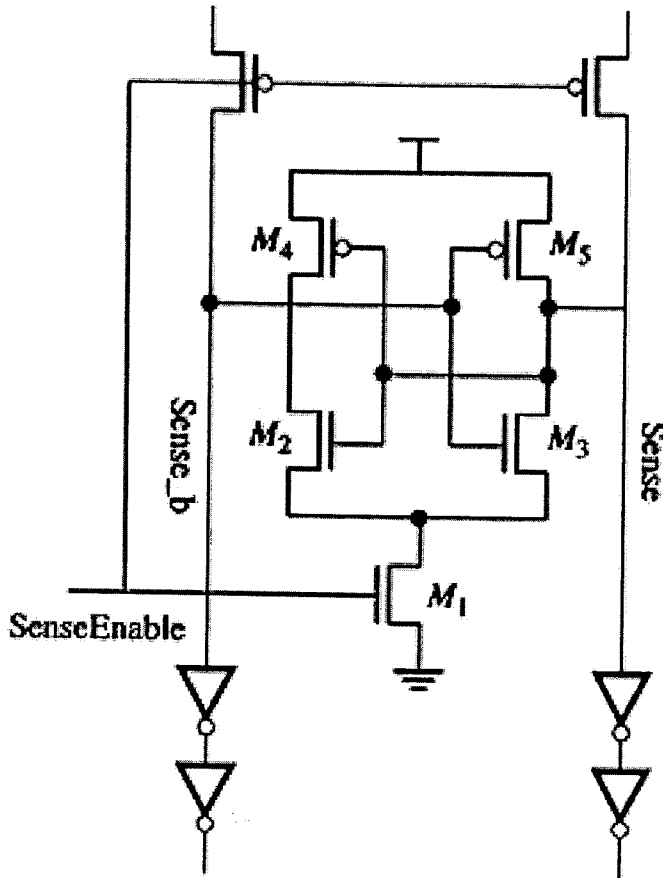


Positive fb is slow initially and fast later.

 Negative
An amplifier is fast initially and slow later.



$$N_{out}(latch) = k e^{t/\tau} V_{in}$$
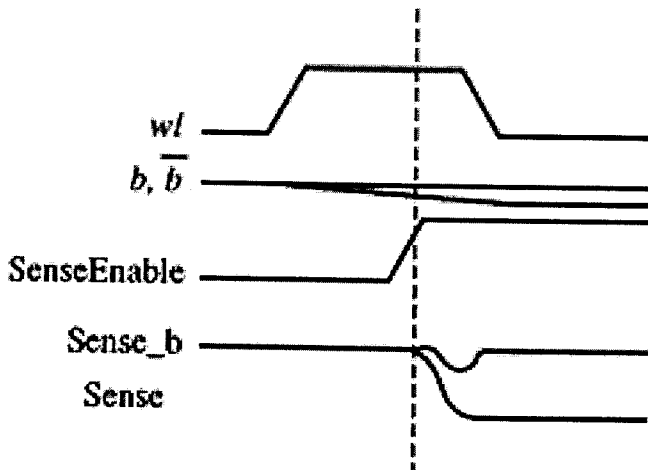
$$N_{out}(amp) = k (1 - e^{-t/\tau}) V_{in}$$




Fast sense amp:

Faster initially

Enable at t_1

Opt. results

ave 6 Amps
with $A = 3.16$

 

$$A_1 (1 - e^{-t/\tau_1})$$

Low power

Figure 8.23 – Replica circuit for sense amplifier clock enable


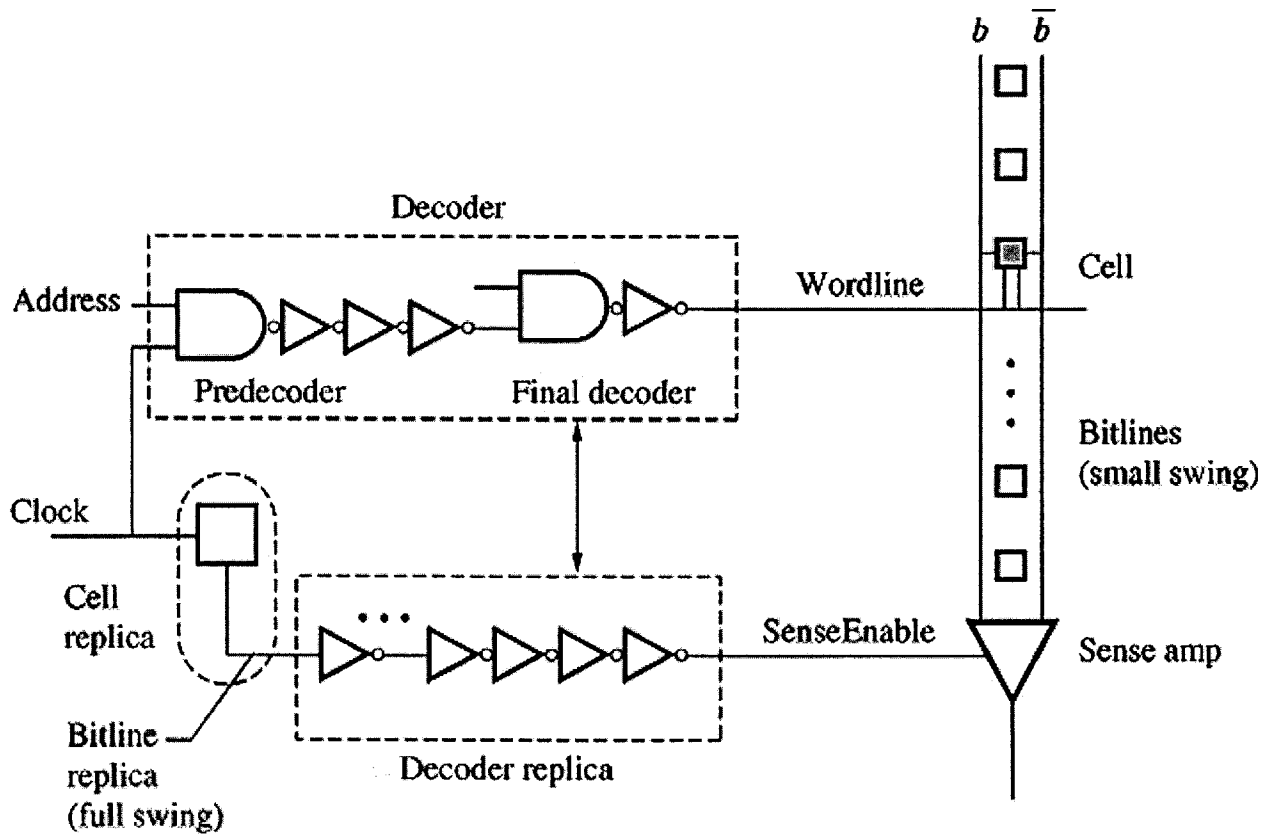


Figure 8.24 – Replica cell design.

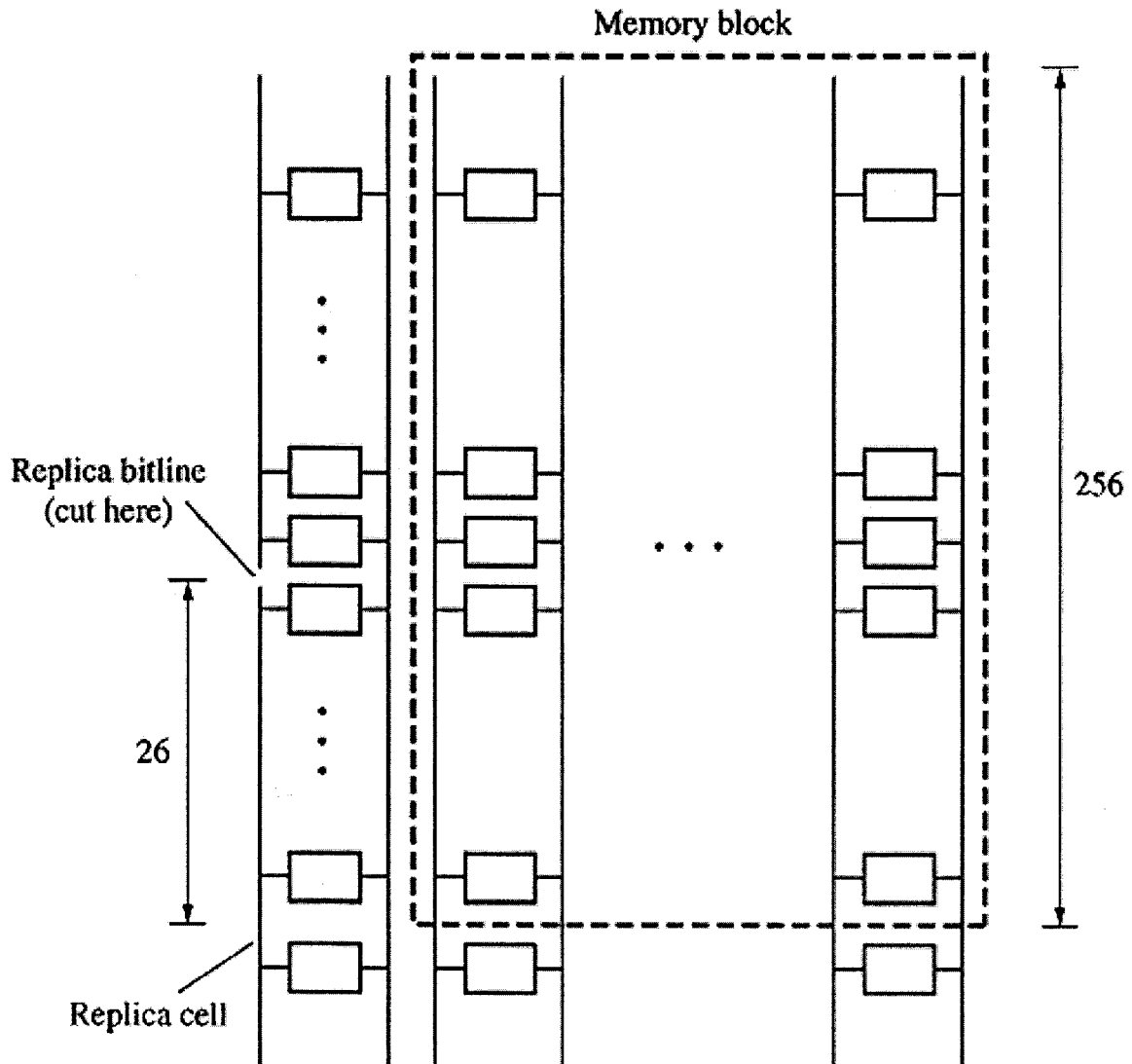

Function of the replica cells is to achieve proper timing between the sense/enable signal and the cell output

- Single cell \rightarrow Full swing is too slow (large C)
- Replica column line \rightarrow ≈ 26 cells give the full swing with the desired delay.

\uparrow

Exam 3

$\downarrow ?$

Chapt. 10 - Interconnects