

- Exam #3 - Wednesday (4/14/04)
- Problem Session - Tuesday 7pm (4/13/04)
- This exam may be taken on Friday at 8-9am or 11-12noon
- ONLY if you contact me today (4/12) by 4pm.
- Please be sure to do the on-line evaluation for this class.

Chapter 10

Elmore Delay -


$$\tau_i \approx \sum_k (C_k R_{ik})$$

i = node of interest


C_k = capacitance at node k

R_{ik} = sum of all the resistance in common with the path from node i to node k .

Example

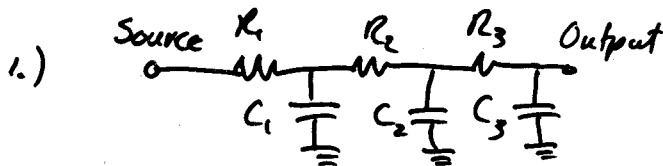
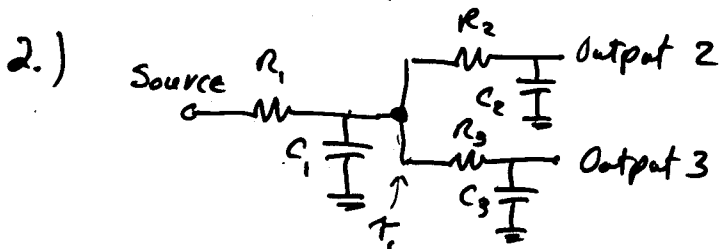
$$\tau \approx R_1 C_1 + C_2 (R_1 + R_2) + C_3 (R_1 + R_2 + R_3)$$




$$\tau_1 = R_1 C_1 + R_1 C_2 + R_1 C_3$$

$$\tau_2 = R_1 C_1 + R_1 C_3 + (R_1 + R_2) C_2$$

$$\tau_3 = R_1 C_1 + R_1 (R_2 + (R_1 + R_3) C_3)$$

RC Delay in Long Wires

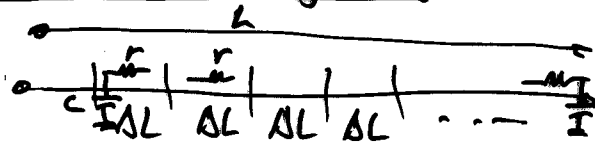

Let $\Delta L = \frac{L}{n} \rightarrow R_{wire} = n R_{int} = nr$
 $C_{wire} = n C_{int} = nc$

$$t_{delay} = (r\Delta L)(c\Delta L) + 2(r\Delta L)(c\Delta L) + \dots + n(r\Delta L)(c\Delta L)$$

$$= (\Delta L)^2 rc \frac{n(n+1)}{2} \approx n^2 \Delta L^2 \frac{rc}{2} = L^2 \frac{rc}{2}$$

$$\approx \frac{R_{wire} C_{wire}}{2} \text{ (Closer to } 0.38 R_{wire} C_{wire} \text{)}$$


Note delay increase with L^2 .

Lumped Models for Interconnect


L-model:



pi Model:

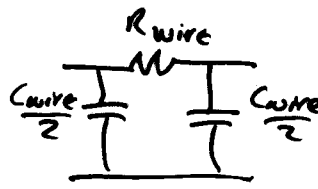


T-model:

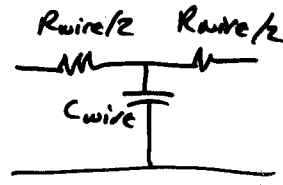

Best since the delay $\approx \frac{1}{2} R_{wire} C_{wire}$

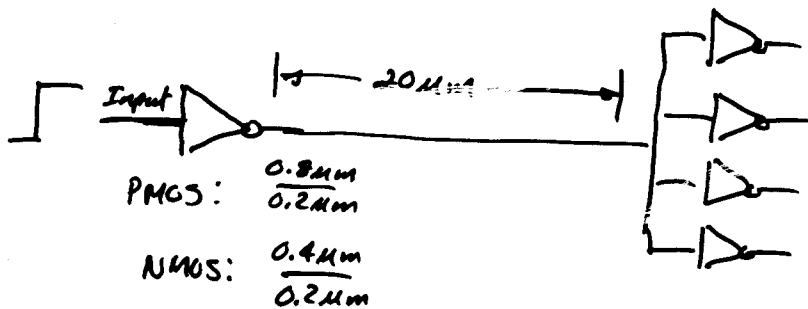
Example of Delay with Short Wires (Ex. 10.2)

Find the propagation delay thru the 1st inverter. Assume 0.18um Technology



$C_g = 2fF/\mu m$
 $C_{eff} = 1fF/\mu m$
 $C_{int} = 0.2fF/\mu m$

Model -

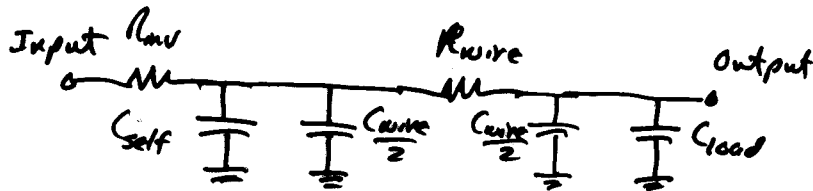

$$C_{self} = C_{eff}(W_p + W_n) = 1 \text{ fF}/\mu\text{m} (0.8 + 0.4) \mu\text{m} = 1.2 \text{ fF}$$

$$C_{wire} = 0.2 \text{ fF}/\mu\text{m} \times 20 \mu\text{m} = 4 \text{ fF}$$

$$C_{load} = 4 C_g (W_n + W_p) = 9.6 \text{ fF}$$

Wire width = 0.2 μm

$$R_{mv} = 12.5 \text{ k}\Omega \left(\frac{0.2}{0.4} \right) = 6.25 \text{ k}\Omega$$

$$R_{wire} = (54 \text{ m}\Omega/\square) \left(\frac{20 \mu\text{m}}{0.2 \mu\text{m}} \right) = 5.4 \text{ }\Omega$$

$$\begin{aligned} \tau_{delay} &\leq R_{mv} \left(C_{self} + \frac{C_{wire}}{2} \right) + (R_{mv} + R_{wire}) \left(C_{load} + \frac{C_{wire}}{2} \right) \\ &= 6.25 \text{ k}\Omega (1.2 \text{ fF} + 2 \text{ fF}) + (6.25 \text{ k}\Omega + 5.4 \Omega) (2 \text{ fF} + 9.6 \text{ fF}) \\ &= 20 \text{ ps} + 72.6 \text{ ps} = 92.6 \text{ ps} \end{aligned}$$

Repeat this example if the wire is 20 mm long. ($W = 0.5 \mu\text{m}$)

$$R_{wire} = R_{int} \left(\frac{L}{W} \right)$$

$$\text{Assume metal 5 (Al)} \rightarrow R_{int} = 27 \text{ m}\Omega/\square$$

$$\therefore R_{wire} = 27 \text{ m}\Omega/\square \left(\frac{20,000}{0.5} \right) = 1080 \Omega$$

Inverter is now $\times 100$

$$R_{mv} = \frac{6.25 \text{ k}\Omega}{100} = 62.5 \Omega$$

$$C_{self} = C_{eff}(3W) \times 100 = 1 \frac{\text{fF}}{\mu\text{m}} (3 \times 0.2 \mu\text{m}) \times 100 = 60 \text{ fF}$$

$$C_{wire} = C_{int} L = \left(0.1 \frac{\text{fF}}{\mu\text{m}} \right) (20,000 \mu\text{m}) = 2 \text{ pF}$$

↑
Metal 5 is further away from
the substrate.

$$\tau_{delay}(\text{long}) \approx \underbrace{(62.5 \Omega)}_{125} (1 \text{ pF}) + \underbrace{(62.5 + 1080)}_{125} (1 \text{ pF}) \approx 1.2 \text{ ns}$$

How do you reduce the delay of long wires?
Buffer insertion.

