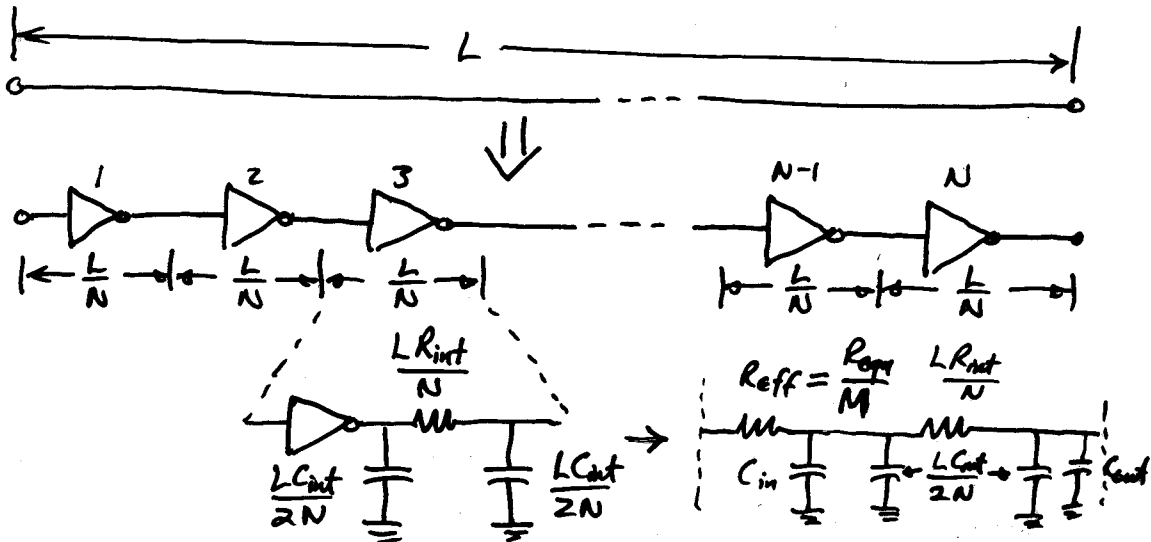


How do you reduce the delay of long wires?

Use the concept of buffer insertion.



$$C_{in} = C_{eff}(W_n + W_p) = C_{eff}W_n(1 + \frac{W_p}{W_n}) = C_J(1+B)$$

where $C_J = C_{eff}W_n$ and $B = \frac{W_p}{W_n}$

$$C_{out} = C_g(W_n + W_p) = C_gW_n(1+B) = C_G(1+B)$$

$R_{eff} = \frac{R_{eqn}}{M}$ where $M =$ optimal buffer size for the insertion problem.

Elmore delay for a segment,

$$\begin{aligned} t_{seg} &= \frac{R_{eqn}}{M} \left[C_J(1+B)M + \frac{C_{int}L}{2N} \right] + \left[\frac{R_{eqn}}{M} + \frac{R_{int}L}{N} \right] \left[\frac{C_{int}L}{2N} + C_G(1+B)M \right] \\ &= R_{eqn}(C_J + C_G)(1+B) + \left[\frac{R_{eqn}}{M} \frac{C_{int}L}{2N} + \frac{R_{eqn}}{M} \frac{C_{int}L}{2N} \right] + \frac{R_{int}L}{N} \left[\frac{C_{int}L}{2N} + C_G M(1+B) \right] \end{aligned}$$

Total delay -

$$\begin{aligned} t_{total} &= N \times t_{seg} = \underbrace{N(C_J + C_G)R_{eqn}(1+B)}_{\text{Interconnect only term}} + \underbrace{\left[C_G(1+B)R_{int}M + \frac{C_{int}R_{eqn}}{M} \right] L}_{\text{Buffer only}} \\ &\quad + \left(\frac{C_{int}R_{int}}{2N} \right) L \quad \text{Error in book} \end{aligned}$$

- 1.) Wire resistance x buffer cap
- 2.) Buffer driving the wire cap

To optimize the wire delay with buffer insertion, find N and M .

$$N = \sqrt{\frac{R_{int} C_{int} L^2}{2 R_{eqn} (C_j + C_g) (1+B)}} = \sqrt{\frac{A_{wire}}{FOI}} \quad \left\{ \begin{array}{l} M = \sqrt{\frac{R_{eqn} C_{int}}{C_g (1+B) R_{int}}} \end{array} \right.$$

where FOI is the delay of an inverter driving an identical inverter and all buffers are sized identically.

Ex. 10.4

Do Ex. 10.3 but use buffer insertion approach.

$$R_{int} = 54 \text{ m}\Omega/\mu\text{m}, \quad C_{int} = 0.1 \text{ fF}/\mu\text{m}, \quad L = 20,000 \mu\text{m}$$


$$R_{eqn} = 12.5 \text{ k}\Omega/13, \quad C_g = 2 \text{ fF}/\mu\text{m}, \quad C_{eff} = 1 \text{ fF}/\mu\text{m}$$

$$W_n = 0.2 \mu\text{m} \text{ and } B = 2 \quad (W_p = 0.4 \mu\text{m})$$

$$N = 6.9 \rightarrow N = 7 \quad \text{and } M = 139 \rightarrow 140$$


$$R_{eff} = \frac{12.5 \text{ k}\Omega}{140} = 90 \Omega \quad C_{self} = C_{eff} (2W + W) 140 = 84 \text{ fF}$$
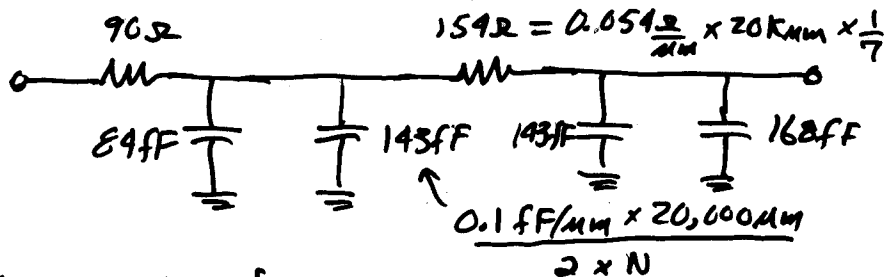
$$\text{Buffer cap.} = C_{in} = C_g (2W + W) 140 = 168 \text{ fF}$$




$$\text{Total delay} \approx 7 \times \left[90 (84 \text{ fF} + 143 \text{ fF}) + (90 + 154) (143 \text{ fF} + 168 \text{ fF}) \right]$$
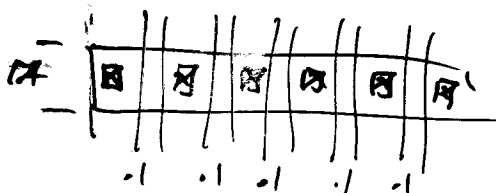
$$= 0.67 \text{ ns} \quad (\text{with no buffers, delay } 1.3 \text{ ns})$$



INTERCONNECT COUPLING CAPACITANCE

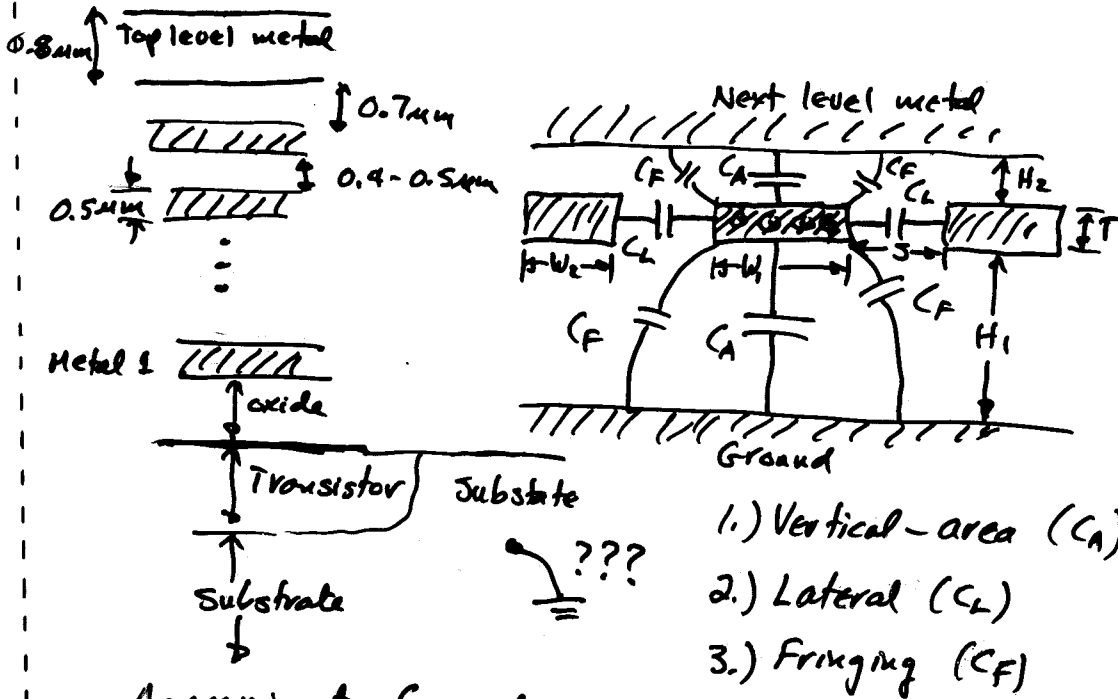

Approximate formulas -

$$C_A = \epsilon_{ox} \frac{W}{H} = 4\epsilon_0 \frac{W}{H} \approx 0.035 \frac{W}{H} \text{ fF}/\mu\text{m}$$

$$C_L = \epsilon_{ox} \frac{T}{S} = 0.035 \frac{T}{S} \text{ fF}/\mu\text{m}$$

$$C_F = \epsilon_{ox} \ln\left(1 + \frac{T}{H}\right) \text{ fF}/\mu\text{m}$$

For 0.18um Upper level metal: $T = 0.8\mu\text{m}$ & $S = 0.4\mu\text{m}$
 Lower level metals: $T = H = 0.5\mu\text{m}$
 $W = 0.4$

	Closely Spaced ($S = 0.4\mu\text{m}$)	Widely Spaced ($S = 4\mu\text{m}$)
Lower Metal $T = 0.5\mu\text{m}$ $H = 0.8\mu\text{m}$	$C_{int} = 2(C_A + C_L + C_F)$ $= 2(0.015) + 2(0.035) + 0$ $= 0.1 \text{ fF}/\mu\text{m}$	$C_{int} = 2(C_A + C_F + C_L)$ $\approx 2(0.015) + 2(0.025) + 0$ $\approx 0.1 \text{ fF}/\mu\text{m}$
Upper metal $T = 0.8\mu\text{m}$ $H = 0.5\mu\text{m}$	$C_{int} = 2C_A + 2C_L + 2C_F$ $= 2(0.03) + 2(0.07) + 0$ $= 0.2 \text{ fF}/\mu\text{m}$	$C_{int} = 2C_A + 2C_F + 2C_L$ $= 2(0.03) + 2(0.025) + 0$ $\approx 0.1 \text{ fF}/\mu\text{m}$