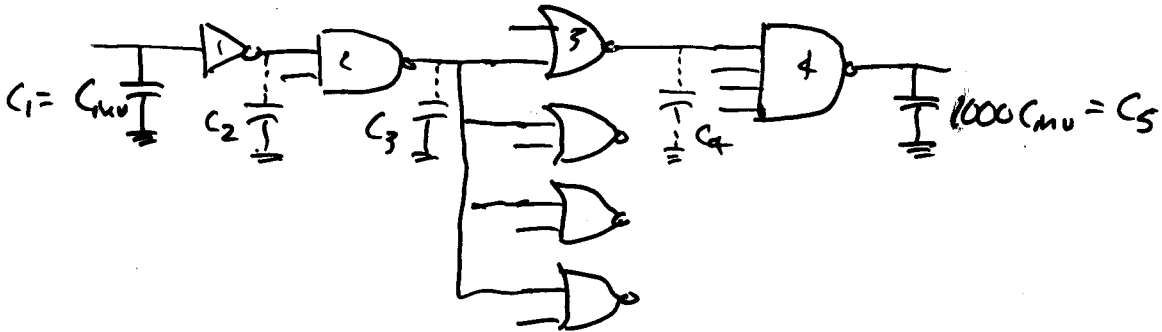


Problem Session 7pm

P6.12




$$C_j = \frac{LE_j C_{j+1} \times BE}{SE}$$

$$C_3 = \frac{LE_4 \times C_4 \times BE_4}{SE} = \frac{(\frac{5}{3})(173.21)(1)}{11.55} = 25 \quad \text{9?}$$

$$C_2 = \frac{LE_3 \times C_3 \times BE_3}{SE} = \frac{(\frac{4}{3})(25)(4)}{11.55} = 11.55$$

P6.9c

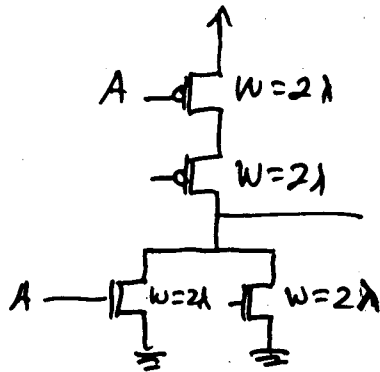

Pull up = λ       $LE_R \uparrow LE_F$   
 Pull down = 2λ

$$LE = \frac{(R_{eff} C_m)_{gate}}{(R_{eff} C_x)_{mv}}$$


$$LE_R = \frac{R_{eqn}(\frac{2}{W}) C_g W}{R_{eqn} C_g L_n}$$

$$LE_R = \frac{4 R_{eqn} (2 C_g W)}{R_{eqn} (3 C_g W)} = \frac{8}{3} \quad LE_F = \frac{R_{eqn} (2 C_g W)}{R_{eqn} (3 C_g W)} = \frac{2}{3}$$

Ex. 7.5

$$LE = \frac{\tau_{gate}}{\tau_{inv}}$$

$$\tau = R_{eff} C_{in}$$

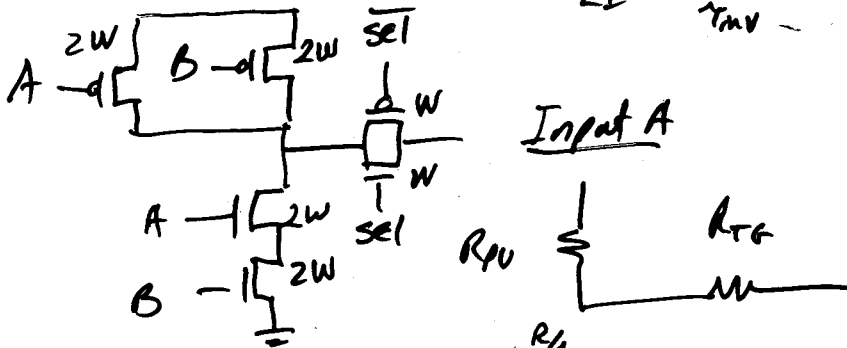


$$LE_A = \frac{(4W)(R+R)}{3WR} = \frac{4 \cdot 2R}{3R} = \frac{8}{3}$$

Input at sel

$$LE_{sel} = \frac{W(2R)}{3WR} = \frac{2}{3}$$

Ex. 7.4

$$2C_{eff} + C_g$$

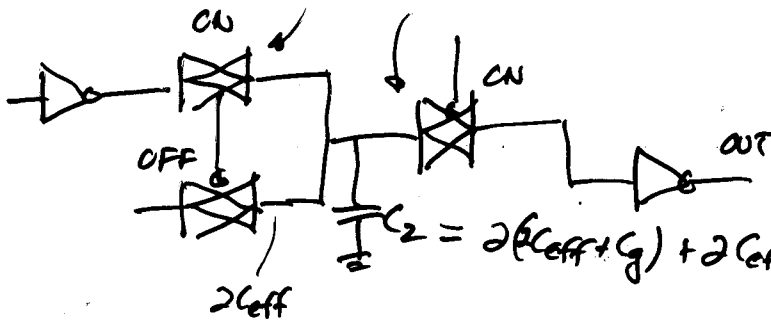

$$C_2 = 2(C_{eff} + C_g) + 2C_{eff} = [3(2C_{eff}) + 2C_g]W$$