

Homework Assignment No. 2

Due on Monday, January 31, 2005

1.) Problem P2.4 of the text.

[Answers - a.) Cutoff, b.) Cutoff, c.) Linear, and d.) Saturated]


2.) Problem P2.5 of the text.

[Answers - a.) $V_x = 0.733V$ and b.) $V_x = 0.6V$

3.) Problem P2.7 of the text.

[Answers - $C_G = 0.64fF$ and $C_j = 0.19fF$]

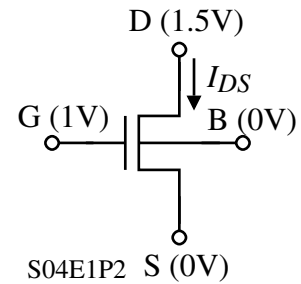4.) Solve for the dc value of the drain current, I_{DS} , for the NMOS transistor shown assuming $0.18\mu m$ CMOS technology. The W and L for this transistor are given in Problem 5.



5.) Given the layout for the NMOS transistor of Problem 2, find the value of C_{gs} , C_{gd} , C_{gb} , C_{db} , and C_{sb} assuming that the junction depth of the source-drain diffusions is $x_j = 50\text{ nm}$, $m = 0.5$ and the lateral diffusion is 10 nm .

