

Homework Assignment No. 4

Due on Wednesday, February 9, 2005


1.) Problem P4.2 of the text. (This problem should refer to Fig. P4.1 not Fig. P4.2)

[Partial Answers: a.) $V_{OH} = V_{DD}$ and $V_{OL} = 0.055\text{V}$ b.) $V_{OH} = 0.733\text{V}$, and $V_{OL} \approx 0.69\text{V}$, c.) $V_{OH} = 1.11\text{V}$ and $V_{OL} = 0.69\text{V}$]

2.) Problem P4.3 of the text. Use SPICE to confirm the results.

[Partial Answers: $V_{IH} = 0.65\text{V}$ and $V_{IL} = 0.55\text{V}$]

3.) Problem P4.9 of the text.

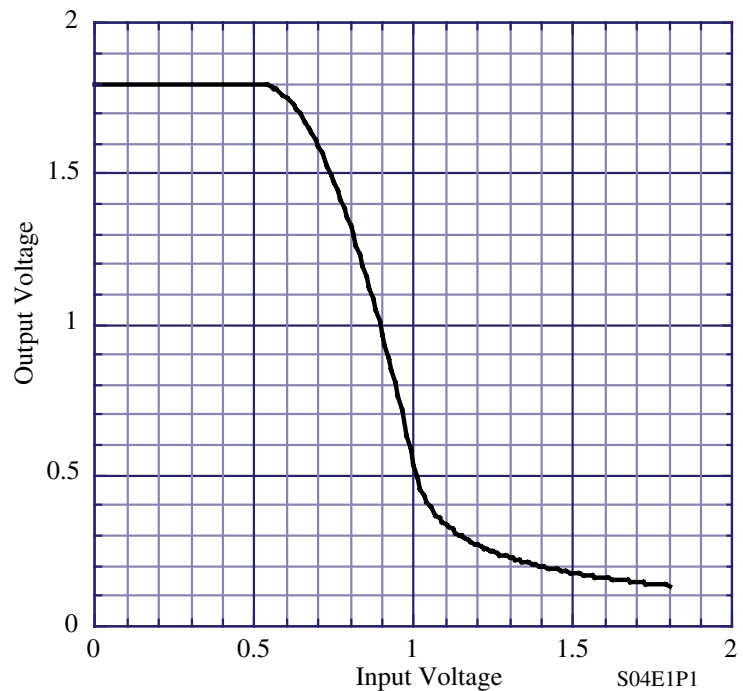[Answers: $W_n = 0.2\mu\text{m}$, $0.1\mu\text{m}$ and $0.6\mu\text{m}$]4.) From the voltage transfer function curve shown, numerically identify, V_{OH} , V_{OL} , V_{IL} , V_{IH} , and V_S . From these values, find the value of NM_H and NM_L .5.) Given the layout for the NMOS transistor of Problem 2, find the value of C_{gs} , C_{gd} , C_{gb} , C_{db} , and C_{sb} assuming that the junction depth of the source-drain diffusions is $x_j = 50\text{ nm}$, $m = 0.5$ and the lateral diffusion is 10 nm .