

Homework No. 5 – Solutions**Problem 1 – P4.3**

For this problem, you are required to use the formulae:

$$V_{IL} = \frac{2V_{out} - V_{DD} - |V_{TP}| + (k_N / k_P)(V_{TN})}{1 + (k_N / k_P)} \quad V_{IH} = \frac{2V_{out} + V_{TN} + (k_P / k_N)(V_{DD} - |V_{TP}|)}{1 + (k_P / k_N)}$$

We already know that $V_{OH}=1.2$ V and $V_{OL}=0$ V. For V_S use:

$$W_N = 4\lambda, \quad W_P = 16\lambda:$$

$$X = \sqrt{\frac{\frac{W_N}{E_{CN}L_N}}{\frac{W_P}{E_{CP}L_P}}} = \sqrt{\frac{W_N E_{CP}}{W_P E_{CN}}} = \sqrt{\frac{(4)(24)}{(16)(6)}} = 1$$

$$V_S = \frac{0.8 + (0.4)1}{1+1} = 0.6V$$

Next V_{IL} and V_{IH} are estimated as follows:

$$V_{IL} = \frac{2V_{out} - V_{DD} - |V_{TP}| + (k_N / k_P)(V_{TN})}{1 + (k_N / k_P)} = \frac{2V_{out} - 1.2 - |-0.4| + (1)(0.4)}{1 + (1)} = \frac{2V_{out} - 1.2}{2} = 0.55V$$

$$V_{IH} = \frac{2V_{out} + V_{TN} + (k_P / k_N)(V_{DD} - |V_{TP}|)}{1 + (k_P / k_N)} = \frac{2V_{out} + 0.4 + (1)(1.2 - 0.4)}{1 + (1)} = \frac{2V_{out} + 1.2}{2} = 0.65V$$

Therefore

$$NM_L = 0.55 - 0 = 0.55V$$

$$NM_H = 1.2 - 0.65V = 0.55V$$

When we cut the size of the PMOS device in half, the VTC shifts to the left. So V_{IL} , V_S , and V_{IH} will all shift to the left. The recalculation of the switching threshold produces $V_S=0.566V$.

We can compute V_{IL} to be roughly 0.533V and V_{IH} to be roughly 0.667V.

Therefore

$$NM_L = 0.533 - 0 = 0.533V$$

$$NM_H = 1.2 - 0.667V = 0.533V$$

Problem 2 - P4.9

Design the circuit for $V_{OL} = 0.1V$, $L = 0.1\mu m$ in $0.1\mu m$ technology.


* Resistive Load inverter:

$E_{CL} = 0.6V$
 $V_{OH} = 1.2V$
 $V_{OL} = 0.1V$
 $C_{ox} = 1.6 \mu F/cm^2$
 $\mu_n = 270 \frac{cm^2}{V \cdot s}$
 $V_{th} = 8 \times 10^6$

$$\frac{V_{DD} - V_{OL}}{R_L} = \frac{W_N}{L_N} \frac{\mu_n C_{ox}}{\left(1 + \frac{V_{OL}}{E_{CL}}\right)} \left[\frac{2(V_{OH} - V_T)V_{OL} - V_{OL}^2}{2} \right]$$

$$\frac{1.2 - 0.1}{10k} = \frac{W_N}{0.1} \frac{(270)(1.6 \times 10^{-6})}{\left(1 + \frac{0.1}{0.6}\right)} \left[\frac{2(1.2 - 0.4)0.1 - 0.1^2}{2} \right]$$

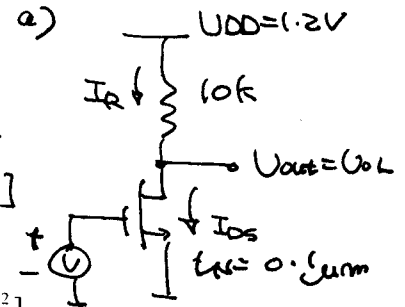$\therefore W_N = 0.2 \mu m$ $W = 0.39 \mu m$ ✓




* Saturated Enhancement Load inverter (ignoring body-effect):

$I_D(\text{lin}) = I_D(\text{sat})$

$$\frac{W_L}{L_L} \frac{\mu_n C_{ox}}{\left(1 + \frac{V_{out}}{E_{CN} L_L}\right)} \left[(V_{in} - V_{TL})V_{out} - \frac{V_{out}^2}{2} \right] = \frac{W_L V_{sat} C_{ox} (V_{DD} - V_{out} - V_{TL})^2}{(V_{DD} - V_{out} - V_{TL}) + E_{CN} L_L}$$

$$\frac{0.1}{0.1} \frac{(270)(1.6 \times 10^{-6})}{\left(1 + \frac{0.1}{0.6}\right)} \left[\frac{2(1.2 - 0.4)0.1 - 0.1^2}{2} \right] = \frac{0.1(10^{-4})(8)(1.6)(1.2 - 0.1 - 0.4)^2}{(1.2 - 0.1 - 0.4) + 0.6}$$

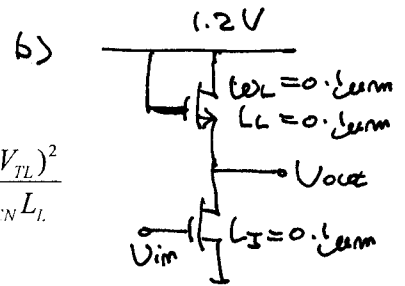$\therefore W_N = 0.1 \mu m$ $W = 0.174 \mu m$ ✓




* Linear Enhancement Load inverter (ignoring body-effect): Load is saturated

$$\frac{W_L}{L_L} \frac{\mu_n C_{ox}}{\left(1 + \frac{V_{out}}{E_{CN} L_L}\right)} \left[(V_{in} - V_{TL})V_{out} - \frac{V_{out}^2}{2} \right] = \frac{W_L V_{sat} C_{ox} (V_{DD} - V_{out} - V_{TL})^2}{(V_{DD} - V_{out} - V_{TL}) + E_{CN} L_L}$$

$$\frac{0.1}{0.1} \frac{(270)(1.6 \times 10^{-6})}{\left(1 + \frac{0.1}{0.6}\right)} \left[\frac{2(1.2 - 0.4)0.1 - 0.1^2}{2} \right] = \frac{0.1(10^{-4})(8)(1.6)(1.6 - 0.1 - 0.4)^2}{(1.6 - 0.1 - 0.4) + 0.6}$$

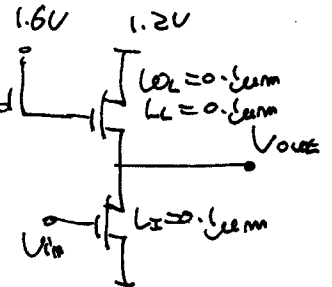$\therefore W_N = 0.6 \mu m$ $W = 0.328 \mu m$ ✓



The linear enhancement load inverter requires the largest pull-down device since it has the strongest pull up device. The resistive load inverter is next and the saturated enhancement load requires the smallest pull-down device.

Problem 3 - P4.10

We will illustrate the process and estimate the solutions for this problem.

We already know that $V_{OH} = 1.2V$ and $V_{OL} = 0V$. For V_S use:

$$W_N = 0.4\mu\text{m}, \quad W_P = 0.8\mu\text{m}:$$

$$X = \sqrt{\frac{W_N}{E_{CN}L_N}} = \sqrt{\frac{W_N E_{CP}}{W_P E_{CN}}} = \sqrt{\frac{(0.4)(24)}{(0.8)(6)}} = 1.41$$

$$V_S = \frac{0.8 + (0.4)1.41}{1 + 1.41} = 0.566$$

Next V_{IL} and V_{IH} are estimated as follows:

$$V_{IL} = \frac{2V_{out} - V_{DD} - |V_{TP}| + (k_N / k_P)(V_{TN})}{1 + (k_N / k_P)}$$

$$V_{IL} = \frac{2V_{out} - 1.2 - |-0.4| + (2)(0.4)}{1 + (2)} = \frac{2V_{out} - 0.6}{3}$$

We can compute V_{IL} to be roughly 0.533V.

$$V_{IH} = \frac{2V_{out} + V_{TN} + (k_P / k_N)(V_{DD} - |V_{TP}|)}{1 + (k_P / k_N)}$$

$$V_{IH} = \frac{2V_{out} + 0.4 + (2)(1.2 - 0.4)}{1 + (2)} = \frac{2V_{out} + 2}{3}$$

We can compute V_{IH} to be roughly 0.667V.

When we double the size of the PMOS device, the VTC shifts to the right. So V_{IL} , V_S , and V_{IH} will all shift to the right. The recalculation of the switching threshold produces $V_S=0.6\text{V}$.

We can compute V_{IL} to be roughly 0.55V and V_{IH} to be roughly 0.65V.


Problem 2 – P5.1

For each problem, restate each Boolean equation into a form such that it can be translated into the p and n-complex of a CMOS gate.

$$a. \text{ Out} = ABC + BD = \overline{\overline{ABC + BD}} = \overline{(\overline{A + \overline{B} + \overline{C}})(\overline{B + D})}$$

$$b. \text{ Out} = AB + \overline{A}C + BC = \overline{\overline{AB + \overline{A}C + BC}} = \overline{(\overline{A + B})(A + \overline{C})(\overline{B + C})}$$

$$c. \text{ Out} = \overline{A + B + CD} + A = \overline{A} \overline{B} (\overline{C} + \overline{D}) + A = \overline{\overline{\overline{A + B + CD} + A}} = \overline{(A + B + CD) \overline{A}}$$

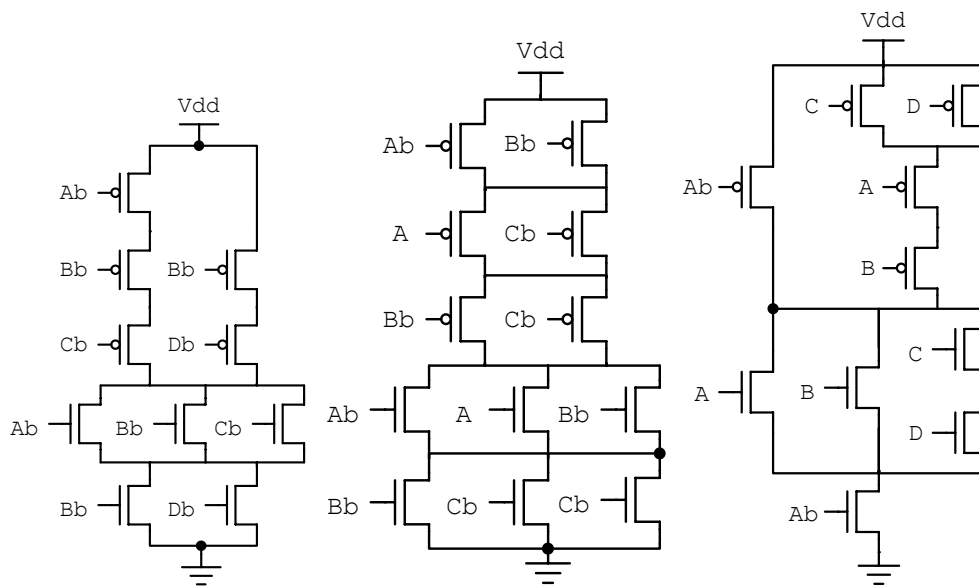Problem 3 – P5.8

The solution is shown below. Notice that there is no relevance with the lengths and widths of the transistors when it comes to V_{OH} , although they do matter when calculating V_{OL} .

$$V_{out} = V_{GG} - V_T$$

$$V_{GG} = V_{out} + V_{T0} + \gamma \left(\sqrt{V_{out} + 2|\phi_F|} - \sqrt{2|\phi_F|} \right)$$

$$= 1.8 + 0.5 + 0.3 \left(\sqrt{1.8 + 0.88} - \sqrt{0.88} \right) = 2.51V$$

Problem 4 – P5.9

For t_{PLH} , we need to size the pull-up PMOS appropriately.

$$t_{PLH} = 0.7RC = 0.7R_{eqp} \frac{L}{W} C_{LOAD}$$

$$W_p = 0.7R_{SQ} \frac{L}{t_{PLH}} C_{LOAD} = 0.7(30k\Omega) \frac{(2\lambda)}{(50 \times 10^{-12})} (100 \times 10^{-15}) = 84\lambda$$

For V_{OL} :

$$I_p(sat) = \frac{W_p v_{sat} C_{OX} (V_{GS} - V_T)^2}{V_{GS} - V_T + E_{CP} L} = \frac{(4.2 \times 10^{-4})(8 \times 10^6)(1.6 \times 10^{-6})(1.2 - 0.4)^2}{1.2 - 0.4 + (24)(0.1)} = 1.08 \text{mA}$$

$$I_p(sat) = \frac{W_N \mu_N C_{OX} (V_{OL} - V_{TN} - \frac{V_{OL}}{2}) V_{OL}}{L_N (1 + \frac{V_{OL}}{E_{CN} L})} = \frac{W_N (270)(1.6 \times 10^{-6})(1.2 - 0.4 - \frac{0.1}{2}) 0.1}{L_N (1 + \frac{0.1}{0.6})}$$

$$\frac{W_N}{L_N} = 38.5 \quad W_N = 77\lambda \quad W_3 = 3 \times 77\lambda = 232\lambda \quad (3 \text{ stack}) \quad W_2 = 155\lambda \quad (2 \text{ stack})$$


Problem 4

An NMOS transistor with a $10\text{k}\Omega$ resistor as a load is used to implement a simple inverter as shown. The alpha-power model of Section 2.6 is used to fit the measured data for the NMOS transistor to produce the following two equations:

$$i_{DS} = (W/L)K_L(v_{GS} - V_{TN})v_{DS} \quad v_{DS} \leq V_{DS(\text{sat})}$$

$$i_{DS} = (W/L)K_S(v_{GS} - V_{TN})^{1.5} \quad v_{DS} \geq V_{DS(\text{sat})}$$

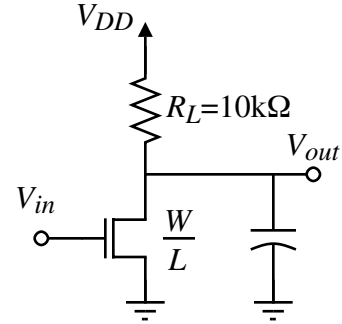where $K_L = 100\mu\text{A}/\text{V}^2$ and $K_S = 100\mu\text{A}/\text{V}^{1.5}$ and $V_{TN} = 0.6\text{V}$.



- Derive the expression for $V_{DS(\text{sat})}$ assuming the model above.
- Design V_{DD} and W/L of the resistively loaded inverter above to achieve $V_{OH} = 3.3\text{V}$ and $V_{OL} = 0.3\text{V}$.
- For the inverter of part b.) derive an expression for V_{IL} using the given alpha-power model. Using the previous values, evaluate V_{IL} .

Solution

- Equate the two equations for the linear and saturation regions to get,

$$\frac{W}{L}K_L(V_{GS}-V_{TN})V_{DS(\text{sat})} = \frac{W}{L}K_S(v_{GS} - V_{TN})^{1.5} \rightarrow \boxed{V_{DS(\text{sat})} = \frac{K_S}{K_L} \sqrt{v_{GS} - V_{TN}}}$$

- Since $V_{OH} = V_{DD}$, let $V_{DD} = \underline{3.3\text{V}}$. Solve for V_{OL} by assuming the MOSFET is in the linear region.

$$\frac{V_{DD} - V_{OL}}{R_L} = \frac{3.3 - 0.3}{10\text{k}\Omega} = 300\mu\text{A} = \frac{W}{L}K_L(V_{DD} - V_{TN})V_{OL} = \frac{W}{L} 100\mu\text{A}/\text{V}^2(3.3 - 0.6)0.3$$

$$\frac{W}{L} = \frac{300\mu\text{A}}{81\mu\text{A}} = \underline{3.7}$$

- For V_{IL} assume the MOSFET is saturated. Therefore,

$$\frac{V_{DD} - V_{out}}{R_L} = \frac{W}{L} K_S(V_{in} - V_{TN})^{1.5}$$

Differentiating with respect to V_{in} gives,

$$-\frac{1}{R_L} \frac{dV_{out}}{dV_{in}} = 1.5 \frac{W}{L} K_S(V_{in} - V_{TN})^{0.5} \rightarrow \frac{1}{R_L} = 1.5 (3.7) K_S(V_{IL} - V_{TN})^{0.5}$$

$$V_{IL} = V_{TN} + \frac{1}{[(1.5 \cdot (W/L))K_S R_L]^2} = 0.6 + \frac{1}{(1.5 \cdot 3.7 \cdot 100 \cdot 0.01)^2}$$

$$= 0.6 + 0.0325 = \underline{0.6325\text{V}}$$


Problem 5

For the pseudo-NMOS load inverter shown using 0.18 μm CMOS technology, determine V_{OH} and estimate V_{OL} using the velocity saturated model with effective mobility (high vertical field). Be sure to clearly state any assumptions used in estimating V_{OL} .

Solution

For this inverter, we know that $V_{OH} \approx V_{DD} = \underline{1.8\text{V}}$

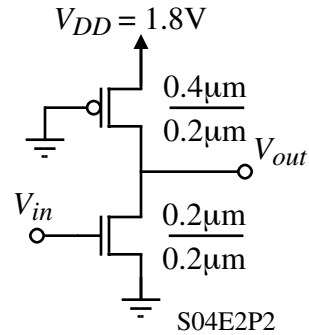For V_{OL} , we need to assume the state of the transistors. To help in this calculate $V_{DS(\text{sat})}$ for the NMOS and PMOS transistors.



$$\text{PMOS: } V_{SD(\text{sat})} = \frac{(V_{SG} - |V_{TP}|)E_{CP}L_P}{(V_{SG} - |V_{TP}|) + E_{CP}L_P} = \frac{(1.8-0.5)4.8}{(1.8-0.5)+4.8} = 1.023\text{V}$$

$$\text{NMOS: } V_{DS(\text{sat})} = \frac{(V_{GS} - V_{TN})E_{CN}L_N}{(V_{GS} - V_{TN}) + E_{CN}L_N} = \frac{(1.8-0.5)1.2}{(1.8-0.5)+1.2} = 0.624\text{V}$$

So if $V_{OL} < 0.624\text{V}$, the PMOS is saturated and the NMOS is linear. Assuming this to be the case, we get:

$$\frac{W_n}{L_n} \frac{\mu_e C_{ox}}{1 + \frac{V_{DS}}{E_{CN}L_N}} \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS} = W_p \nu_{sat} C_{ox} \frac{(V_{SG} - |V_{TP}|)^2}{(V_{SG} - |V_{TP}|) + E_{CP}L_P}$$

Assuming V_{DS} which is V_{OL} is small, we can simplify the above to,

$$\frac{W_n}{L_n} \mu_e (V_{GS} - V_{TN}) V_{OL} \approx W_p \nu_{sat} \frac{(V_{SG} - |V_{TP}|)^2}{(V_{SG} - |V_{TP}|) + E_{CP}L_P}$$

Substituting the values gives,

$$270(\text{cm}^2/\text{v}\cdot\text{s})(1.8-0.5)V_{OL} = 0.4 \times 10^{-4}(\text{cm})(8 \times 10^6)(\text{cm}/\text{s}) \frac{(1.8-0.5)^2}{1.8-0.5+4.8}$$

$$351V_{OL} = 88.656 \quad \rightarrow \quad V_{OL} = \underline{0.253\text{V}}$$

This problem can also be solved exactly for V_{OL} as follows.

$$\frac{270(1.8-0.5-0.5V_{OL})V_{OL}}{1+V_{OL}/1.2} = (0.4 \times 10^{-4})(8 \times 10^6) \frac{(1.8-0.5)^2}{1.8-0.5+4.8} = 88.656$$

$$270(1.3-0.5V_{OL})V_{OL} = 88.656(1+0.833V_{OL})$$

$$351V_{OL} - 135V_{OL}^2 = 88.656 + 73.88V_{OL}$$

$$\therefore 135V_{OL}^2 + (73.88-351)V_{OL} + 88.656 = 0 \quad \rightarrow \quad V_{OL}^2 - 2.053V_{OL} + 0.6567 = 0$$

$$V_{OL} = 1.0265 \pm 0.5\sqrt{2.053^2 - 4 \cdot 0.6567} = 1.0265 \pm 0.5\sqrt{1.588} = 1.0265 \pm 0.6300$$

$$\therefore V_{OL} = \underline{0.3964\text{V}}$$

Either answer will be accepted provided the work is correct and the assumptions consistent.