

Homework No. 6 – SolutionsProblem 1 – P5.9

For t_{PLH} , we need to size the pull-up PMOS appropriately.

$$t_{PLH} = 0.7RC = 0.7R_{eq} \frac{L}{W} C_{LOAD}$$


$$W_p = 0.7R_{SQ} \frac{L}{t_{PLH}} C_{LOAD} = 0.7(30k\Omega) \frac{(2\lambda)}{(50 \times 10^{-12})} (100 \times 10^{-15}) = 84\lambda$$

For V_{OL} :

$$I_p(sat) = \frac{W_p \nu_{sat} C_{OX} (V_{GS} - V_T)^2}{V_{GS} - V_T + E_{CP}L} = \frac{(4.2 \times 10^{-4})(8 \times 10^6)(1.6 \times 10^{-6})(1.2 - 0.4)^2}{1.2 - 0.4 + (24)(0.1)} = 1.08\text{mA}$$

$$I_p(sat) = \frac{W_N \mu_N C_{OX} (V_{OL} - V_{TN} - \frac{V_{OL}}{2}) V_{OL}}{L_N (1 + \frac{V_{OL}}{E_{CN}L})} = \frac{W_N (270)(1.6 \times 10^{-6})(1.2 - 0.4 - \frac{0.1}{2}) 0.1}{L_N (1 + \frac{0.1}{0.6})} \quad \text{Pr}$$

$$\frac{W_N}{L_N} = 38.5 \quad W_N = 77\lambda \quad W_3 = 3 \times 77\lambda = 232\lambda \quad (3 \text{ stack}) \quad W_2 = 155\lambda \quad (2 \text{ stack})$$

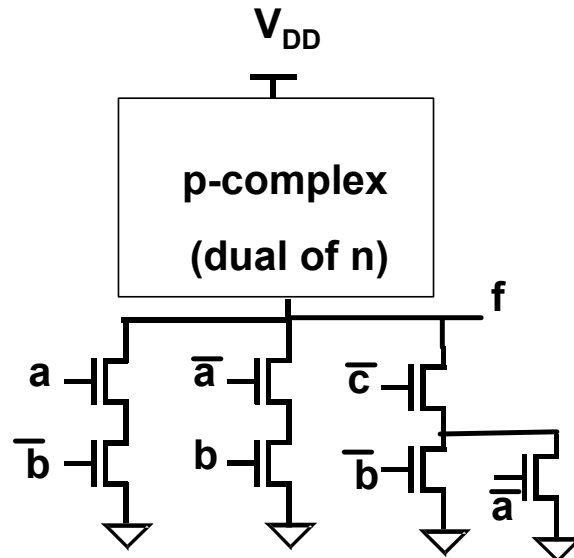Problem 2 – P5.10

Problem 5.10 Continued

$$t_{PLH} = 0.7RC = R_{EQP} \frac{L}{W_P} C_{LOAD}$$

$$W_P = 0.7R_{EQP} \frac{L}{t_{PLH}} C_{LOAD} = 0.7(30 \times 10^3) \frac{(2\lambda)}{(50 \times 10^{-12})} (75 \times 10^{-15}) = 63\lambda$$

$$t_{PHL} = RC = 0.7R_{EQN} \frac{L}{W_N} C_{LOAD}$$

$$W_N = 0.7R_{EQN} \frac{L}{t_{PHL}} C_{LOAD} = 0.7(12.5 \times 10^3) \frac{(2\lambda)}{(50 \times 10^{-12})} (75 \times 10^{-15}) = 26.6\lambda \approx 27\lambda$$

Because the number of transistors in series is more than one, we must multiply the widths by the appropriate number. Here, all the NMOS transistors will have a width of 54λ . The PMOS transistors will have widths of 126λ and 190λ , respectively.

Problem 3 – P5.11

We estimate the dc power and dynamic switching power for this problem.

a.) The circuit's dc power can be computed by computing the dc current when the output is low. This is given by $I_{DS} = 550 \mu\text{A}/\mu\text{m} \times 0.1 \mu\text{m} = 55 \mu\text{A}$. Then $P_{DC} = 66 \mu\text{W}$ when the output is low.

b.) Its dynamic power can be calculated by simply using the equation $P_{dyn} = \alpha C V_{DD}^2 f$. Therefore, $P_{dyn} = (50 \text{fF})(V_{DD} - V_{TN})(V_{DD})(100 \text{MHz}) = 4.4 \mu\text{W}$.

Problem 4 – P5.12

The pseudo-NMOS inverter has static current when the output is low. We can estimate it as:


$$I_P(sat) = \frac{W_P V_{sat} C_{OX} (V_{GS} - V_T)^2}{V_{GS} - V_T + E_{CP} L} = \frac{(0.1 \times 10^{-4})(8 \times 10^6)(1.6 \times 10^{-6})(1.2 - 0.4)^2}{1.2 - 0.4 + (24)(0.1)} = 25.6 \mu\text{A}$$

Then the average static power is $P_{stat} = (25.6 \mu\text{A})(1.2)/2 = 15.4 \mu\text{W}$.


The dynamic power is $P_{dyn} = C V_{DD} V_{swing} f_{avg} = (50 \text{fF})(1.2)(1.1) f_{avg}$ assuming that V_{OL} is 0.1V .

For the CMOS inverter, the static power is almost zero: $P_{stat} = I_{sub} V_{DD}$. It is far less than the pseudo-NMOS case. The dynamic power $P_{dyn} = C V_{DD} V_{swing} f_{avg} = (50 \text{fF})(1.2)^2 f_{avg}$ is slightly larger than the pseudo-NMOS case.

Problem 5.12 - Continued

 


Pseudo-NMOS

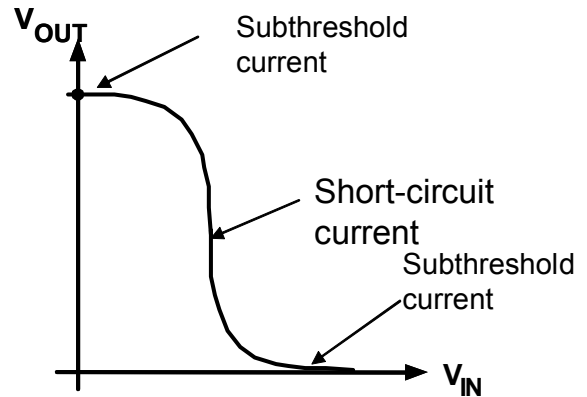

CMOS Inverter

 Problem 5 – P5.16

The circuit is shown below. The delay should incorporate both Q and Qb settling in 400ps. All NMOS and PMOS devices are the same size in both NAND gates.



$$\begin{aligned}
 t_p &= t_{PHL} + t_{PLH} = 0.7R_{UP}C_{LOAD} + 0.7R_{DOWN}C_{LOAD} = 0.7C_{LOAD} \left(R_{eqp} \frac{L_P}{W_P} + R_{eqn} \frac{2L_N}{W_N} \right) \\
 &= \frac{0.7C_{LOAD} (R_{eqp}L + 2R_{eqn}L)}{W} \\
 W &= \frac{0.7C_{LOAD} (R_{eqp}L + 2R_{eqn}L)}{t_p} = \frac{0.7(100 \times 10^{-15}) ((30 \times 10^3)(0.1) + 2(12.5 \times 10^3)(0.1))}{400 \times 10^{-12}} \\
 &\approx 1 \mu\text{m}
 \end{aligned}$$