

**Homework 1 – Solutions**Problem 1

This question is as easy as it looks, no tricks here.

- a. The delay from ‘a’ to ‘b’ is simply the delay of an inverter times the number of inverters which would be 10 ns.
- b.
  - i. The period in this case is simply twice the delay around the loop,  $T=20$  ns.
  - ii. The frequency is  $1/T = 50$  MHz.

Problem 2

The delay of an RC circuit with a step input applied is:

$$V(t) = 1.2(1 - e^{-t/RC})$$

In our case, we are solving for  $t$ :

- a.) For  $V(t)=0.6V$ :

$$t = 12.5(10^3) \times (100)10^{-15} \ln\left(\frac{1.2}{0.6}\right) = 12.5 \times 10^{-10} \ln(2) = 866 \text{ ps}$$

- b.) 1.2V:

$$t = \infty$$

This circuit will never read 1.2V.

- c.) The delay from 10% to 90%  $V_{DD}$ :

$$0.1 = (1 - e^{-t/RC})$$

$$\therefore t_{10\%} = 132 \text{ ps}$$

$$0.9 = (1 - e^{-t/RC})$$

$$\therefore t_{90\%} = 2.88 \text{ ns}$$

$$t = t_{90\%} - t_{10\%} = 2.88 - 0.132 = 2.75 \text{ ns}$$

Problem 3

The delay for 0 and 0 uses the exponential rise/fall equation:

a.) For  $R_{DOWN}$ :

$$V(t) = 1.2 e^{-t/RC} \quad \therefore t_{DOWN} = 8.66ms$$

b.) For  $R_{UP}$ :

$$V(t) = 1.2(1 - e^{-t/RC}) \quad \therefore t_{UP} = 20.8ms$$

c.) The ratio of delays is:

$$t_{RATIO} = \frac{t_{UP}}{t_{DOWN}} = \frac{20.8}{8.7} = 2.4$$

or 0.42 (depending on which way you did the ratio.)

Problem 4

a) The solution for the NMOS case is based on Example 2.4:

The equation for  $V_{T0}$  is:  $V_{T0} = V_{FB} - 2\phi_F - \frac{Q_B}{C_{OX}}$

Calculate each individual component.

$$\phi_{Fp} = \frac{kT}{q} \ln \frac{n_i}{N_A} = -0.026 \ln \frac{3 \times 10^{17}}{1.4 \times 10^{10}} = -0.44 \text{ V}$$

$$\phi_{GC} = \phi_{Fp} - \phi_{G(\text{gate})} = -0.44 - 0.55 = -0.99 \text{ V}$$

$$\epsilon_{OX} = 4\epsilon_0 = 3.5 \times 10^{-13} \text{ F/cm} \quad C_{OX} = 1.6 \times 10^{-6} \text{ F/cm}^2$$

$$Q_{B0} = 3 \times 10^{-7} \text{ C/cm}^2 \quad \frac{Q_{B0}}{C_{OX}} = \frac{3 \times 10^{-7}}{1.6 \times 10^{-6}} = 0.188 \text{ V}$$

$$\frac{Q_{OX}}{C_{OX}} = \frac{6 \times 10^{11} \times 1.6 \times 10^{-19}}{1.6 \times 10^{-6}} = 0.06 \text{ V}$$

$$V_{T0} = -0.99 - (-0.88) - (-0.188) - 0.060 = +0.018 \text{ V}$$

Problem 4 - Continued

For the PMOS device:

$$\phi_{Fn} = \frac{kT}{q} \ln \frac{N_D}{n_i} = 0.026 \ln \frac{3 \times 10^{17}}{1.4 \times 10^{10}} = 0.44 \text{ V}$$

$$\phi_{GC} = \phi_{Fn} - \phi_{G(\text{gate})} = 0.44 + 0.55 = +0.99 \text{ V}$$

$$Q_{B0} = 3 \times 10^{-7} \text{ C/cm}^2 \quad \frac{Q_{B0}}{C_{OX}} = \frac{3 \times 10^{-7}}{1.6 \times 10^{-6}} = 0.188 \text{ V}$$

$$\frac{Q_{OX}}{C_{OX}} = \frac{6 \times 10^{11} \times 1.6 \times 10^{-19}}{1.6 \times 10^{-6}} = 0.06 \text{ V}$$

$$V_{T0} = 0.99 - (0.88) - (0.188) - 0.060 = -0.138 \text{ V}$$

b) The magnitude of  $V_{T0}$  would be higher. Since the device is PMOS this means that  $V_{T0}$  is lowered. Since the only thing that's been changed is the doping of the gate, only  $\phi_G$  changes.

The new  $V_{T0}$  then becomes:

$$V_{T0} = -0.11 - 0.88 - 0.188 - 0.6 = -1.24 \text{ V}$$

c) Since  $V_{T0}$  will be adjusted with implanted charge ( $Q_I$ ):

$$\frac{Q_I}{C_{OX}} = 0.4 - 0.018$$

$$\frac{Q_I}{C_{OX}} = 0.382 \text{ V}$$

$$Q_I = (1.6 \times 10^{-6})(0.382 \text{ V})$$

To calculate the threshold implant level  $N_I$ :

$$qN_I = |Q_I|$$

$$N_I = \frac{|Q_I|}{q}$$

For the NMOS device from part(a):

$$N_I = -\frac{Q_I}{q} = -\frac{0.6 \times 10^{-6}}{1.6 \times 10^{-19}} = 3.82 \times 10^{12} \text{ ions/cm}^2 \text{ (p-type)}$$

Problem 4 - Continued

For the PMOS device from part(a):

$$N_I = -\frac{Q_I}{q} = -\frac{(1.6 \times 10^{-6})(0.4 - 0.138)}{1.6 \times 10^{-19}} = 2.62 \times 10^{12} \text{ ions/cm}^2 \text{ (n-type)}$$


For the PMOS device from part(b):

$$N_I = -\frac{Q_I}{q} = -\frac{(1.6 \times 10^{-6})(1.24 - 0.4)}{1.6 \times 10^{-19}} = 8.4 \times 10^{12} \text{ ions/cm}^2 \text{ (p-type)}$$

- d) The advantage of having the gate doping be  $n^+$  for NMOS and  $p^+$  for PMOS could be seen from analysis above. Doping the gates in such a way leads to devices with lower threshold voltages, but enables the implant adjustment with the same kind of impurities that used in the bulk (p-type for NMOS and n-type for PMOS). If we were to use the same kind of doping in gate as in the body (i.e.  $n^+$  for PMOS and  $p^+$  for NMOS) that would lead to higher un-implanted threshold voltages. Adjusting them to the required lower threshold voltage would necessitate implantation of the impurities of the opposite type near the oxide-Si interface. This is not desirable. Also, the doping of the poly gate can be carried out at the same time as the source and drain and therefore does not require an extra step.
 
### Problem 5

Solve for the dc value of the drain current,  $I_{DS}$ , for the NMOS transistor shown assuming 0.18 $\mu\text{m}$  CMOS technology. The  $W$  and  $L$  for this transistor are given in Problem 3.



### Solution

Check for saturation.

$$V_{DS}(\text{sat}) = \frac{(V_{GS} - V_T)E_c L}{(V_{GS} - V_T) + E_c L} = \frac{(1-0.5)(1.2)}{(1-0.5) + 1.2} = 0.353\text{V}$$

$$V_{DS} = 1.5\text{V} \Rightarrow \text{NMOS in saturation}$$

$$\therefore I_{DS} = W v_{sat} C_{ox} \frac{(V_{GS} - V_T)^2}{(V_{GS} - V_T) + E_c L}$$

$$W = 0.6 \times 10^{-4} \text{ cm}$$

$$v_{sat} = \frac{\mu_e E_c}{2} = \frac{270 \text{ (cm}^2/\text{V}\cdot\text{s)} \cdot 6 \times 10^4 \text{ (V/cm)}}{2} = 8.1 \times 10^6 \text{ cm/sec}$$

$$C_{ox} = \frac{\epsilon_r(\epsilon_o)}{t_{ox}} = \frac{4.8.85 \times 10^{-14} \text{ (F/cm)}}{35 \times 10^{-8} \text{ cm}} = 1.01 \times 10^{-6} \text{ F/cm}^2$$

$$\begin{aligned} \therefore I_{DS} &= (0.6 \times 10^{-4} \text{ cm}) (8.1 \times 10^6 \text{ cm/sec}) (1.01 \times 10^{-6} \text{ F/cm}^2) \left( \frac{0.5^2}{0.5 + 1.2} \right) (\text{V}) \\ &= \underline{72.18 \mu\text{A}} \end{aligned}$$