

Homework No. 11 – Solutions**Problem 1 – P7.15**

$$V_{OUT} = V_{OL}$$

$$V_X = V_{DD} - V_T$$

First, let's find the required change in voltage:

$$\Delta V_{OUT} = V_{DD} - V_{OL}$$

$$\Delta V_X = (V_{DD} + V_T) - (V_{DD} - V_T) = 2V_T$$

Now, let's set up the clock feedthrough equation and solve for C_b :


$$\Delta V_X = \frac{C_b \Delta V_{OUT}}{C_b + C_X}$$

$$C_b = \frac{\Delta V_X C_X}{\Delta V_{OUT} - \Delta V_X} = \frac{2V_T C_X}{V_{DD} - V_{OL} - 2V_T}$$

 Problem 2 – P8.4

To compute the device sizes, start with the access transistor and the pull-down transistor:

We can compute the needed size of M_3 to deliver 300uA:



$$I_{cell} = \frac{W_L V_{sat} C_{ox} (V_{DD} - V_{OL} - V_{TL})^2}{(V_{DD} - V_{OL} - V_{TL}) + E_{CN} L_L} = \frac{W_L (8)(1.6)(1.8 - 0.5 - 0.5)^2}{(1.8 - 0.5 - 0.5) + 1.2} = 300 \mu A$$

$$W_L \approx 0.75 \mu m$$

Now determine the minimum W_D for the pull-down transistor:


$$\therefore \frac{W_D}{L} \frac{\mu_N C_{ox}}{\left(1 + \frac{V_{OL}}{E_{CN} L}\right)} \left[(V_{DD} - V_T) V_{OL} - \frac{V_{OL}^2}{2} \right] = \frac{W_L V_{sat} C_{ox} (V_{DD} - V_{OL} - V_{TL})^2}{(V_{DD} - V_{OL} - V_{TL}) + E_{CN} L}$$

$$\frac{W_D}{L} \frac{(270)(1.6 \times 10^{-6})}{\left(1 + \frac{0.5}{1.2}\right)} \left[(1.8 - 0.5) 0.5 - \frac{0.5^2}{2} \right] = I_{cell}$$

$$\frac{W_D}{L} \approx 2 \quad W_D = 0.4 \mu m \quad (\text{min})$$

P8.4 - Continued

 For the write operation, we must pull the internal node low against the PMOS pullup device. Try forcing the output to 0.5V which is below the expected V_S .



$$I_N = \frac{W_D}{L} \frac{\mu_N C_{ox}}{\left(1 + \frac{V_{OL}}{E_{CN} L}\right)} \left[(V_{DD} - V_T) V_{OL} - \frac{V_{OL}^2}{2} \right] = (3.75) \frac{(270)(1.6 \times 10^{-6})}{\left(1 + \frac{0.5}{1.2}\right)} \left[(1.8 - 0.5)0.5 - \frac{0.5^2}{2} \right] = 600 \mu A$$

$$I_P = \frac{W_P V_{sat} C_{ox} (V_{DD} - |V_{TP}|)^2}{(V_{DD} - |V_{TL}|) + E_{CP} L} = \frac{W_L (8)(1.6)(1.8 - 0.5)^2}{(1.8 - 0.5) + 4.8} = 600 \mu A$$

$$W_p \approx 1.7 \mu m \quad (\text{max})$$

Set $W_p = 0.75 \mu m$.

Compute V_S to ensure that the output will be below this value:


$$X = \sqrt{\frac{\frac{W_N}{E_{CN} L_N}}{\frac{W_P}{E_{CP} L_P}}} = \sqrt{\frac{W_N E_{CP}}{W_P E_{CN}}} = \sqrt{\frac{(24)}{(6)}} = 2$$

$$V_S = \frac{1.3 + (0.5)2}{1 + 2} = 0.767V$$

Yes. This is still above the target V_{OL} so it should work just fine.

 Problem 3 – P8.7

The following is a resistive load SRAM cell:



The circuit is static in nature. Assume that q is low and qbar is high. During a read, M3 and M1 behave the same as a 6T cell and

act to discharge b. Meanwhile, M4 turns on and hold the high value at qbar. To write a 1 into q, the bbar line is pulled low and M4 pulls qbar low while M3 pulls q high. Effectively, M3 and M4 acts as pull-ups for this type of SRAM cell.

Problem 4 – P8.8

(a)

$$I_{SS} = C \frac{dV}{dt} = 50 \text{ fF} \frac{0.9V}{500 \text{ ps}} = 90 \mu A$$

(b) Assume long channel transistors:

$$I_{DS} = \frac{W}{L} \frac{\mu_N C_{ox}}{2} (V_{GS} - V_T)^2$$

$$45 \mu A = \frac{W}{L} \frac{(270)(1.6 \mu F / \mu m^2) C_{ox}}{2} (0.1)^2$$

$$W / L = 21$$

(c) Use 8.13(c) as the column pullup circuitry. The initial voltage is $V_{DD} - V_T$.

(d) The voltage at the sources of the input transistors are both at $V_{DD} - V_T - V_T - 0.1 = 0.7V$.

The maximum allowable gate voltage of M5 is $0.7 + V_T = 1.2V$. Choose 1.0V.

$$I_{DS} = \frac{W}{L} \frac{\mu_N C_{ox}}{2} (V_{GS} - V_T)^2$$

$$90 \mu A = \frac{W}{L} \frac{(270)(1.6 \mu F / \mu m^2) C_{ox}}{2} (1.0 - 0.5)^2$$

$$W / L = 1.7$$

(e) Assume loads are in saturation and have $V_{GS} - V_T = 0.5V$.


$$I_{DS} = \frac{W}{L} \frac{\mu_N C_{ox}}{2} (V_{GS} - V_T)^2$$

$$45 \mu A = \frac{W}{L} \frac{(270)(1.6 \mu F / \mu m^2) C_{ox}}{2} (0.5)^2$$

$$W / L = 0.8$$

 Problem 5

For the logic circuit shown below, assume that the transmission gates are all $4\lambda:2\lambda$ and that the inverters driving the transmission gates have PMOS transistors that are $8\lambda:2\lambda$, and NMOS transistors that are $4\lambda:2\lambda$, where $\lambda = 0.1\mu\text{m}$. The output inverter is to drive a 50 fF load. The output inverter is 4 times larger than the input inverters.



(a.) Write the logic expression for the output function in terms of A , B , sel , and $selB$.


(b.) Draw an equivalent RC circuit model for the path from A to C assuming that the sel signal is high. Write down the individual contributions for each resistance and capacitance and place the total values at the appropriate nodes.

(c.) Find the Elmore delay from A to C .

Solution

$$(a.) \text{OUT} = \overline{sel \cdot A} + \overline{sel \cdot B} = (\overline{sel} + A) \cdot (sel \cdot B) = A \cdot sel + B \cdot selB$$

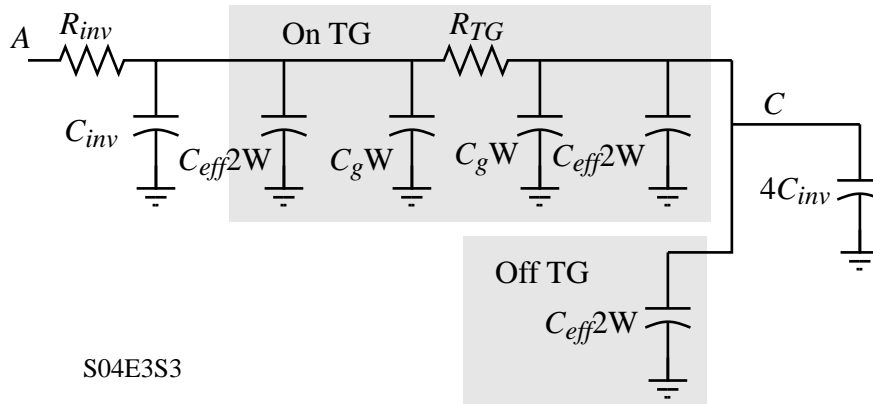(b.) The equivalent RC circuit model is shown below.



The quantities in this model are:

$$R_{inv} = 12.5\text{k}\Omega \left(\frac{2\lambda}{4\lambda} \right) = 6.25\text{k}\Omega, \quad C_{inv} = C_{eff}(W_n + W_p) = 1\text{fF}/\mu\text{m}(0.4\mu\text{m} + 0.8\mu\text{m}) = 1.2\text{fF},$$

$$C_{eff}(2W) = 1\text{fF}/\mu\text{m}(0.8\mu\text{m}) = 0.8\text{fF}, \quad C_gW = 2\text{fF}/\mu\text{m}(0.4\mu\text{m}) = 0.8\text{fF}$$

$$R_{TG} = 12.5\text{k}\Omega \left(\frac{2\lambda}{4\lambda} \right) = 6.25\text{k}\Omega, \quad \text{and} \quad 4C_{inv} = 4C_gW = 4(2\text{fF}/\mu\text{m})(1.2\mu\text{m}) = 9.6\text{fF}$$

(c.) The Elmore delay from A to C is given as

$$\begin{aligned} t_{AC} &= 6.25\text{k}\Omega(1.2\text{fF} + 0.8\text{fF} + 0.8\text{fF}) + (6.25\text{k}\Omega + 6.25\text{k}\Omega)(0.8\text{fF} + 0.8\text{fF} + 0.8\text{fF} + 9.6\text{fF}) \\ &= 6.25\text{k}\Omega(2.8\text{fF}) + 6.25\text{k}\Omega(12\text{fF}) = 17.5\text{ps} + 150\text{ps} = \underline{167.5\text{ps}} \end{aligned}$$