

# DIGITAL INTEGRATED CIRCUITS

## INTRODUCTION

### ① Course

Objective - Design of digital ICs in DSM technologies.

Goals -


- Develop the models & intuition to do digital IC design in DSM technology
- Examine actual circuits designed in industry and learn about tradeoffs
- Be able to work with future advances in technology

$$f_T \propto \frac{1}{(\text{Channel length})^2}$$

- Provide the basis and foundation for more courses on the topic of logic design.


### ② Design

Systems level -

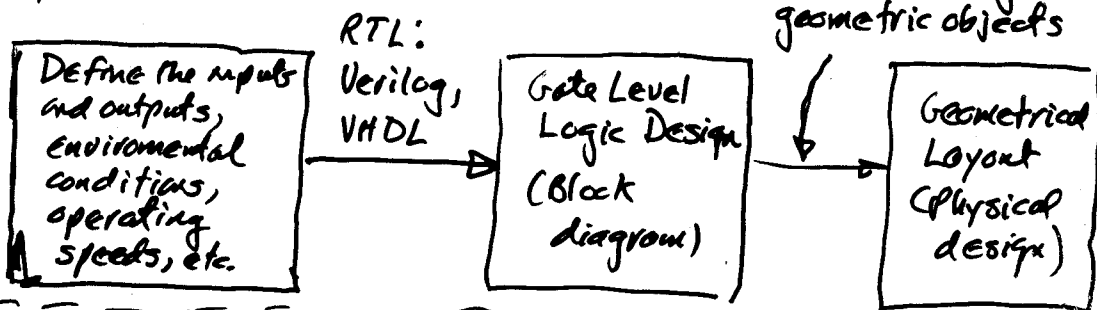


Circuits Level -

ECE 4420

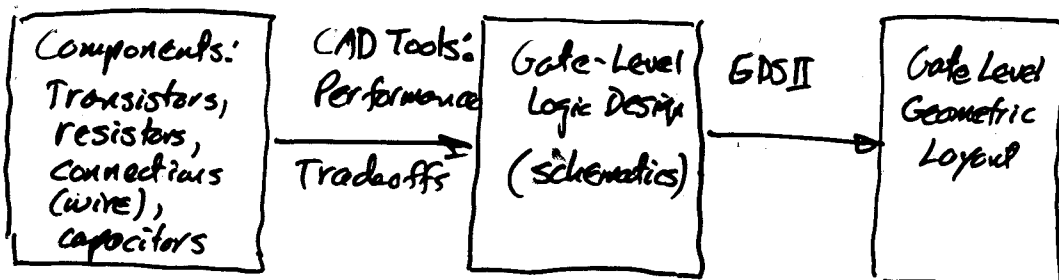

Design Flow (Digital Logic)

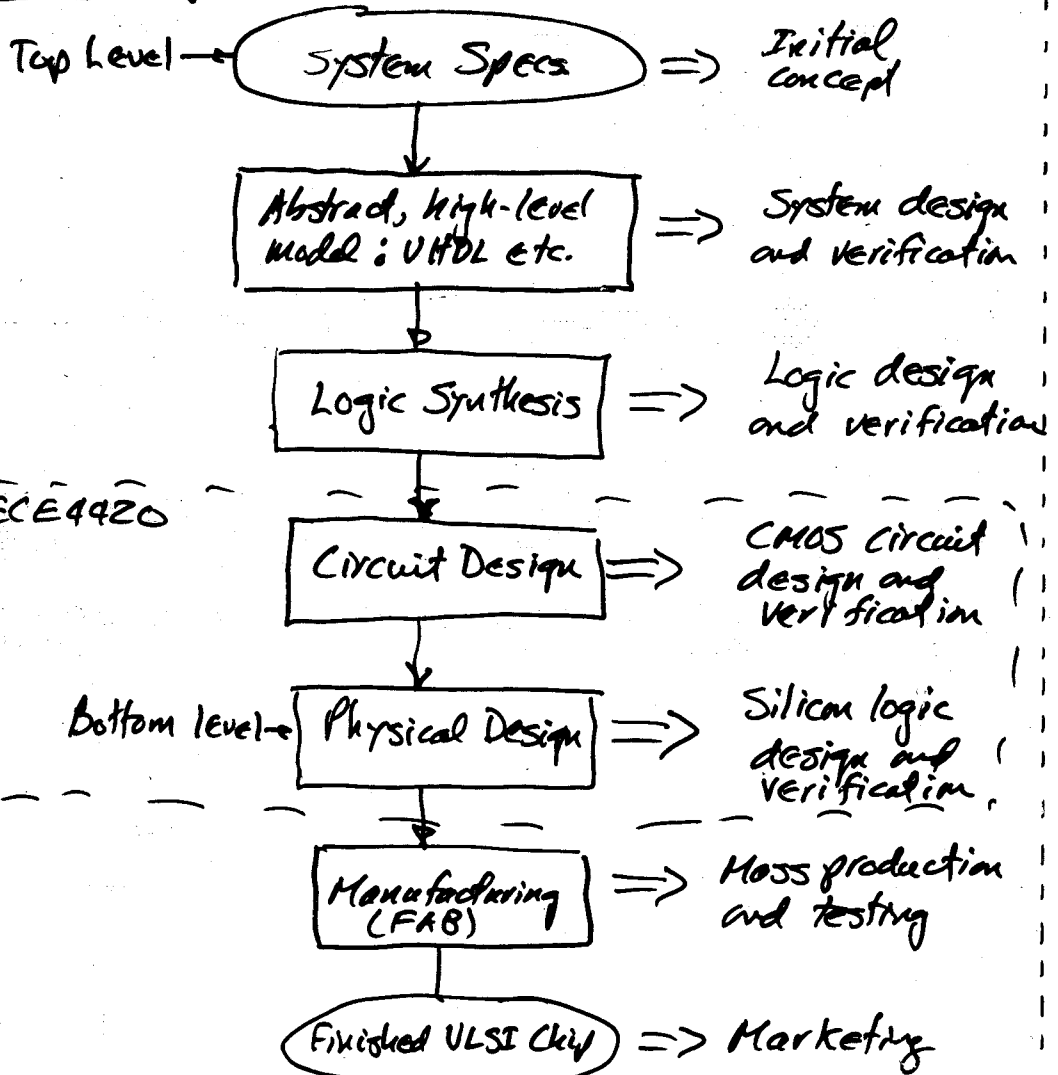

REVIEW OF DIGITAL GATE LOGIC


Basic Logic Functions-

1.) Inverter (NOT)




A	F
0	1
1	0

2.) AND ("•")

 


A	B	F
0	0	0
0	1	0
1	0	0
1	1	1


3.) NAND

 


A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

 

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

 


A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

 

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

7.) XNOR . . . .


De Morgan's Laws

 

Sequential Logic Circuits

A digital ckt. whose output is determined by both the present input and the results of a previous event

 Flip-flops (FF):  
 D-FF, JK-FF,  
 T-FF, SR-FF,  
 etc.



Positive-edge triggered DFFs

CLK	D	Q(old)	Q(new)
0	X	0	0
0	X	1	1
0 → 1	0	X	0
0 → 1	1	X	1
1	X	0	0
1	X	1	1
1 → 0	X	0	0
1 → 0	X	1	1