
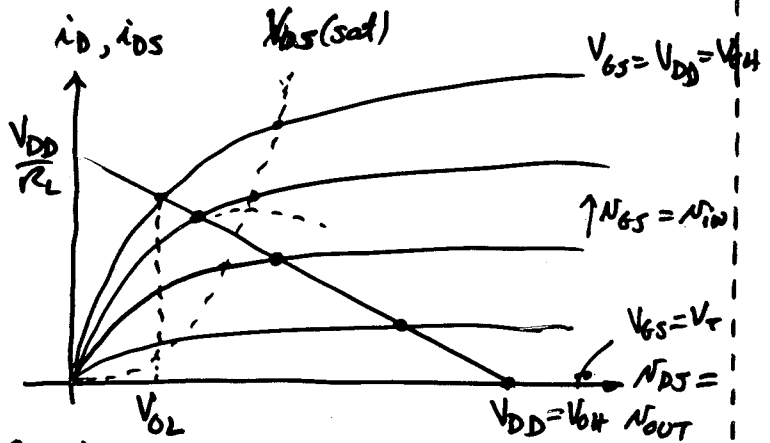


Exam 1 - Friday, Feb. 11 (see website for Exam 1 Preview)


Problem Session - 7pm - 8pm, Thurs. Homework: P.43 & P.49 → #5

RESISTOR LOAD INVERTER DESIGN

Graphical Perspective

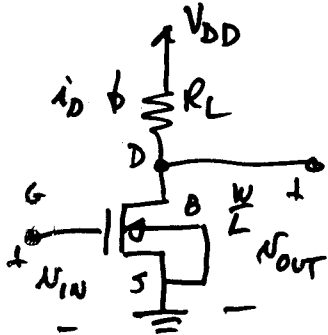

Voltage Transfer Curve (VTC):

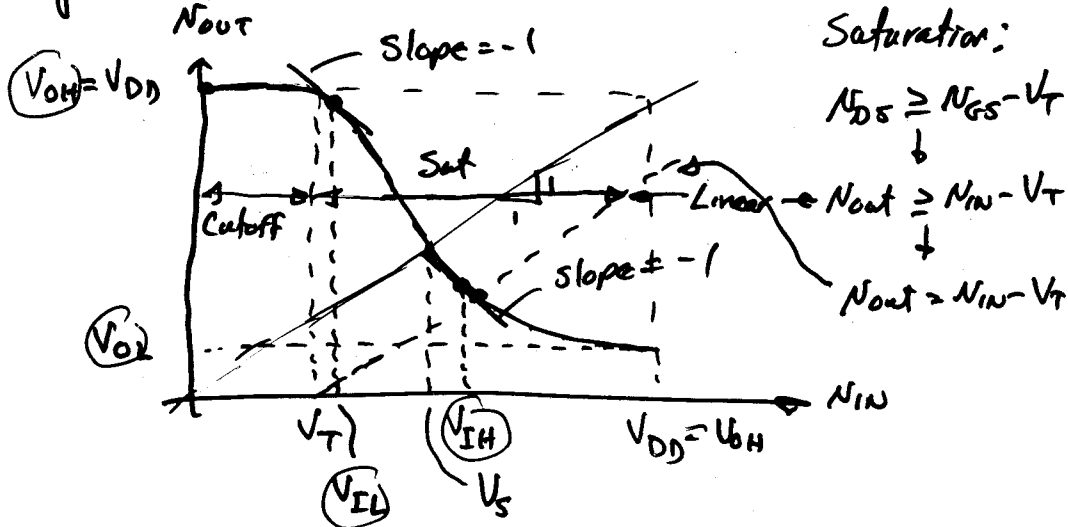

Saturation:

$$N_{DS} \geq N_{GS} - V_T$$

$$\downarrow$$

$$N_{out} \geq N_{in} - V_T$$

$$\downarrow$$

$$N_{out} = N_{in} - V_T$$

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

Mathematical Perspective

1.) $V_{OH} = V_{DD}$ If $N_m \leq V_T$

2.) $V_{OL} = ?$ Assume the MOSFET is in the linear region & mm. channel length (velocity saturation)

$$I_R = I_{DS}(\text{linear}) \text{ and } N_{GS} = V_{DD} = V_{OH} \text{ \& } N_{DS} = V_{OL}$$

$$\frac{V_{DD} - V_{OL}}{R_L} = \frac{1}{2} \frac{W_n}{L_n} \left(\frac{\mu_n C_{ox}}{1 + \frac{V_{OL}}{E_c L_n}} \right) [2(V_{OH} - V_T)V_{OL} - V_{OL}^2]$$

Assume also that $E_c L_n > V_{OL}$,

$$\frac{V_{DD} - V_{OL}}{R_L} \approx \underbrace{\frac{\mu_n C_{ox} W_n}{2 L_n}}_{\frac{k}{2}} [2(V_{OH} - V_T)V_{OL} - V_{OL}^2]$$

where $k = \mu_n C_{ox} \frac{W_n}{L_n}$

$$\frac{2(V_{DD} - V_{OL})}{k R_L} = 2(V_{OH} - V_T)V_{OL} - V_{OL}^2$$

Writing as a quadratic,

$$V_{OL}^2 - 2\left(\frac{1}{k R_L} + V_{OH} - V_T\right)V_{OL} + \frac{2V_{DD}}{k R_L} = 0$$

Assume further that V_{OL}^2 is small, i.e. $V_{OL}^2 \approx 0$

$$\underline{\underline{V_{OL} \approx \frac{V_{DD}}{1 + k R_L (V_{OH} - V_T)}}} \quad (V_{DD} = V_{OH})$$

Tradeoffs:

$k \uparrow \Rightarrow V_{OL} \downarrow, \text{ Area } \uparrow, \text{ Fall time } \downarrow, \text{ Power } \uparrow$

$R_L \uparrow \Rightarrow V_{OL} \downarrow, \text{ Area } \uparrow, \text{ Rise time } \uparrow, \text{ Power } \downarrow$

3.) $V_{IL} = ?$ Assume the MOSFET is saturated and that $N_{IN} - V_T$ is small.

$$I_R = I_{DS} \rightarrow \frac{V_{DD} - N_{OUT}}{R_L} = \frac{W N_{sat} C_{ox} (N_{IN} - V_T)^2}{(N_{IN} - V_T) + E_{CL}} \approx \frac{W N_{sat} C_{ox} (N_{IN} - V_T)^2}{E_{CL}}$$

However, $N_{sat} = \frac{\mu E_{CL}}{2 k'}$

$$\frac{V_{DD} - N_{OUT}}{R_L} = \frac{\mu_n C_{ox} \frac{W_n}{L_n} (N_{IN} - V_T)^2}{2} = \frac{k}{2} (N_{IN} - V_T)^2$$

Differentiate w.r.t. N_{IN} ,

$$-\frac{1}{R_L} \frac{\partial N_{OUT}}{\partial N_{IN}} = k (N_{IN} - V_T) \cdot 1 \rightarrow \frac{1}{R_L} = k (V_{IL} - V_T)$$

$$\underline{V_{IL} = V_T + \frac{1}{k R_L}}$$

$$NM_L = V_{IL} - V_{OL} = V_T + \frac{1}{k R_L} - \frac{V_{DD}}{1 + k R_L (V_{DD} - V_T)}$$

4.) V_{IH} Assume that the MOSFET is in linear operation and $N_{OUT} < E_{CL}$

$$I_{DS} = I_R \rightarrow \frac{W}{L} \frac{\mu_n C_{ox}}{1 + \frac{N_{OUT}}{E_{CL}}} \left[(N_{IN} - V_T) N_{OUT} - \frac{N_{OUT}^2}{2} \right] = \frac{V_{DD} - N_{OUT}}{R_L}$$

$$k \left[(N_{IN} - V_T) N_{OUT} - \frac{N_{OUT}^2}{2} \right] \approx \frac{V_{DD} - N_{OUT}}{R_L}$$

Take the partial derivative w.r.t. N_{IN} ,

$$k \left[(V_{IN} - V_T) \frac{\partial N_{OUT}}{\partial N_{IN}} + N_{OUT} - N_{OUT} \frac{\partial N_{OUT}}{\partial N_{IN}} \right] = \frac{1}{R_L} \frac{\partial N_{OUT}}{\partial N_{IN}}$$

$$k \left[-(V_{IN} - V_T) + 2 N_{OUT} \right] = \frac{1}{R_L} \rightarrow V_{IN} = V_{IH} = 2 V_{OUT} + V_T - \frac{1}{k R_L}$$

Solve for V_{IH} from the following eqs.

$$\left. \begin{array}{l} 1.) V_{IH} = 2V_{OUT} + V_T - \frac{1}{kR_L} \\ 2.) \frac{k}{2} [2(V_{IH} - V_T)V_{OUT} - V_{OUT}^2] = \frac{V_{DD} - V_{OUT}}{R_L} \end{array} \right\} \underline{\underline{V_{IH} = V_T + \sqrt{\frac{8V_{DD}}{3kR_L}} - \frac{1}{kR_L}}}$$

$$\therefore NM_H = V_{OH} - V_{IH} = V_{DD} - V_T - \sqrt{\frac{8V_{DD}}{3kR_L}} + \frac{1}{kR_L}$$

Example

Find NM_L and NM_H if $k' = 430 \frac{\mu A}{V^2}$, $V_T = 0.4V$,
 $\frac{W}{L} = 2$, $V_{DD} = 1.2V$ and $R_L = 20k\Omega$.

Solution:

$$V_{OH} = V_{DD} = 1.2V \quad k = k' \frac{W}{L} = 860 \frac{\mu A}{V^2}$$

$$V_{OL} \approx \frac{1.2}{1 + (0.86)(20)(1.2 - 0.4)} = 0.081V$$

$$V_{IL} = 0.4 + \frac{1}{(0.86)(20)} = 0.46V$$

$$V_{IH} = 0.4 + \sqrt{\frac{8(1.2)}{3(0.86)(20)}} - \frac{1}{(0.86)(20)} = 0.773$$

$$NM_L = V_{IL} - V_{OL} = 0.46 - 0.081 = 0.38V$$

$$NM_H = V_{OH} - V_{IH} = 1.2 - 0.773 = 0.43V$$