
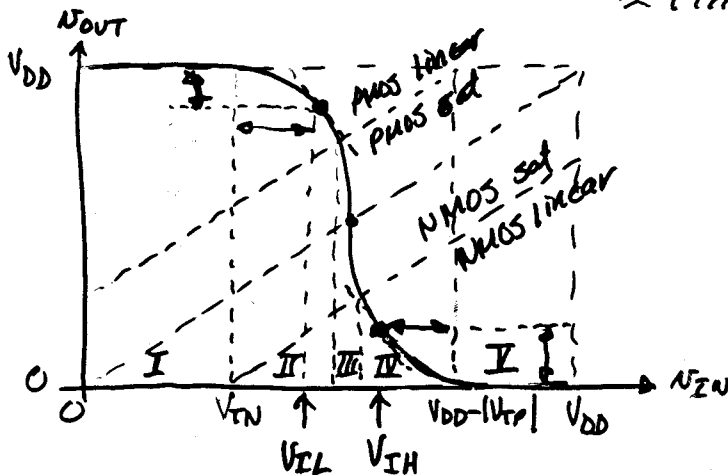


DC Analysis of the CMOS Inverter - Cont'd

Exam #1 Aver.
≈ 79/100

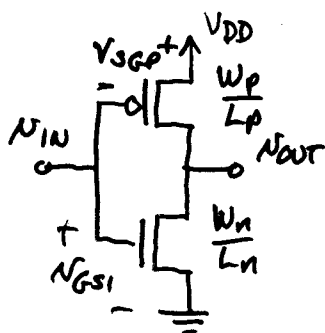

V_{IL} (Region II)

Procedure:

- 1.) Equate currents for the correct operating region of FETs
- 2.) Perform $\frac{\partial N_{out}}{\partial N_{in}}$ and set $\frac{\partial N_{out}}{\partial N_{in}} = -1$
- 3.) Solve the above two eqs. for V_{IL}

$$I_{DN}(sat) = I_{DP}(lin)$$

$$\frac{W_N N_{sat} C_{ox} (N_{in} - V_{TN})^2}{(N_{in} - V_{TN}) + E_{CN} L_N} = \frac{W_P}{L_P} \frac{\mu_p C_{ox}}{1 + \frac{V_{DD} - N_{out}}{E_{CP} L_P}} \left[(V_{DD} - N_{in} - |V_{TP}|)(V_{DD} - N_{out}) - \frac{(V_{DD} - N_{out})^2}{2} \right]$$

Assumptions: $N_{in} - V_{TN} \neq 0$ and $N_{out} \approx V_{DD} \Rightarrow N_{out} - V_{DD} = \text{small}$

$$\frac{W_N N_{sat} C_{ox} (N_{in} - V_{TN})^2}{E_{CN} L_N} \approx \frac{W_P}{L_P} \mu_p C_{ox} \left[(V_{DD} - N_{in} - |V_{TP}|)(V_{DD} - N_{out}) - \frac{(V_{DD} - N_{out})^2}{2} \right]$$

Since $N_{sat} = \frac{\mu_n E_{CN}}{2}$

$$(1) \quad \frac{W_N}{L_N} \frac{\mu_n}{2} (N_{in} - V_{TN})^2 = \frac{W_P}{L_P} \mu_p \left[(V_{DD} - N_{in} - |V_{TP}|)(V_{DD} - N_{out}) - \frac{(V_{DD} - N_{out})^2}{2} \right]$$

Differentiating w.r.t. N_{in}

$$\frac{W_N}{L_N} \mu_n (N_{in} - V_{TN}) = \frac{W_P}{L_P} \mu_p \left[(V_{DD} - N_{in} - |V_{TP}|) \left(-\frac{\partial N_{out}}{\partial N_{in}} \right) + (V_{DD} - N_{out})(-1) - (V_{DD} - N_{out}) \left(-\frac{\partial N_{out}}{\partial N_{in}} \right) \right]$$

If $N_{IN} = V_{IL}$ and $N_{OUT} = V_{OUT}$

$$\frac{W_N}{L_N} \mu_n (V_{IL} - V_{TN}) = \frac{W_P}{L_P} \mu_p \left[(V_{DD} - V_{IL} - |V_{TP}|) + (V_{DD} - V_{OUT}) \right] + (V_{DD} - V_{OUT})$$

$$(2) \quad V_{IL} = \frac{2V_{OUT} - V_{DD} - |V_{TP}| + (k_N/k_P)(V_{TN})}{1 + k_N/k_P}$$

$$k_N = \mu_n C_{ox} \frac{W_N}{L_N}$$

$$k_P = \mu_p C_{ox} \frac{W_P}{L_P}$$

Solve eqs. (1) and (2) to find V_{IL} .

V_{IH} (Region IV)

$$i_{DN}(lm) = i_{DP}(sat)$$

$$\frac{W_P}{L_N} \frac{\mu_n C_{ox}}{1 + \frac{N_{OUT}}{E_{CN} L_N}} \left[(N_{IN} - V_{TN}) N_{OUT} - \frac{N_{OUT}^2}{2} \right] = \frac{W_P \mu_{sat} C_{ox} (V_{DD} - N_{IN} - |V_{TP}|)^2}{(V_{DD} - N_{IN} - |V_{TP}|) + E_{CP} L_P}$$

Assumptions:

$$N_{OUT} \text{ is small } \rightarrow \frac{N_{OUT}}{E_{CN} L_N} \ll 1 \text{ and } (V_{DD} - N_{IN} - |V_{TP}|) < E_{CP} L_P$$

$$(1) \quad \therefore \mu_n C_{ox} \frac{W_N}{L_N} \left[(N_{IN} - V_{TN}) N_{OUT} - \frac{N_{OUT}^2}{2} \right] \approx \frac{W_P C_{ox} \mu_p}{L_P} \left[V_{DD} - N_{IN} - |V_{TP}| \right]^2$$

Differentiating w.r.t. N_{IN} , gives

$$\begin{aligned} \mu_n C_{ox} \frac{W_N}{L_N} \left[(V_{IN} - V_{TN}) \left(\frac{\partial N_{OUT}}{\partial N_{IN}} \right) + N_{OUT} - N_{OUT} \frac{\partial N_{OUT}}{\partial N_{IN}} \right] \\ = \mu_p C_{ox} \frac{W_P}{L_P} \left[(V_{DD} - V_{IN} - |V_{TP}|) \right] (-1) \end{aligned}$$

$$\text{If } \mu_p C_{ox} \frac{W_P}{L_P} = k_P \text{ and } \mu_n C_{ox} \frac{W_N}{L_N} = k_N \text{ and } \frac{\partial N_{OUT}}{\partial N_{IN}} = -1$$

$$(2) \quad \therefore V_{IH} = \frac{2V_{OUT} + V_{TN} + (k_P/k_N)(V_{DD} - |V_{TP}|)}{1 + k_P/k_N}$$

Solve Eqs. (1) and (2) for V_{IH} .

Example

Find NM_H and NM_L for a CMOS inverter if

$$W_N = 400\text{nm}, W_P = 800\text{nm}, \mu_n = 270\text{cm}^2/\text{V}\cdot\text{s},$$

$$\mu_p = 70\text{cm}^2/\text{V}\cdot\text{s}, C_{ox} = 1\text{mF}/\text{cm}^2, V_{TN} = 0.5\text{V},$$

$$V_{TP} = -0.5\text{V}, E_{cNLN} = 1.2\text{V}, E_{cPLP} = 4.2\text{V}, N_{\text{sat}} = 8 \times 10^{-6}\text{cm}^3/\text{s},$$

$$V_{DD} = 1.8\text{V} \text{ and } L_P = L_N = L = 200\text{nm}.$$

Solution:

$$V_{OH} = V_{DD} = \underline{1.8\text{V}}, V_{OL} = \underline{0}, k_n = (270)(10^{-6})(2) = 540\ \mu\text{A}/\text{V}^2$$

$$k_p = (70)(10^{-6})(4) = 280\ \mu\text{A}/\text{V}^2$$

$$V_{IL}: V_{IL} = \frac{2V_{out} - 1.8 - 0.5 + \left(\frac{540}{280}\right)0.5}{1 + \frac{540}{280}} \rightarrow V_{out} = 1.4645V_{IL} + 0.668 \quad (1)$$

2nd eq.

$$\frac{540}{2}(V_{IL} - 0.5)^2 = 280 \left[(1.8 - V_{IL} - 0.5)(1.8 - V_{out}) - \frac{(1.8 - V_{out})^2}{2} \right]$$

Assume $V_{out} \approx 1.8 \rightarrow 1.8 - V_{out} \approx 0$

$$(V_{IL} - 0.5)^2 = 1.037(1.3 - V_{IL})(1.8 - V_{out}) \quad (2)$$

Substituting (1) into (2) gives

$$V_{IL}^2 - 4.141V_{IL} + 2.460 = 0 \rightarrow V_{IL} = \underline{0.719\text{V}}$$

$$V_{IH}: V_{IH} = \frac{2V_{out} + 0.5 + \frac{280}{540}(1.8 - 0.5)}{1 + \frac{280}{540}} \rightarrow V_{out} = 0.7593V_{IH} - 0.5875 \quad (3)$$

$$540 \left[(V_{IH} - 0.5)V_{out} - \frac{V_{out}^2}{2} \right] = \frac{280}{2} [1.8 - V_{IH} - 0.5]$$

Assume $V_{out} \approx 0$

$$\therefore (V_{IH} - 0.5)V_{out} = \frac{280}{2 \cdot 540} (1.3 - V_{IH})^2 \quad (2)$$

$$(1) \rightarrow (2) \Rightarrow V_{IH}^2 - 0.6299V_{IH} - 0.3098 = 0$$

$$V_{IH} = \underline{0.954\text{V}} \quad (0.909\text{V})$$

$$NM_H = V_{OH} - V_{IH} = 1.8 - 0.954 = \underline{\underline{0.846V}}$$

$$NM_L = V_{IL} - V_{OL} = 0.719 - 0 = \underline{\underline{0.719V}}$$

Layout

(See layout of CMOS inverter)