 


Shengyuan Li will lecture in ECE 4420 2/21 - 2/25



Fan-out (FO):

$$FO = \frac{C_{out}}{C_{gate}} = \frac{\text{Total capacitance driven by the gate}}{\text{Input capacitance of the gate}}$$





Voltage Transfer Curve of Some Simple CMOS Gates

NAND2:

 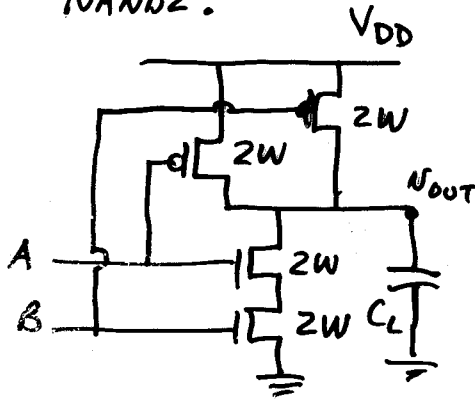

NOR2:

  

Example 5.2

Compute V_S for a NAND2 when a.) One input is at V_{DD} and the other is switched from 0 to V_{DD} . b.) When both inputs are switched together. Assume $0.18 \mu\text{m}$ technology and all W 's = $0.4 \mu\text{m}$. (Assume $L = 0.2 \mu\text{m}$)

$$a.) X = \sqrt{\frac{W_n/E_{cn}L_n}{W_p/E_{cp}L_p}} = \sqrt{\left(\frac{W_n}{W_p}\right) \frac{E_{cp}L_p}{E_{cn}L_n}} = \sqrt{\frac{400 \cdot 4.8}{400 \cdot 1.2}} = 2$$

$$\therefore V_S = \frac{V_{DD} - |V_{tp}| + X V_{tn}}{1 + X} = \frac{1.8 - 0.5 + (2)(0.5)}{1 + 2} = \underline{\underline{0.77V}}$$

b.) With both inputs tied together $W_p = 800 \text{ nm}$
 $W_n = 200 \text{ nm}$

$$X = \sqrt{\frac{200(4.8)}{800(1.2)}} = 1 \rightarrow V_{SS} = \frac{1.8 - 0.5 + 0.5(1)}{1 + 1} = \underline{\underline{0.9V}}$$

COMPLEX CMOS GATESExample

Synthesize $F = \overline{(A+B) \cdot C}$ in CMOS logic
 How?

1.) De Morgan's Laws

$$\overline{(a+b)} = \bar{a} \cdot \bar{b}$$

$$\overline{(a \cdot b)} = \bar{a} + \bar{b}$$

Duality Relationships

$$ab \Leftrightarrow a + b$$

$$(a+b)c \Leftrightarrow ab + c$$

2.) AND in CMOS means series NMOS and parallel PMOS
 OR in CMOS means parallel NMOS and series PMOS


$$F = \overline{(A+B) \cdot C} = \overline{A+B} + \bar{C} = \bar{A} \cdot \bar{B} + \bar{C}$$

3.) Since NMOS acts to pull F low, synthesize the NMOS from \bar{F} .

$$F = \overline{(A+B) \cdot C} \rightarrow \bar{F} = \overline{\overline{(A+B) \cdot C}} = (A+B) \cdot C$$


3.) Cont'd

$$\bar{F} = (A+B) \cdot C$$

 


 4.) Since the PMOS pulls F high, we can realize the PMOS by realizing F with all inputs complimented.

$$F = \overline{(A+B) \cdot C} = \bar{A} \cdot \bar{B} + \bar{C} \rightarrow F = (A \cdot B) + C$$




5.)

 

6.) Note the \bar{F} is the dual of $F(\bar{A}, \bar{B}, \bar{C})$

$$F(\bar{A}, \bar{B}, \bar{C}) = A \cdot B + C \xrightarrow{\text{Dual}} \bar{F} = (A+B) \cdot C$$

Generalization of Complex Gate Synthesis

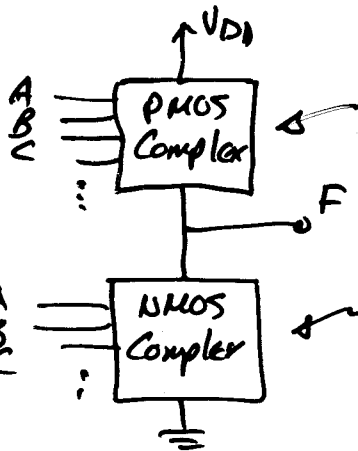

Function of complemented variables that sets $F=1$ and creates a path from F to V_{DD} .

Complement of the function that sets the output to 0 due to a path from F to ground.

- 1.) \bar{F} implements the NMOS complex
- 2.) Dual \bar{F} is used to implement the PMOS complex.

Ex. 5.3

Implement $F = \overline{AB+CD}$ as a single-stage CMOS gate and as a pseudo-NMOS gate.



CMOS Gate:

$$F = AB + CD$$

$$\bar{F} = (\overline{A+B}) \cdot (\overline{C+D})$$

dual

pseudo-NMOS gate:

  


XOR Gate

$$F_{xor} = \bar{a}b + a\bar{b} \rightarrow \bar{F}_{xor} = \overline{\bar{a}b + a\bar{b}} = (\overline{\bar{a}b}) \cdot (\overline{a\bar{b}})$$

$$= (a + \bar{b}) \cdot (\bar{a} + b) = a\bar{a} + ab + \bar{b}\bar{a} + \bar{b}b$$

$$= ab + \bar{a}\bar{b} \rightarrow \text{NMOS}$$
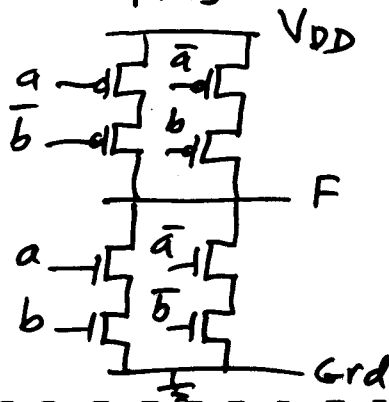
$$F_{xor} / \text{dual} = \underbrace{a\bar{b} + \bar{a}b}_{\text{PMOS}}$$



F_{XNOR} next