

XOR and XNOR Gates

$F_{XOR} = \bar{a}b + a\bar{b}$





$\Rightarrow \bar{F}_{XOR} = \overline{\bar{a}b + a\bar{b}} = (\overline{\bar{a}b})(\overline{a\bar{b}})$

PMOS:

$F_{XOR} = \bar{a}\bar{b} + \bar{a}b$
 $= (\bar{a} + \bar{b})(\bar{a} + b)$

NMOS:

    $\bar{F}_{XOR} = (a + \bar{b})(\bar{a} + b)$
 $= ab + \bar{a}\bar{b}$







$F_{XNOR} = \bar{a}\bar{b} + ab$

PMOS:

$\bar{F}_{XNOR} = \bar{a}b + a\bar{b}$
 $= (\bar{a} + \bar{b})(\bar{a} + b)$

NMOS:

    $\bar{F}_{XNOR} = (a + b)(\bar{a} + \bar{b})$
 $= a\bar{b} + \bar{a}b$





Multiplexer (two inputs)

$F = as + b\bar{s}$

PMOS: $F = \bar{a}\bar{s} + \bar{b}\bar{s}$

  NMOS: $\bar{F} = \overline{as + b\bar{s}}$
 $= (\bar{a} + \bar{s})(\bar{b} + s)$





Flip-Flops AND LATCHES

DEF:

Combinational Logic ckt: no feedback, output = $f(\text{inputs})$
 sequential " : new output = $f(\text{inputs, old outputs})$,
 use positive feedback

Basic Bistable ckt:

 
 


- A bistable ckt can be triggered to move from one state to another by moving past V_s for a duration of $2t_p$

$$t_p = (t_{PHL} + t_{PLH}) / 2$$

- In the absence of a trigger, the bistable remains in that state

SR latch w/ NOR gates:

 
 


S	R	Q	Q̄
0	0	Q	Q̄ (Hold)
0	1	0	1 (Reset)
1	0	1	0 (Set)
1	1	0	0 (N/A)

Delay from $S \rightarrow \bar{Q}$ or $R \rightarrow Q$ is one NOR delay

" " $S \rightarrow Q$ or $R \rightarrow \bar{Q}$ " two "

SR Latch w/ NAND gates:

  


S	R	Q	Q̄
0	0	Q	Q̄ (Hold)
0	1	1	0 (set)
1	0	0	1 (reset)
1	1	1	1 (N/A)

$S \rightarrow Q$ or $R \rightarrow \bar{Q}$: one NAND delay

$S \rightarrow \bar{Q}$ or $R \rightarrow Q$: two "

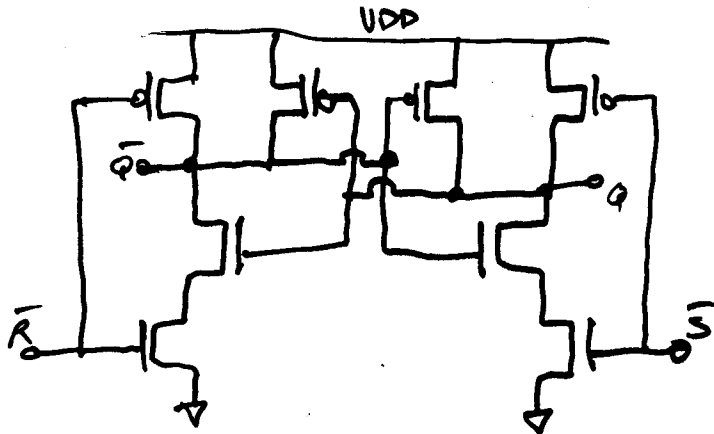EX 5.4 NAND-based SR Latch, $t_p = 400$ ps, $C_L = 100$ fF
 0.13 μ m CMOS $L = 0.1$ μ m \Rightarrow sizes?



$$t_{pHL} = t_{pLH} = 0.7 R_{eff} C_L = 200 \text{ ps}$$

$$t_{pHL} = 0.7 (2 \times 12.5 \text{ k}\Omega / 2) \frac{C_L}{W} (100 \text{ fF})$$


$$\Rightarrow \frac{W}{L} = \frac{(0.7)(25)(100)}{200} = 8.75$$

$$\Rightarrow W_n = 0.875 \text{ } \mu\text{m}$$


$$t_{pLH} = (0.7)(30 \text{ k}\Omega / 2) \frac{C_L}{W} (100 \text{ fF})$$

$$\Rightarrow W/L = \frac{(0.7)(30)(100)}{200} = 10.5 \Rightarrow W_p = 1.05 \text{ } \mu\text{m}$$

 JK Flip-Flop: Two additional feedback lines remove ambiguity
 $S \bar{R} \Rightarrow J \bar{K}$




J_n	K_n	Q _{n+1}
0	0	Q _n
0	1	0 (Reset)
1	0	1 (Set)
1	1	\bar{Q}_n

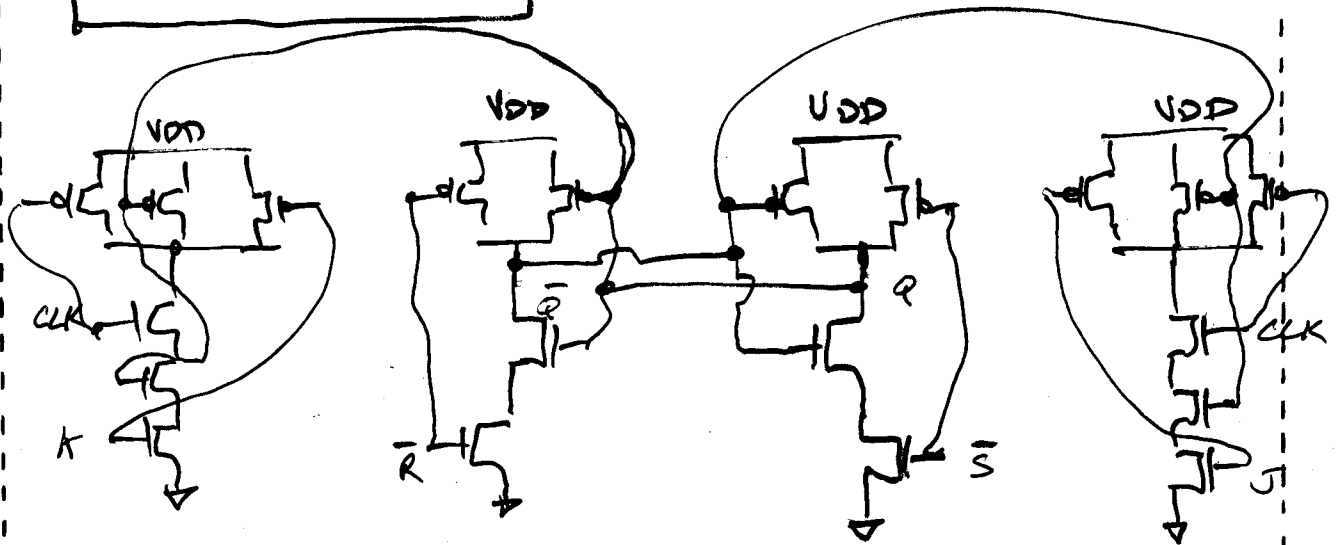

CMOS implementation

JK Master-Slave Flip Flop

 


Operation:

1. CK rises, \overline{CK} goes down and disables the slave NAND gates.
2. CK enables the input NAND gates of the master.
3. The influence of J and K is entered into the master.
4. On the falling edge of CK, the master is disabled and the slave enabled.
5. The state of the master is transferred to the slave.

One-catching problem:

With CK high and the slave in the reset state, if the J input gate is enabled for a short while and returns to 0, the high value on J will propagate into the master and lock in place.

JK Edge-Triggered Flip-Flop

 

J_n	K_n	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$


Operation:

Set up time: Time JK must be stable before CK.
 Hold time: Time JK must be stable after CK

- 1.) With CK high, entry into the input NAND gates is controlled by J & K, feedback lines. Entry into the NAND latch requires CK to go low.
- 2.) When CK goes low, the input NAND gates are disabled and the output of flip-flop changes due to the state of the J and/or K inputs prior to CK going low.

D Flip-Flops and Latches (D-Flops)


D-Latch -

 


D	Q _{n+1}
0	0
1	1

"Transparent" to the input.

Edge-triggered D-Flop -

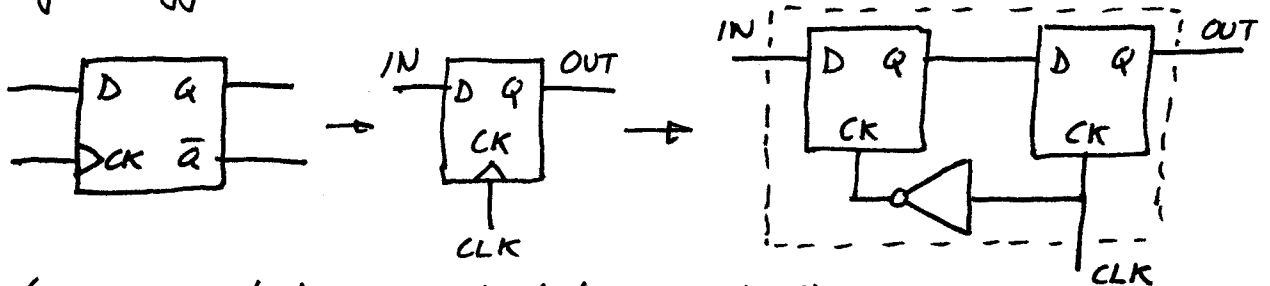

 Comparison between a D-latch and D-flop -



TIMING ISSUES -

T_{setup} = time incoming data must be stable before the clock

T_{hold} = " " " " " " " " after " "

T_{ck-q} = delay from the time the clock arrives to the point when Q stabilizes

T_{d-q} = time it takes the data to propagate thru the D-latch

Implementation of a D-latch -

