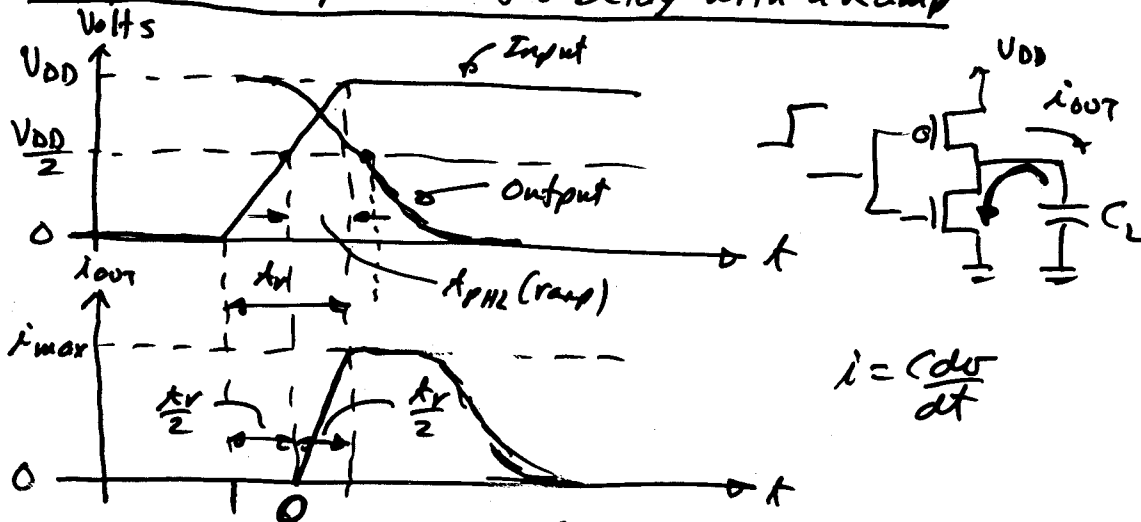


Exam #2 - Friday 11th

Prob. Session - Thursday 5pm-6pm (C240?)

Analytical Expression for Delay with a Ramp

$$i_{out} = C \frac{dV_{out}}{dt} \Rightarrow \int i_{out} dt = \int C_L dV_{out}$$

$$\int_0^{t_r/2} i_{out} dt + \int_{t_r/2}^{t_r + t_{PHL}(\text{ramp})} i_{out} dt = C_L \int_0^{V_{DD}/2} dV_{out}$$

$$\Downarrow$$

$$i_{max} \left(\frac{t_r}{4} + t_{PHL}(\text{ramp}) - \frac{t_r}{2} \right) = \frac{C V_{DD}}{2}$$

$$t_{PHL}(\text{ramp}) = \frac{t_r}{4} + \frac{C V_{DD}}{2 i_{max}} = \frac{t_r}{4} + t_{PHL}(\text{step})$$


Generalization:

If t_{in} is the input rise/fall time and is approximated at $\frac{t_r}{2}$, then

$$t_{ramp} \approx \frac{t_{in}}{2} + t_{step} = \frac{t_{in}}{2} + 0.7 RC$$

Taking these concepts to an inverter chain we can develop a general formula -

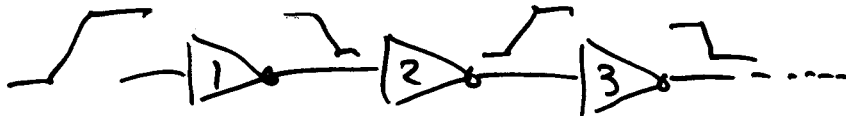
$$\text{Total delay} \approx \sum_i R_i C_i$$



$$\begin{aligned} \text{Total delay} &= \frac{t_m}{2} + t_{PHL1} + \frac{t_{m1} + t_{PHL2}}{2} + \frac{t_{m2}}{2} + t_{PHL3} + \dots \\ &= \frac{t_m}{2} + \underbrace{0.7 R_1 C_1 + 0.7 R_1 C_1}_{\approx R_1 C_1} + \underbrace{0.7 R_2 C_2 + 0.7 R_2 C_2}_{\approx R_2 C_2} + \dots \\ &\approx \sum_{i=1}^n R_i C_i \end{aligned}$$


How Do you Optimally Size The Inverters for Min Delay?

Minimize the delay globally -

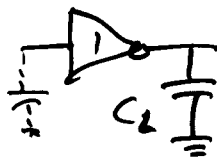


$$R_{eff1} C_L$$

Inverter delay -

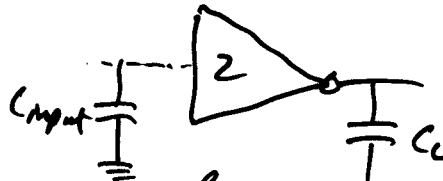

$$R_{eff2} C_L$$

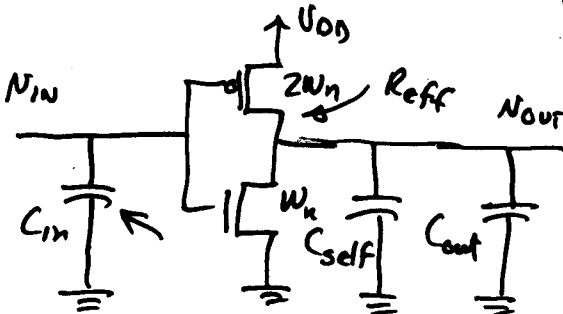If $R_{eff} \downarrow$, the C_{input} goes up
(Move the delay to the previous stage)



Gate time constant, τ_{inv} :

$$\begin{aligned} \tau_{inv} &\equiv R_{eff} C_{in} = R_{eqn} \left(\frac{L_n}{W_n} \right) C_g (3W_n) \\ &= 3 R_{eqn} C_g L_n \end{aligned}$$

$$\begin{aligned} \tau_{\text{delay}} &= R_{\text{eff}} [C_{\text{out}} + C_{\text{self}}] = R_{\text{eff}} C_{\text{in}} \left[\frac{C_{\text{out}}}{C_{\text{in}}} + \frac{C_{\text{self}}}{C_{\text{in}}} \right] \\ &= \tau_{\text{inv}} \left[\frac{C_{\text{out}}}{C_{\text{in}}} + \gamma_{\text{inv}} \right] \quad \gamma_{\text{inv}} \equiv \frac{C_{\text{self}}}{C_{\text{in}}} \end{aligned}$$

Note: C_{self} is strongly dependent on the layout

$$\text{Fanout of the inverter} = f = \frac{C_{\text{out}}}{C_{\text{in}}}$$

$$\therefore \tau_{\text{delay}} = \tau_{\text{inv}} [f + \gamma_{\text{inv}}]$$


Ex. 6.8

Find τ_{inv} and γ_{inv} for 0.18 μm technology

$$\tau_{\text{inv}} = 3 R_{\text{eqn}} C_g L_n = 3 (12.5 \text{ k}\Omega) (2 \text{ fF}/\mu\text{m}) (0.2 \mu\text{m}) = 15 \text{ ps}$$

$$\gamma_{\text{inv}} = \frac{C_{\text{self}}}{C_{\text{in}}} = \frac{C_{\text{eff}} (3W)}{C_g (3W)} = \frac{1 \text{ fF}}{2 \text{ fF}} = \frac{1}{2}$$

Optimal Sizing of an Inverter Chain

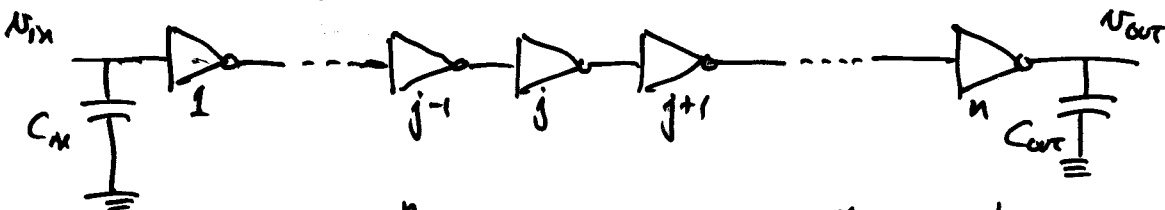

$$\begin{aligned} \text{Total Delay} &= \sum_{j=1}^n \tau_{\text{inv}} \left(\frac{C_{j+1}}{C_j} + \gamma_{\text{inv}} \right) = \sum_{j=1}^n \tau_{\text{inv}} \left(\frac{C_j W_{j+1}}{C_j W_j} + \gamma_{\text{inv}} \right) \\ &= \sum_{j=1}^n \tau_{\text{inv}} \left(\frac{W_{j+1}}{W_j} + \gamma_{\text{inv}} \right) \end{aligned}$$

$$\text{Consecutive Delay} \equiv D_j = \tau_{\text{inv}} \left(\frac{W_j}{W_{j-1}} + \gamma_{\text{inv}} \right) + \tau_{\text{inv}} \left(\frac{W_{j+1}}{W_j} + \gamma_{\text{inv}} \right)$$


$$\frac{\partial D_j}{\partial W_j} = \tau_{\text{inv}} \frac{1}{W_{j-1}} - \tau_{\text{inv}} \frac{W_{j+1}}{(W_j)^2} = 0 \rightarrow W_j = \sqrt{W_{j+1} W_{j-1}}$$

In general,

$$W_j = (W_1 W_2 W_3 \cdots W_{j-1} W_{j+1} \cdots W_{n-1} W_n)^{1/n}$$

How do we achieve the corresponding geometrical sizing?

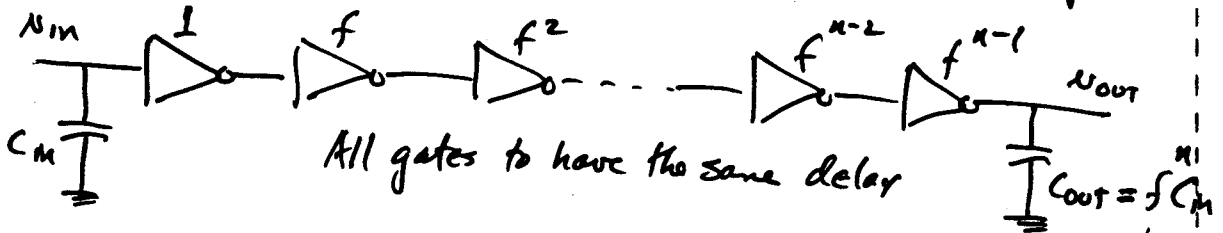Increase the size of each inverter by a fanout, $f = \frac{W_{j+1}}{W_j}$



Total delay = $n \times \text{gate delay} = n \times \tau_{inv} \left(\frac{C_j}{C_{j+1}} + \delta_{inv} \right)$ $n = \frac{\ln \left(\frac{C_{out}}{C_{in}} \right)}{\ln f}$

Total delay = $\frac{\ln \left(\frac{C_{out}}{C_{in}} \right)}{\ln f} \tau_{inv} (f + \delta_{inv})$

What is τ_{inv} ?

$\tau_{inv} = 0 \rightarrow f = e = 2.72$
 $0.5 < \tau_{inv} < 2 \rightarrow 2.5 < f < 4$ } Fig. 6.23

Ex 6.9

1.) Find the optimal fanout for $n=N=3$ and the total delay if $C_{out} = 200fF$ and $C_{in} = 1fF$. Assume $\tau_{inv} = 7.5ps$ and $\delta_{inv} = \frac{1}{2}$

$\ln f = \frac{\ln \left(\frac{C_{out}}{C_{in}} \right)}{n} = \frac{\ln(200)}{3} = 1.766 \rightarrow f = 5.85$

Total delay = $3 (7.5ps) (5.85 + \frac{1}{2}) = \underline{\underline{143ps}}$

2.) Find the optimal n and the delay for this case.

$N = 4 \rightarrow 123ps$

From Fig. 6.23 for $\delta_{inv} = 0.5$ we see that $f \approx 3.6$

$\therefore N = \frac{\ln(200)}{\ln(3.6)} = 4.13 \rightarrow \underline{\underline{N=4}}$

Total delay = $4 (7.5ps) [3.6 + 0.5] = \underline{\underline{123ps}}$