

Exam #2 - Friday, March 11, 2005


Problem Session - Thursday, March 10, 2005 - 5pm - 6pm (C240)

Optimizing Logic Paths with NAND's, NOR's & Combinations

Inverters

$$\text{Total delay} = \sum_j \tau_{inv} \left(\frac{C_{j+1}}{C_j} + \gamma_{inv} \right)$$

$$\tau_{inv} = 3 R_{eqn} C_g L_n$$

 


1.) NAND2

$$\text{Total delay} = \sum_j \tau_{nand} \left(\frac{C_{j+1}}{C_j} + \tau_{nand} \right)$$

$$\tau_{nand} = R_{eff} C_n = R_{eqn} \left(\frac{L_n}{W_n} \right) (W_n + W_p) C_g = 4 R_{eqn} C_g L_n$$
 
$$f_{optimum} \approx 4 \quad (\text{Fig. 6.23 for NAND})$$




2.) NOR2

$$\text{Total delay} = \sum_j \tau_{nor} \left(\frac{C_{j+1}}{C_j} + \tau_{nor} \right)$$

$$\tau_{nor} = R_{eqn} \left(\frac{L_n}{W_n} \right) (5W_n) C_g = 5 R_{eqn} C_g L_n$$


3.) Combinations of Gates

 

Delay is minimized when $\gamma \cdot FO$ of a given gate is equal to the $\gamma \cdot FO$ of the next gate, regardless of the type of gate.

 Example of Computing the Optimal Gate Sizes along a Critical Path

Find the device sizes that optimize the delay thru the path indicated.



We know that

$$T_{\text{NAND}} \left(\frac{C_{j+1}}{C_j} \right) = T_{\text{NAND}} \left(\frac{C_{j+1}}{2fF} \right) = T_{\text{INV}} \left(\frac{C_{j+2}}{C_{j+1}} \right) = T_{\text{NOR}} \left(\frac{200fF}{C_{j+2}} \right)$$

$$\begin{aligned} \text{Fanout-delay} &= \sqrt[3]{T_{\text{NAND}} \left(\frac{C_{j+1}}{2fF} \right) T_{\text{INV}} \left(\frac{C_{j+2}}{C_{j+1}} \right) T_{\text{NOR}} \left(\frac{200fF}{C_{j+2}} \right)} \\ &= \sqrt[3]{T_{\text{NAND}} \cdot T_{\text{INV}} \cdot T_{\text{NOR}} \left(\frac{200}{2} \right)} = \sqrt[3]{5 \cdot 3 \cdot 4 (\text{Reqn } C_g L_n)^3 \cdot 100} \\ &= 18.17 \text{ Reqn } C_g L_n \approx 18.2 \text{ Reqn } C_g L_n \end{aligned}$$

C_{j+2} :

$$T_{\text{NOR}} \left(\frac{C_{\text{load}}}{C_{j+2}} \right) = 5 \text{ Reqn } C_g L_n \left(\frac{200}{C_{j+2}} \right) = 18.2 \text{ Reqn } C_g L_n$$

$$C_{j+2} = \frac{5(200fF)}{18.2} = 55fF = 5W_n C_g$$

$$11fF = W_n 2fF/\mu\text{m} \rightarrow W_n = \frac{11}{2} \mu\text{m} = \underline{5.5\mu\text{m}}$$

$$W_p = 4W_n = \underline{22\mu\text{m}}$$

C_{j+1} :

$$T_{\text{INV}} \left(\frac{C_{j+2}}{C_{j+1}} \right) = 3 \text{ Reqn } C_g L_n \left(\frac{55}{C_{j+1}} \right) = 18.2 \text{ Reqn } C_g L_n$$

$$C_{j+1} = \frac{3}{18.2} 55fF = 9.1fF = 3W_n C_g \rightarrow W_n = \underline{1.5\mu\text{m}}$$

$$W_p = \underline{3\mu\text{m}}$$

C_{in} :

$$T_{\text{NAND}} \left(\frac{C_{j+1}}{C_{in}} \right) = 4 \text{ Reqn } L_n \left(\frac{9.1fF}{C_{in}} \right) = 18.2 \text{ Reqn } L_n$$

$$C_{in} = \frac{4}{18.2} \times 9.1fF = 2fF = 4W_n C_g \rightarrow W_n = \underline{0.25\mu\text{m}}$$

$$W_p = \underline{0.25\mu\text{m}}$$

OPTIMIZING LOGIC DELAY PATHS WITH LOGICAL EFFORT

Logical Effort = $LE = \frac{\text{Total delay}}{\tau_{inv}}$

General path:

$$\frac{\text{Total Delay}}{\tau_{inv}} = \frac{\tau_{nand}}{\tau_{inv}} \left(\frac{C_{j+1}}{C_j} + \tau_{nand} \right) + \frac{\tau_{mux}}{\tau_{inv}} \left(\frac{C_{j+2}}{C_{j+1}} + \tau_{mux} \right) + \frac{\tau_{nor}}{\tau_{inv}} \left(\frac{C_{j+3}}{C_{j+2}} + \tau_{nor} \right)$$

Normalized Total delay = $D = \frac{\tau_{nand}}{\tau_{inv}} \frac{C_{j+1}}{C_j} + \frac{\tau_{nand}}{\tau_{inv}} \tau_{nand} + \dots$

$$= [LE_{nand} \cdot FO_1 + P_{nand}] + [LE_{mux} \cdot FO_2 + P_{mux}] + [LE_{nor} \cdot FO_3 + P_{nor}]$$

where $LE_{gate} = \frac{\tau_{gate}}{\tau_{inv}}$, $FO_j = \frac{C_{j+1}}{C_j}$, $P_{gate} = LE_{gate} \tau_{gate}$

What are the LE_{gate} ?

$$\tau_{inv} = 3R_{eqn}C_gL_n, \tau_{nand2} = 4R_{eqn}C_gL_n, \tau_{nor2} = 5R_{eqn}C_gL_n$$


$$LE_{inv} = 1 \quad LE_{nand2} = \frac{4}{3} \quad \& \quad LE_{nor2} = \frac{5}{3}$$

For n-input gates $\rightarrow LE_{nand} = \frac{n+2}{3} \quad \& \quad LE_{nor} = \frac{2n+1}{3}$



Parasitic term, P_0

Table 6.1
 
$$P_{inv} = LE_{inv} \tau_{inv} = LE_{inv} \frac{C_{self}}{C_{in}} = LE \times \frac{C_{eff} 3W}{C_g \cdot 3W} = LE \frac{C_{eff}}{C_g} = \frac{1}{2}$$


  
$$P_{nand} = LE_{nand} \times \frac{C_{self}}{C_m} = LE_{nand} \times \frac{C_{eff}(2W+2W+2W)}{C_g(2W+2W)} = \left(\frac{4}{3}\right)\left(\frac{1}{2}\right)\left(\frac{6}{4}\right) = 1$$



$$P_{nor} = LE_{nor2} \times \frac{C_{self}}{C_m} = LE_{nor} \times \frac{C_{eff}[W+4W+4W]}{C_g[W+4W]} = \frac{5}{3}\left(\frac{1}{2}\right)\left(\frac{9}{5}\right) = \frac{3}{2}$$

For n-input gates:

$$P_{nand}(n\text{-inputs}) = \frac{n}{2}$$

$$P_{nor}(n\text{-inputs}) = \frac{3n}{4} \text{ (Table 6.2)}$$

Next - Path Optimization of previous example using 2F