 


Implementation of Logic Functions using TG's



- 1.) Identify the control signals
- 2.) Build a truth table
- 3.) Convert the truth table to a multiplexer-style design by creating a path for each row of T.T. to the output.
- 4.) The desired outputs are routed from the input to output.

Example 1


$$F = AB + A\bar{B}C + \bar{A}\bar{C}$$

1.) Let A & B be control signals.

2.)

A	B	F
0	0	$\bar{C}$
0	1	$\bar{C}$
1	0	C
1	1	1

3.) Two-level MUX

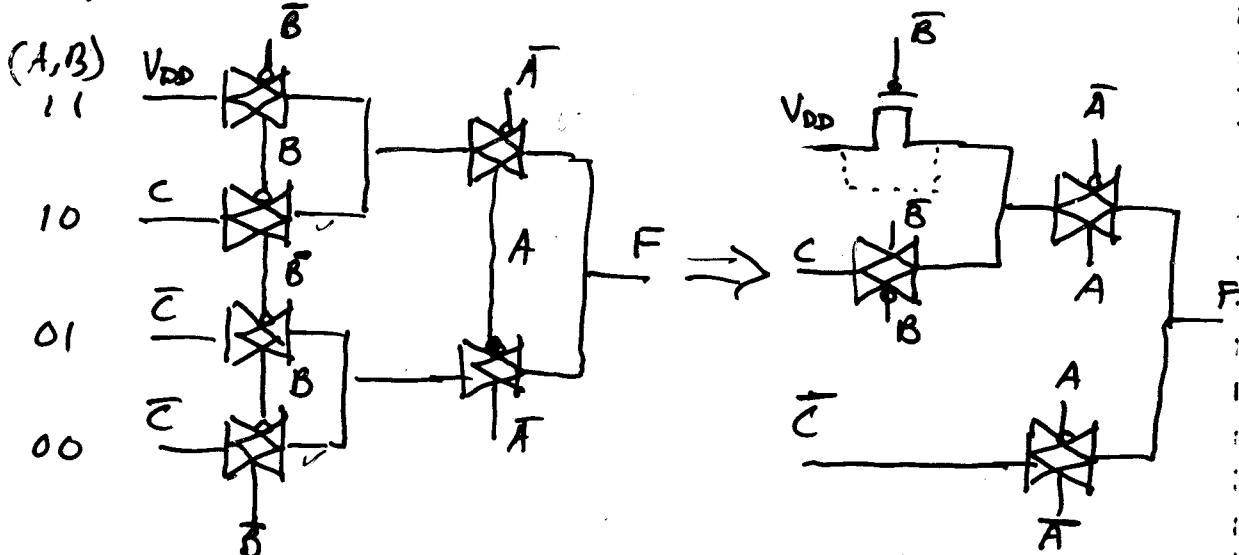

Note that one can combine TG's with static logic gates to achieve efficient implementations of logic functions.

Example 2 (Prob. 7.4c)

$$F = \overline{(A+B+C)} + \bar{A}\bar{B} = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}$$

1.) Let A, B, C be control signals


2.)

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


⇒

A	B	F
0	0	1
0	1	1
1	0	0
1	1	0

3.)

 

CMOS Transmission Gate Delays

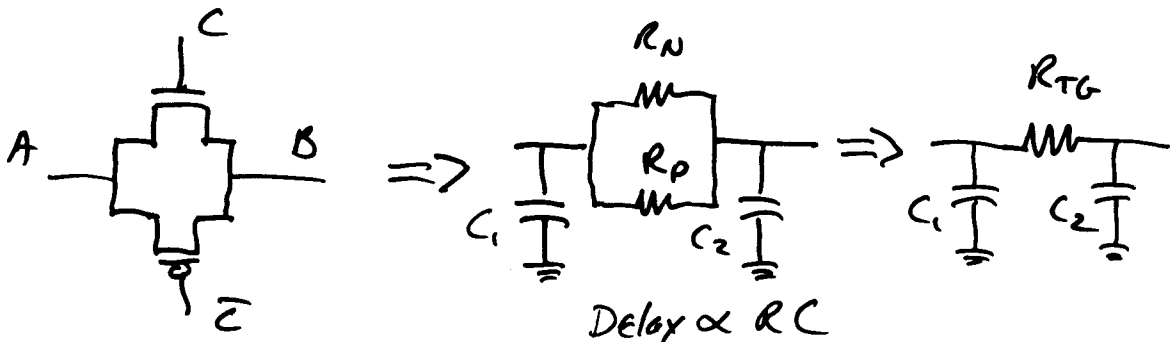

b) What is  $R_{TG}(R)$ ?

a.) For the propagation of  $V_{DD}$

$$R_{TG} = R_{n1} || R_p \approx (2R_{eqn}) || R_{eqp} = 2R_{eqn} || 2.4R_{eqn} \approx \underline{\underline{R_{eqn}}}$$

↑  
This approximates  
the NMOS skirting  
off

b.) For propagation of a zero.


$$R_{TG} = R_{n1} || R_p \approx R_{eqn} || 2(2.4R_{eqn}) = R_{eqn} || 4.8R_{eqn} \approx \underline{\underline{R_{eqn}}}$$

↑  
Approximating the  $R_{eqp}$   
for a PMOS skirting off


 
2.) What is  $C_1$  and  $C_2$  ( $C_i = C_o$ )?

a.) In off state:  $C_1 = C_{in} = C_2 = C_{out} = C_{eff}(W_n + W_p) = 2WC_{eff}$

b.) In on state:  $C_1 = C_2 = C_{eff}(W_n + W_p) + \frac{1}{2} C_g(W_n + W_p)$



 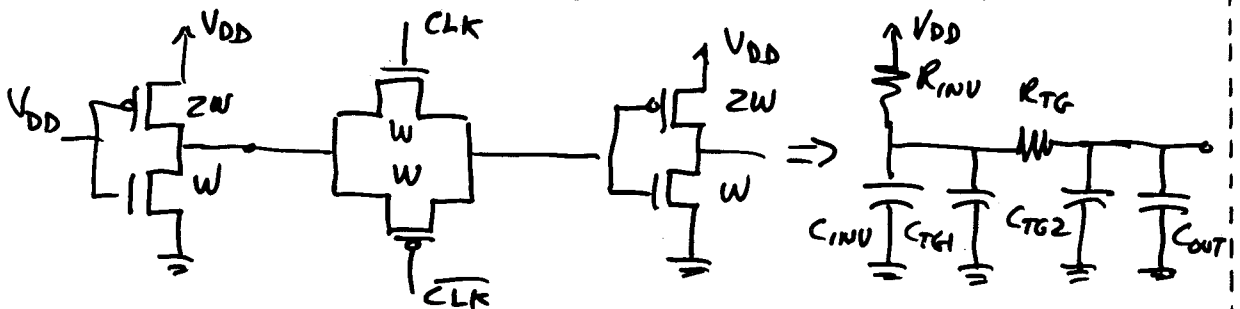Transmission Gate Driven and Loaded by Inverters



Elmore's Delay:


$$\text{Elmore's Delay} = R_1 C_1 + (R_1 + R_2) C_2 + (R_1 + R_2 + R_3) C_3 + \dots$$

For the above,

$$\text{Elmore Delay} = R_{INV} (C_{INV} + C_{TG1}) + (R_{INV} + R_{TG}) (C_{TG2} + C_{OUT})$$

 Example 7.4

Find the Elmore delay for the following -



To be cont'd