
 


 Example 7.4

Find the Elmore delay for the path shown where the fanout of the invert at the output of the multiplexer is f .



Review of TG Capacitances:




OFF:

$$C_{in} = 2WC_{eff}$$

ON:

$$C_{in} = 2WC_{eff} + C_g W$$

RC equivalent:

 

$$\text{Elmore Delay} = R_{inu} C_1 + (R_{inu} + R_{TG1}) C_2 + (R_{inu} + R_{TG1} + R_{ro2}) C_3$$

$$C_1 = 3WC_{eff} + WC_g + 2C_{eff}W = (5C_{eff} + C_g)W$$

$$C_2 = 6WC_{eff} + 2C_g W$$

$$C_3 = 3WC_g f + 4WC_{eff} + C_g$$

$$\begin{aligned} \text{Elmore Delay} &= RW \left[(5C_{eff} + C_g) + 2(6C_{eff} + 2C_g) + 3(3C_g f + C_g + 4C_{eff}) \right] \\ &= WR [29C_{eff} + 8C_g + 9fC_g] \end{aligned}$$


Logical Effort for a Transmission Gate

$$\text{Recall that } LE = \frac{\tau_{gate}}{\tau_{nv}} = \frac{\tau_{gate}}{3RW C_g}$$

$$\tau = (\text{pull resistance of gate})(\text{Input } C \text{ of gate})$$

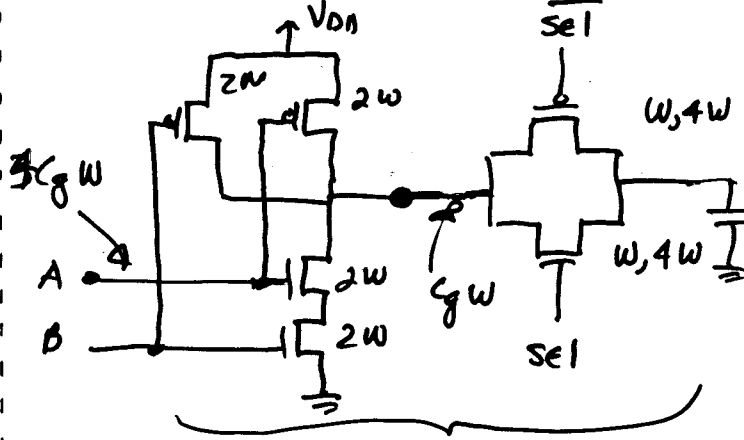Example 7.5


Compute the LE_A and LE_{sel} for the NAND gate shown which drives a TG with a width W and $4W$



Width of TG = W

$$LE_A = \frac{t_{gate}}{3WC_gR} = \frac{4WC_g(2R)}{3WC_gR} = \frac{8}{3}$$
 
$$LE_{sel} = \frac{WC_g(2R)}{3WC_gR} = \frac{2}{3}$$




Width of TG = $4W$

$$LE_A = \frac{4WC_g(\frac{5}{4}R)}{3WC_gR} = \frac{5}{3}$$


$$LE_{sel} = \frac{4WC_g(\frac{5}{4}R)}{3WC_gR} = \frac{5}{3}$$

DYNAMIC D-LATCHES AND D-FLIP-FLOPS

 
Evolution of Simple D-Latches using TG's -



 Problems: Propagation of V_{DD}
 Clock feedthrough
 No \bar{Q} available
 Output becomes hi-Z when the clock is low.



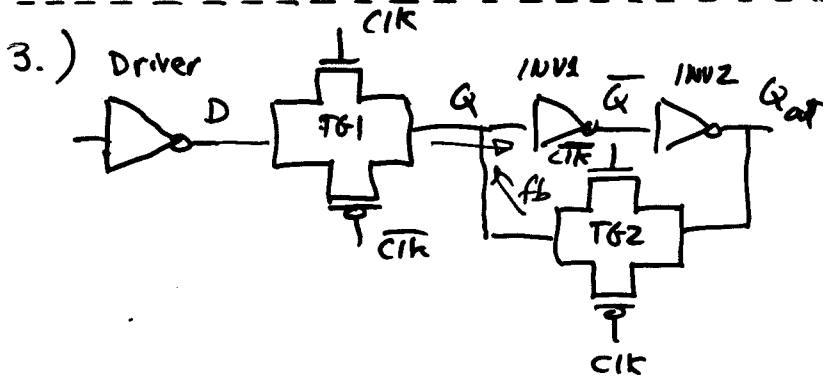
Solves:
 Propagation of V_{DD}
 Helps to reduce clock feedthrough



New problem: When the clk goes high, the delay before clk goes low can cause a conflict at Q between TG1 & TG2

Solution:

 a.) Size INV2, TG2 and TG1 and the driving gate D so that the forward path is stronger than the feedback path



$clk = 1$: Transparent mode (Delay = TG + 2 INV)

If $D = 0 \rightarrow \bar{Q} = 1$ ($M1 = ON, M2 = OFF, M3 = OFF, M4 = OFF$)

If $D = 1 \rightarrow \bar{Q} = 0$ ($M1 = OFF, M2 = OFF, M3 = OFF, M4 = ON$)

$clk = 0$ Latch Mode

If $D = 1 \rightarrow \bar{Q} = 0$ ($M1 = OFF, M2 = ON, M3 = ON, M4 = ON$)


If $D = 0 \rightarrow \bar{Q} = 1$ ($M1 = ON, M2 = ON, M3 = ON, M4 = OFF$)

Master-Slave D Flip-Flops

(See slide)

3/30/05

Figure 7.24 – Positive edge-triggered D-type flip-flop

 

Note that this circuit is the cascade of two D-Latches

The positive edge of the CLK shuts off the first latch and enables the second.


CLK=0:

- 1st latch is transparent
- 2nd latch is disabled

CLK=1:





- TG1 shuts off and holds D at its output (1st latch)
- TG2 allows Q to flow to the output

 Since D is only transmitted to the output on the rising edge of the clock, this flip flop is called edge triggered.



Domino Logic

Evolution -

    

3-input dynamic NOR gate next -