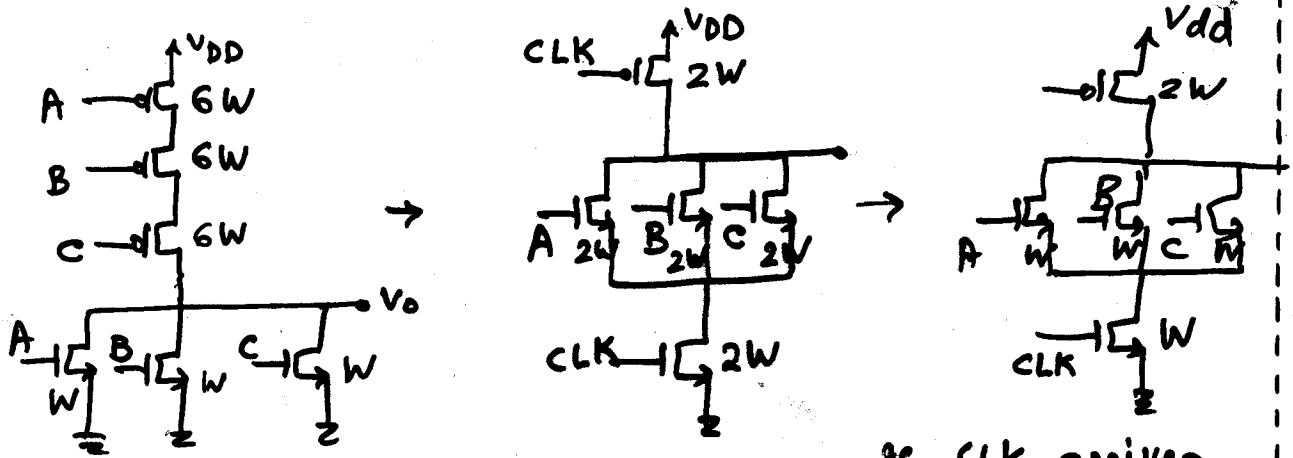



### 3 input Dynamic NOR Gate

Static



If CLK arrives before A, B, C.


### General structure of a dynamic gate

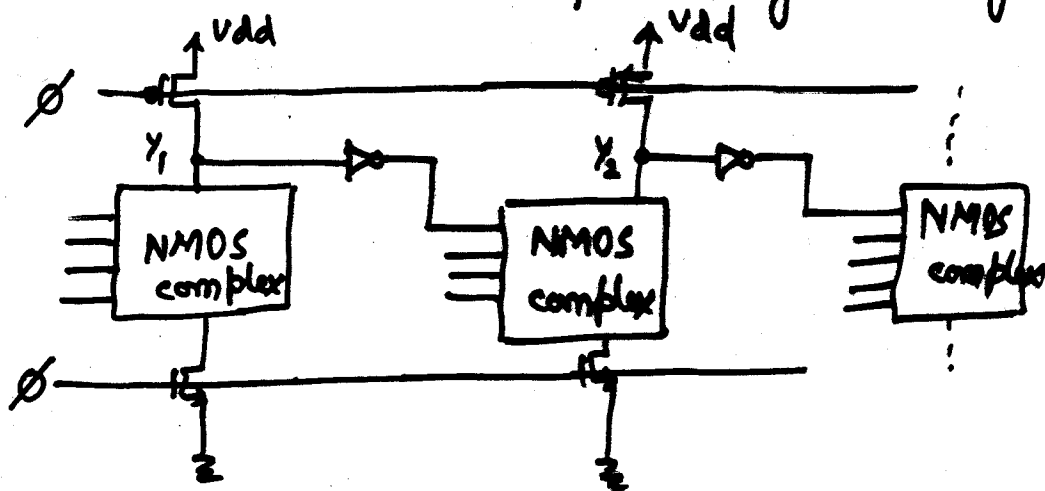

### Domino Logic - some observations

- 1) Since the output is already high, we can speed up the gate by increasing the sizes of NMOS transistors.

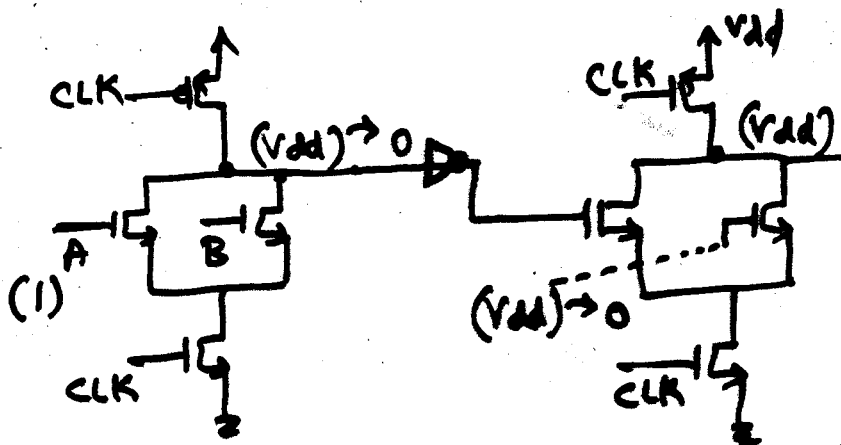- 2) Since there is no pull up fighting the pull down  $\rightarrow$  switch faster.
- 3) Power savings.
- 4) Domino logic  $\rightarrow$  only implement non-inverting logic function.




Logic Effort for Domino Logic

NOR2

Static

$L = 2\lambda$

 


$$LE_{NOR} = \frac{\text{NOR input cap.}}{\text{INV input cap.}}$$

$$= \frac{16\lambda + 4\lambda}{8\lambda + 4\lambda} = \frac{5}{3}$$

$\approx 1.67$

Dynamic NOR2

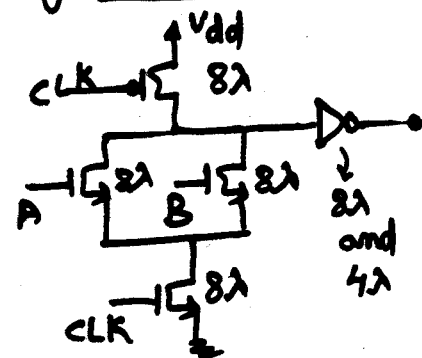

$$LE_{DYN-NOR} = \frac{8\lambda}{12\lambda} = \frac{2}{3}$$


$LE_{INV} = 1$

$$LE_{DOMINO} = \sqrt{(LE_{DYN-NOR})(LE_{INV})}$$

$\approx 0.8$


## Limitations of Domino Logic

### ① Charge sharing.

 

① Precharge Cout to VDD

② IN → goes from 0 to 1.  
and CLK → 1.

 

$$V_o = \left\{ \frac{C_{out}}{C_x + C_{out}} \right\} V_{DD}$$

If,  $C_x = C_{out}$ ,  $V_o = \frac{V_{DD}}{2}$

### Solutions

- 1) Increase  $C_{out} \rightarrow$  Speed  $\downarrow \downarrow$
- 2) Precharge  $x$  to  $V_{DD}$ .
- 3) Use Keepers.

