 


Limitations of Domino Logic


1.) Charge sharing



As IN goes from 0 to 1, $N_{out} \approx \frac{C_{out}}{C_x + C_{out}} V_{DD}$
 If $C_x = C_{out}$, then $N_{out} = \frac{V_{DD}}{2}$

Solutions:

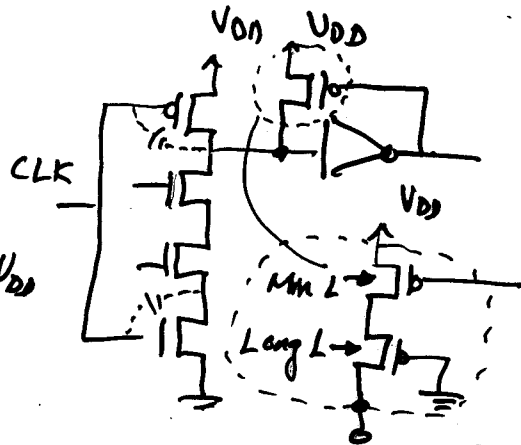
- 1.) Increase C_{out}
- 2.) Precharge node X to V_{DD}
- 3.) Use Keepers



2.) Leakage

Solutions:


- 1.) Increase the size of capacitors
- 2.) Use keepers (passive biasing)
- 3.) Clock feedthrough from the clk.

 

Example 7.8

For the domino logic function shown, assume 0.13 μm technology and find:

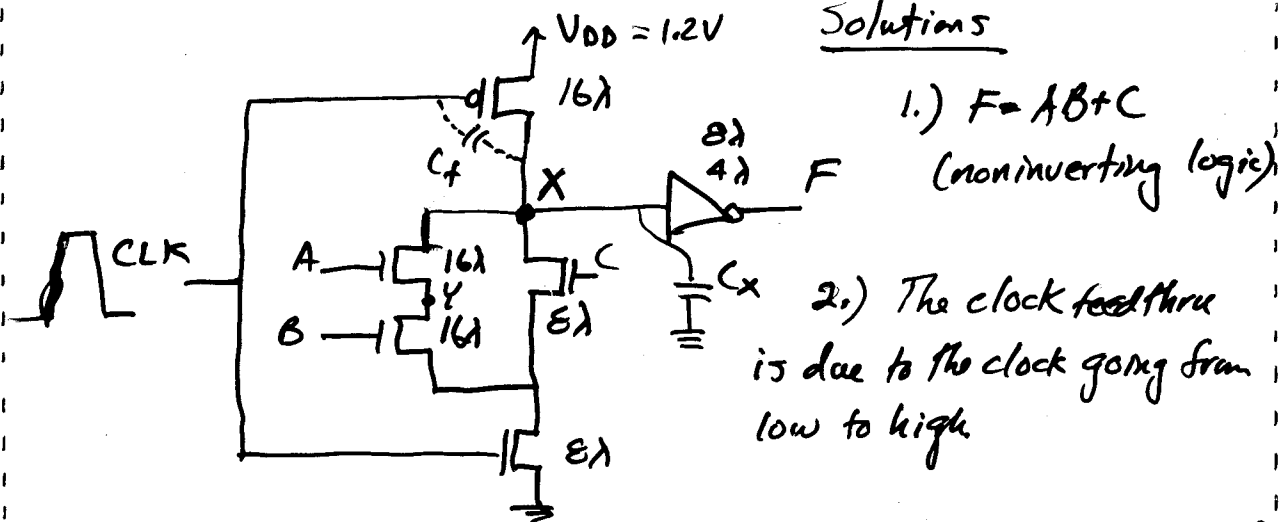- 1.) What logic function does the gate perform?
- 2.) How much clock feedthru is observed at node X.
- 3.) What is the worst-case charge sharing at node X.



PMOS (1meas): $C_f = C_{gd} = \frac{C_g W_p}{2} = \frac{(2fF/\mu m)(16\lambda)(0.05\frac{\mu m}{\lambda})}{2}$
 $= 0.8fF$

Capacitance to ground from node X:

$$C_x = C_{eff}(16\lambda + 16\lambda + 8\lambda) + C_g(8\lambda + 4\lambda)$$

$$= 1fF/\mu m(40\lambda)(0.05\frac{\mu m}{\lambda}) + 2fF/\mu m(12\lambda)(0.05\frac{\mu m}{\lambda}) = 3.2fF$$

$$\therefore \Delta V_x = \frac{C_f \Delta V_{clk}}{C_f + C_x} = \frac{0.8}{0.8 + 3.2}(1.2) = \underline{\underline{0.24V}}$$

3.) What is the worst case sharing at node X?

The worst case charge sharing occurs for the output at 1.2V, and $A=1, B=C=0$.

$$C_y = (1fF/\mu m)(16\lambda)(0.05\frac{\mu m}{\lambda}) = 0.8fF$$

Charge sharing between X & Y:

$$V^* = \frac{C_x(1.2V)}{C_x + C_y} = \frac{3.2(1.2V)}{3.2 + 0.8} = 0.96V$$


But the maximum voltage at node Y is $V_{DD} - V_{TN} = 1.2 - 0.4 = \underline{\underline{0.8V}}$

The rest of the charge is at node X

$$\therefore (3.2fF)(1.2V) - (0.8fF)(0.8V) = 3.84fC - 0.64fC = 3.2fC$$


$$3.2fC = 3.2fF V_x \rightarrow \underline{\underline{V_x = 1V}}$$

Dual-Rail (Differential) Domino Logic

 

Can achieve both
an inverting and
noninverting logic


NAND2 Example

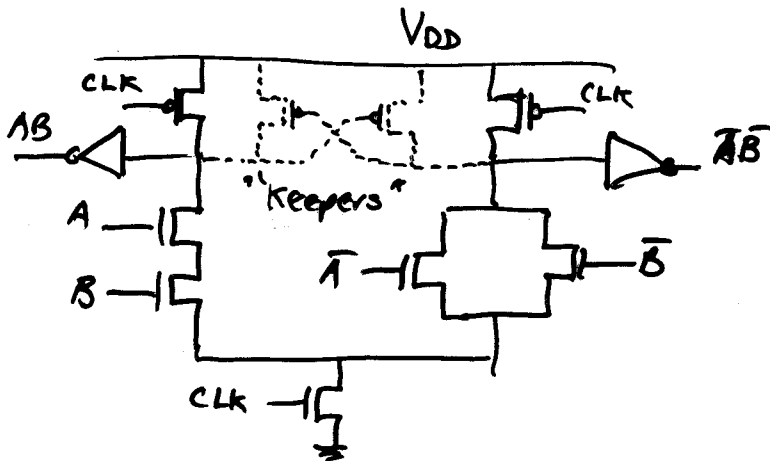

"Keepers"

Chapter 8 - Semiconductor Memory Design

Chapter 10 - Interconnect Design

 

CHAPTER 8 - SEMICONDUCTOR MEMORY DESIGN

Memory Classification

