

SEMICONDUCTOR MEMORY DESIGN- CONT'D

Introduction-

- Memories are circuits or systems that store digital information in large quantities.
- 100 bits < Size of memories < 1GB
- Units of size -

Bit = Digital "1" or "0" (flip-flop or similar ckt.)

Byte = 8 bits (a single alphanumeric character)


Word = 32 to 128 bits

"K" =  $2^{10} = 1024$

"M" =  $2^{20} = 1,048,576$

Memory Organization

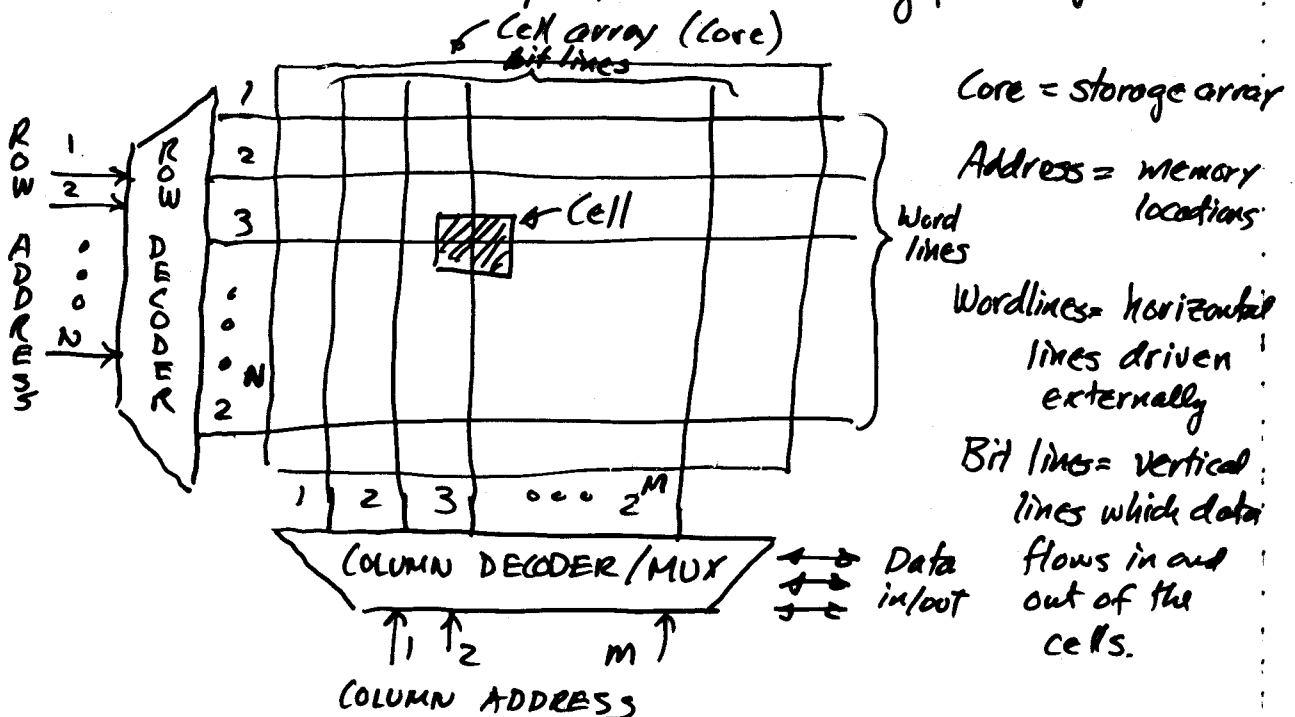- Non-random access - FIFO, LIFO, shift registers, etc.
- Random access - memory locations can be accessed in a random or fixed order independent of the physical location for the purpose of reading & writing.



# Overall Architecture of a 64Kb RAM



 


Figure 8.6 – Structure of two-level decoder for 6-bit address

 

 
Example 8.1 - Decoder Sizing using LE Techniques

Size the decoder on the previous slide using FOA rules assuming the the normalized output loading is 1, (FOA rules imply that the optimal stage effort is equal to 4.)




Static RAM (SRAM) Cell Design

6 transistor:

 


4 transistor:

 

$R_s = R_c \geq 10M\Omega$   
 (Lightly doped poly)

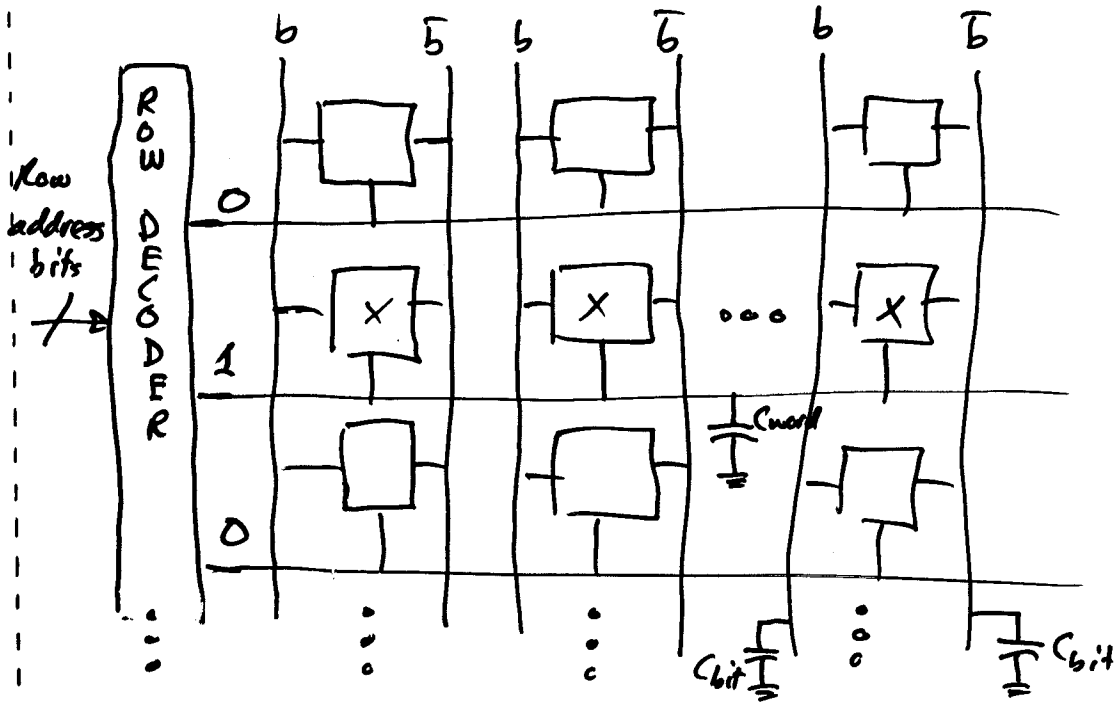
Wordline and Double Bit-line Architecture



$$C_{word} = (2 \times \text{gate capacitance} + \text{wire capacitance}) \times \text{no. of cells in a row}$$

$$C_{bit} = (\text{Source/drain cap.} + \text{wire cap.} + \text{contact cap.}) \times \text{no. of cells in a column}$$

Read operation

 

- 1.) Assume  $q = 0$  and  $\bar{q} = 1$
- 2.) Bit lines are precharged to  $V_{DD}$ .
- 3.) M1 ON and M2 OFF
- 4.)  $b$  drops,  $\bar{b}$  stays constant
- 5.) The difference between  $b$  and  $\bar{b}$  is applied to the sense amplifier.