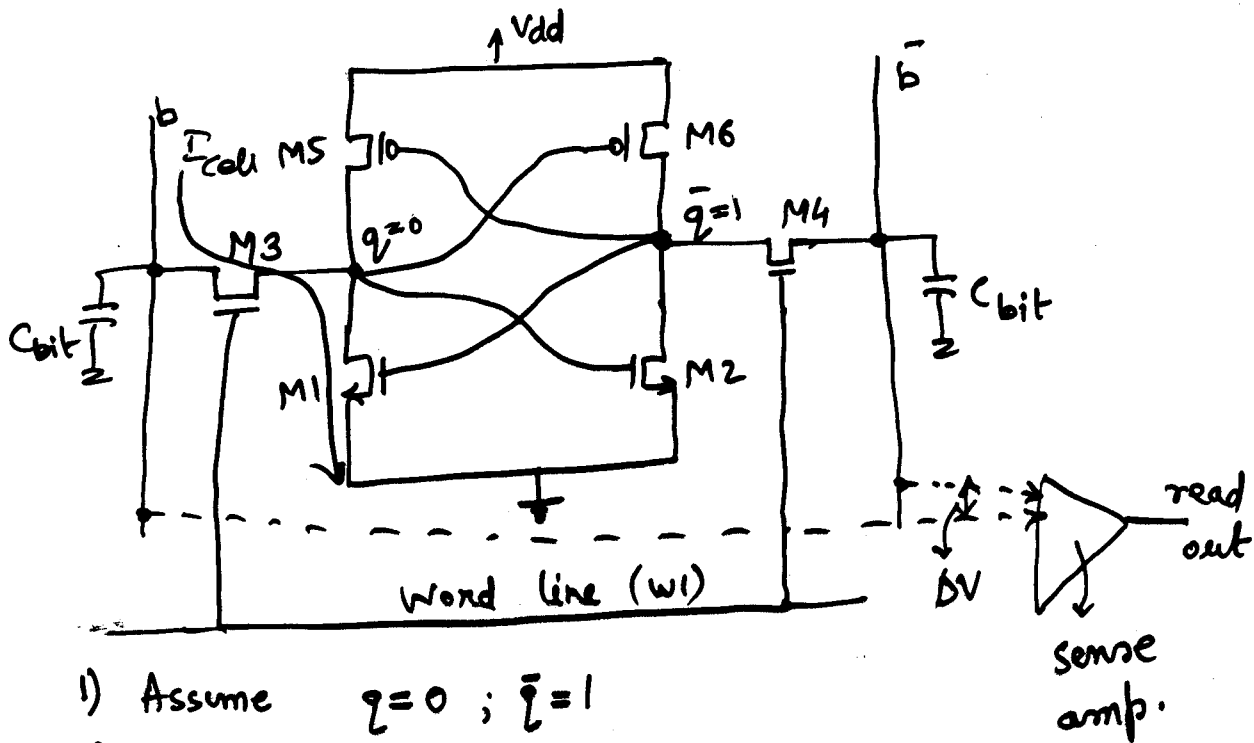



Read operation of the 6T SRAM cell



- 1) Assume $q=0$; $\bar{q}=1$
- 2) Bit lines are precharged to V_{DD}
- 3) $M1 - ON$; $M2 - OFF$
- 4) $WL - ON \Rightarrow M3$ and $M4 - ON$

↓
($b \rightarrow M3 \rightarrow M1 - \text{gnd}$)

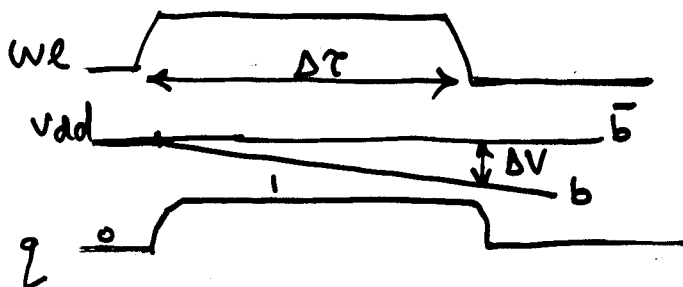- 5) b drops, but \bar{b} remains at V_{DD} .
- 6) Difference between b and \bar{b} is applied to a sense amplifier.



$$I_{cell} = C_{bit} \cdot \frac{\Delta V}{\Delta T}$$


$$\Delta V = \left\{ \frac{I_{cell} \cdot \Delta T}{C_{bit}} \right\}$$

Ex. 8.2

Compute W_1 and W_3 given that q node can change 100mV during the read operation.

Assume $C_{bit} = 2\text{pF}$ and the sense amplifier requires a transition of 200mV on the bit line in 2ns. Use 0.13 μm technology.
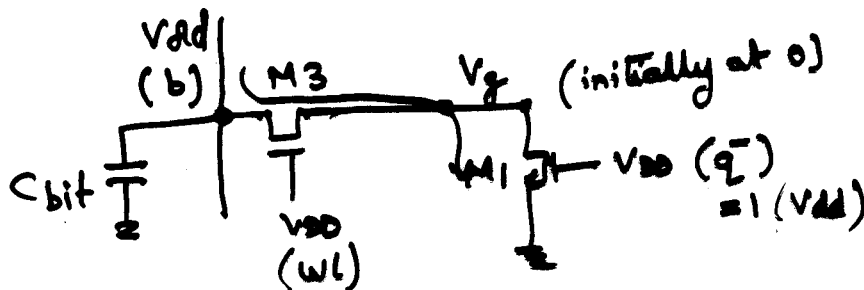
$$I_{cell} = C_{bit} \times \frac{\Delta V}{\Delta t} = 2\text{pF} \times \frac{200\text{mV}}{2\text{ns}} = 200\mu\text{A}.$$



$$\left(\frac{W_1}{L_1}\right) \frac{\mu_n C_{ox}}{\left(1 + \frac{V_g}{E_{CN} L_1}\right)} \left[(V_{DD} - V_{T1}) V_g - \frac{V_g^2}{2} \right] = \frac{(W_3) v_{sat} C_{ox} (V_{DD} - V_g - V_{T3})^2}{\left\{ (V_{DD} - V_g - V_{T3}) + E_{CN} L_3 \right\}}$$


$$\left(\frac{W_1}{W_3}\right) \cong 1.73$$

$$200\mu\text{A} = I_{cell} = I_3 = \frac{(W_3) (v_{sat}) C_{ox} (V_{DD} - V_g - V_{T3})^2}{\left\{ (V_{DD} - V_g - V_{T3}) + E_{CN} L_3 \right\}}$$

| |
|-------------------------|
| $W_3 = 0.4 \mu\text{m}$ |
| $W_1 = 0.7 \mu\text{m}$ |

Normal practice \rightarrow $\frac{W_1}{W_3} \cong 1.5$

Write operation for a 6T SRAM cell

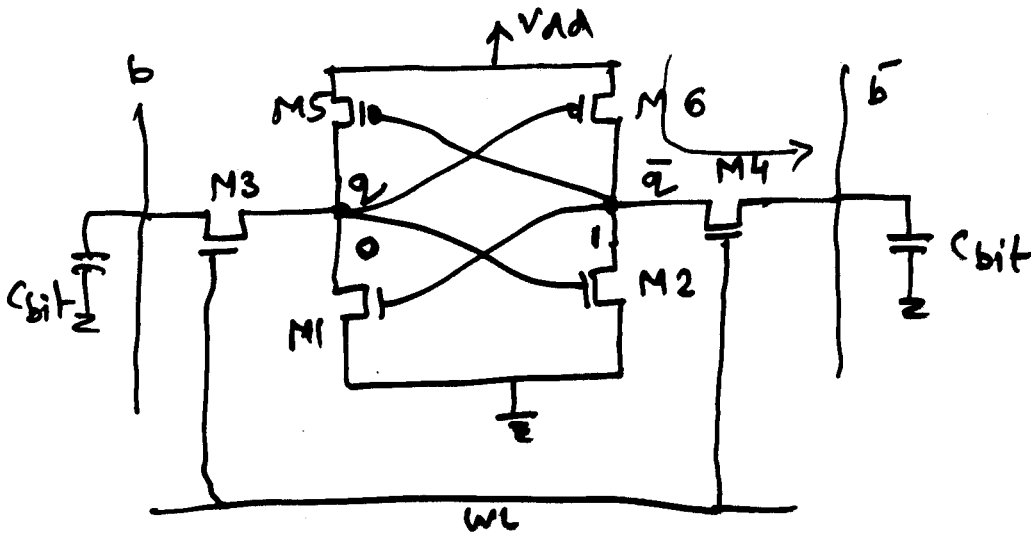


Operation to write 1. \rightarrow ($q=1$)

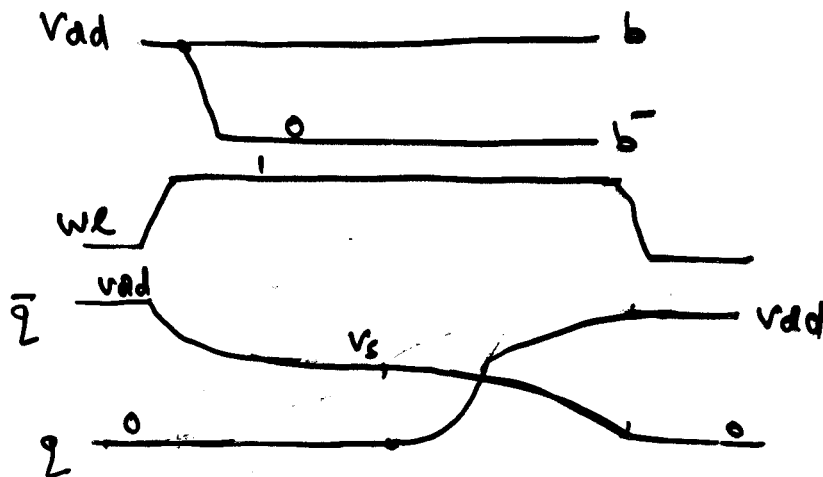- 1) Precharge b and \bar{b} to V_{DD} .
- 2) Keep $b = V_{DD}$ but $\bar{b} = 0$.
- 3) WL is ON, both $M3$ and $M4$ are ON
($M6$ and $M4 \rightarrow$ ON)

$M4$ needs to be stronger than $M6$.

$$\left(\frac{W_4}{W_6}\right) \approx 1.5 = \left(\frac{W_3}{W_5}\right)$$



Also, $\left(\frac{W_1}{W_3}\right) = \left(\frac{W_2}{W_4}\right) \approx 1.5$

$$\begin{aligned} \left(\frac{W_1}{W_5}\right) &= \left(\frac{W_2}{W_6}\right) \\ &= (1.5)^2 \\ &= 2.25 \end{aligned}$$