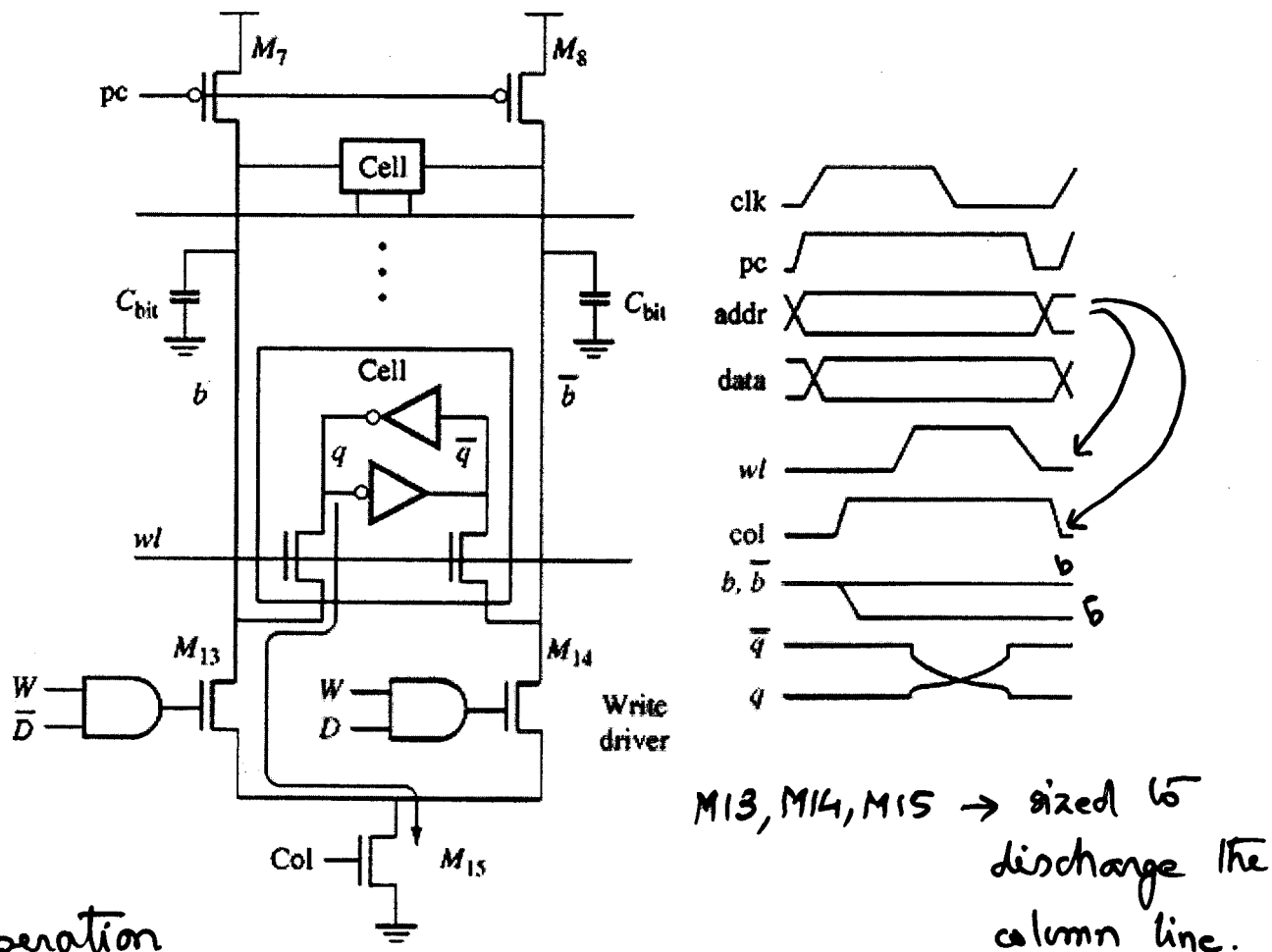


Write Circuitry


Figure 8.18 – Write driver circuit.

Operation

- 1) Columns are precharged to V_{DD} .
- 2) Address and Data – applied and held stable.
- 3) Clock converts the address signals into column select and "wl" activation signals.
- 4) Data and write signals are applied to pull one column to ground while leaving the other at V_{DD} .
- 5) When "wl" goes high, current flows out of the cell and flips the sense of the cell.
- 6) Once the cell flips, "wl" and "Col" select lines go to their standby values.

Read Circuitry


Figure 8.19 – Basic read circuit.

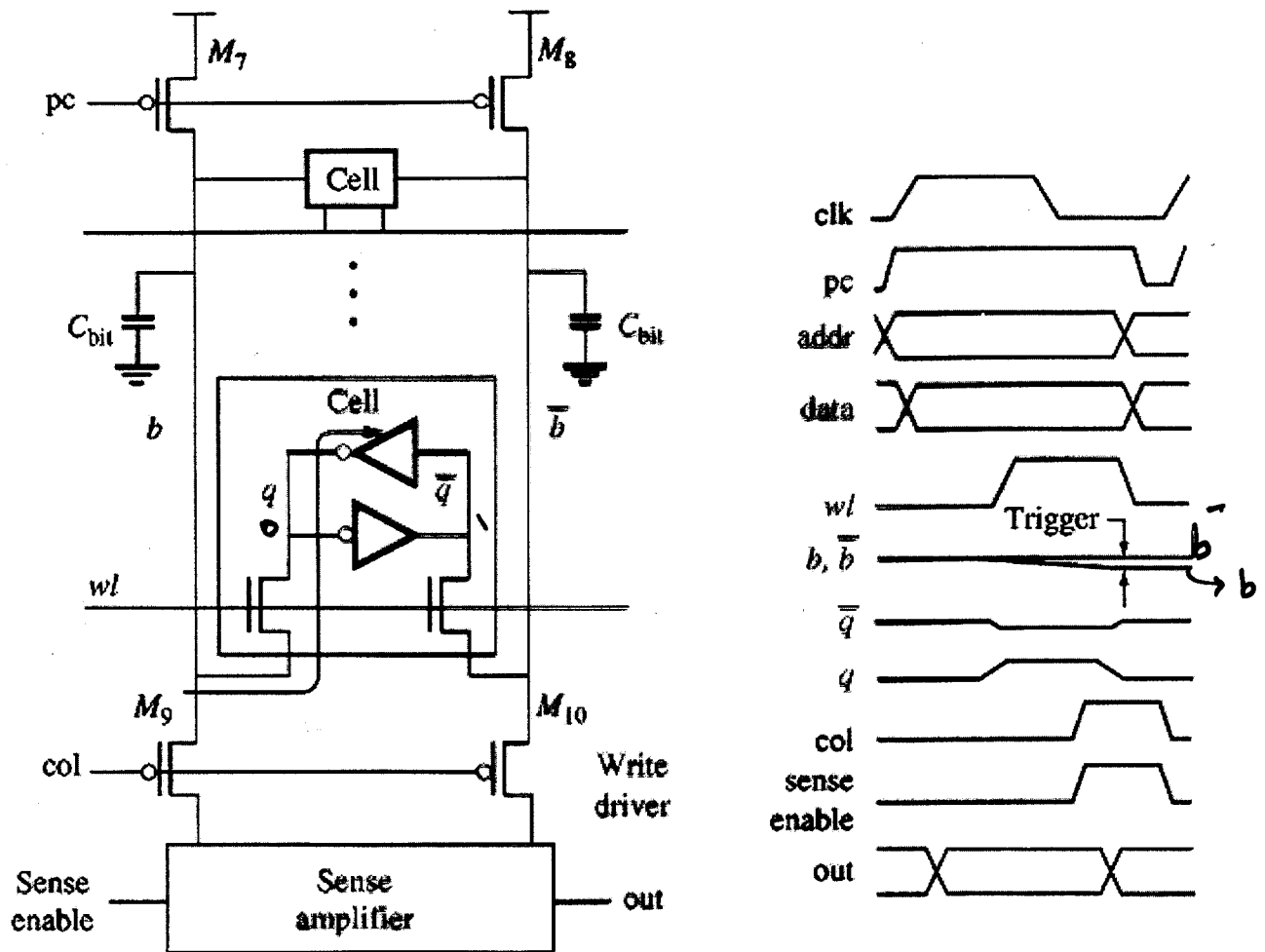Operation

- 1) Precharge column lines to V_{DD} .
- 2) Address, Data, and CLK are applied.
- 3) Address signals translate into column enable and "wl" activation signals.
- 4) Bitline (initially precharged to V_{DD}) begins to fall.
- 5) Sense amplifier \rightarrow amplifies the difference in voltage between b and \bar{b} .

Sense Amplifiers

Figure 8.21 – Differential sense amplifier.

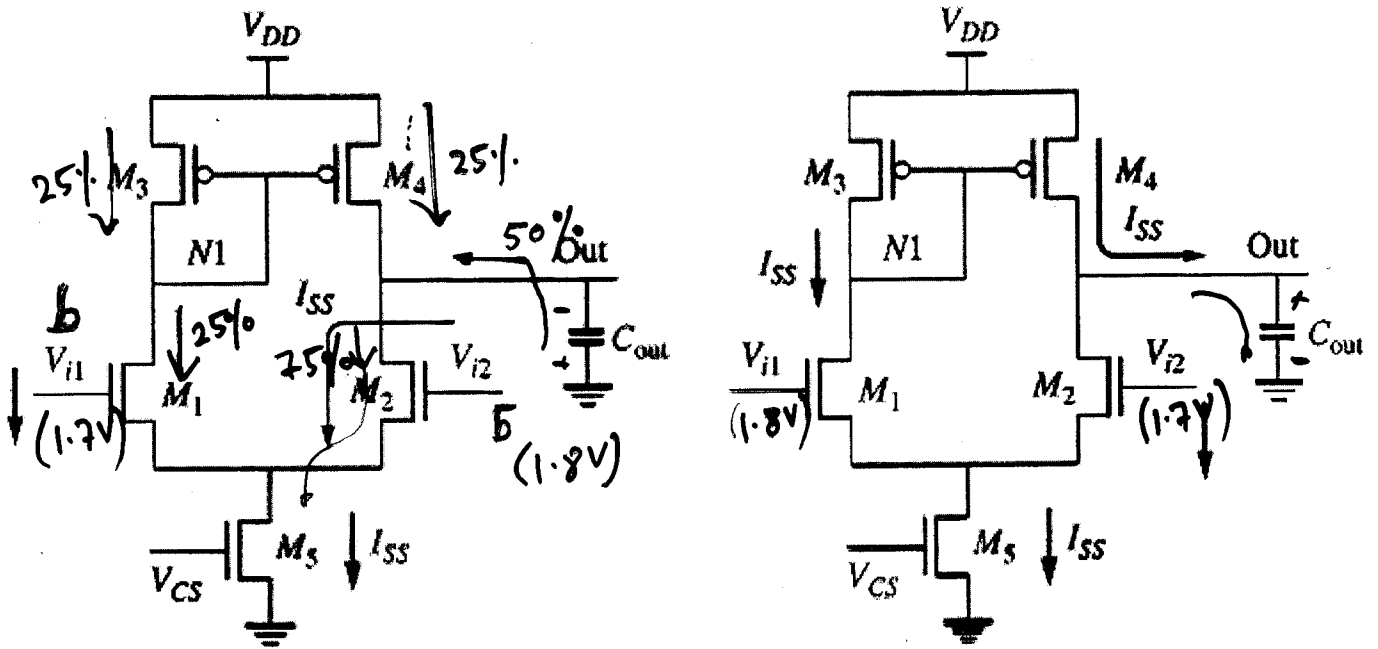

(a) Discharging output


(b) Charging output

- Pull ups must be saturated enhancement loads.
- Need noise immunity (~~from~~ ^{from} noise common to \bar{b} , \bar{b})
- Rejects common-mode signals.
- Amplifies differential signals.
- Precharge V_{i1} and V_{i2} to $(V_{DD} - V_{TN})$.

$$P_{diss} = (V_{DD} \cdot I_{SS})$$

$$\text{slew rate} = \frac{I_{SS}}{C_{out}} \Rightarrow \Delta\tau = \frac{C_{out}}{I_{SS}} \cdot (\Delta V_{out})$$

Figure 8.22 – Latch-based sense amplifier.

 

- Low power
- Slower
- Sensitive to noise as it needs large input voltage change.

 
 


Figure 8.23 – Replica circuit for sense amplifier clock enable

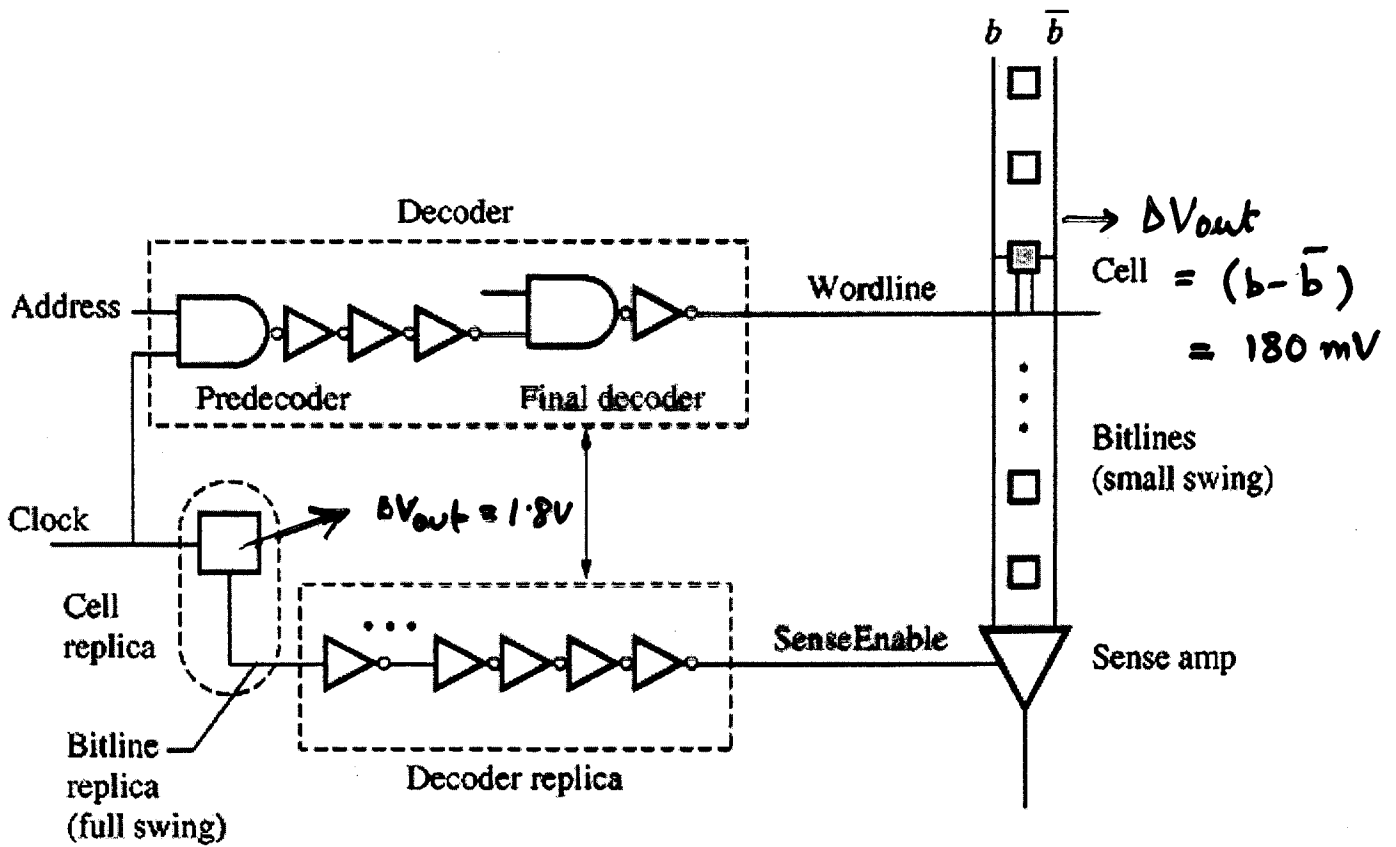


Figure 8.24 - Replica cell design.

