
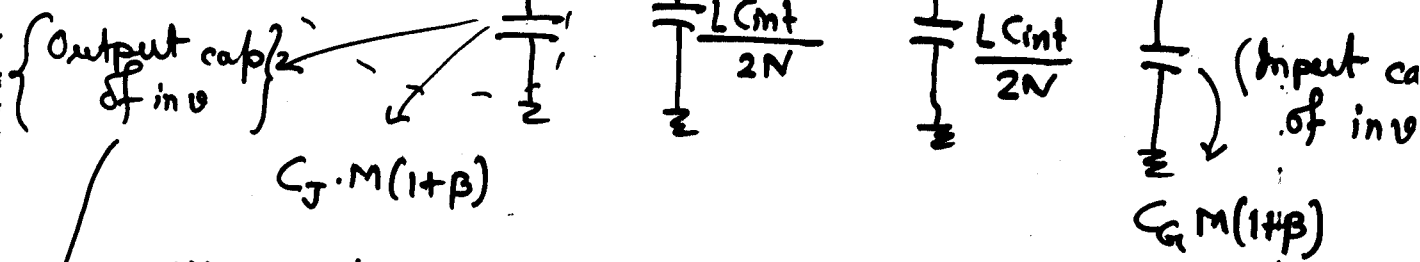
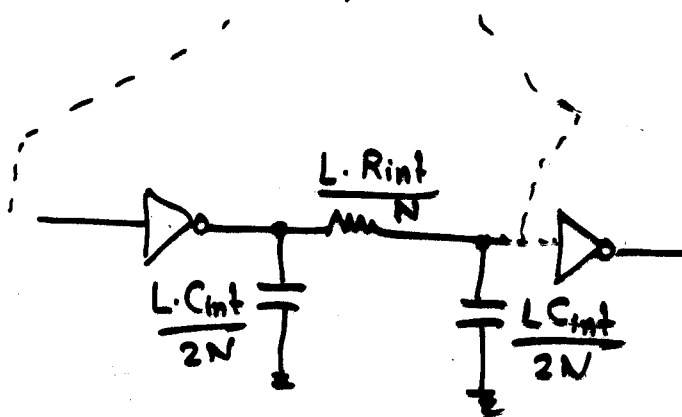


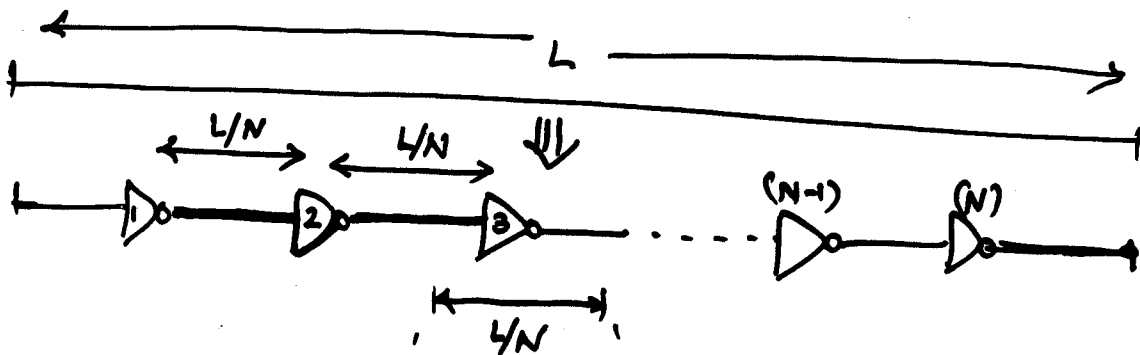How do you reduce the delay of long wires  
Buffer insertion



1X inverter

$$C_{out} = C_{eff} \cdot W_n(1+\beta) \quad ; \quad \beta = \frac{W_p}{W_n}$$

$$C_{in} = C_g (W_n + W_p) = C_g (W_n) (1+\beta)$$

### Elmore delay for 1 segment

$$t_{\text{seg}} = \frac{R_{\text{eqn}}}{M} \left( C_G (1+\beta)M + \frac{C_{\text{int}} \cdot L}{2N} \right) +$$

$$\left\{ \frac{R_{\text{eqn}}}{M} + \frac{R_{\text{int}} \cdot L}{N} \right\} \left[ \frac{C_{\text{int}} \cdot L}{2N} + C_G (1+\beta)M \right]$$

### Total delay for N segments

$$t_{\text{total}} = N \cdot (t_{\text{seg}})$$

$$= \left\{ N (C_G + C_J) R_{\text{eqn}} (1+\beta) \right.$$

Buffer  
only

$$+ \left\{ C_G (1+\beta) \cdot R_{\text{int}} M + \frac{C_{\text{int}} \cdot R_{\text{eqn}}}{M} \right\} L$$

Buffer &  
Interconnect

$$+ \left\{ \frac{C_{\text{int}} R_{\text{int}}}{2N^2} \right\} L^2$$

Interconnect  
only

→ error in the book.

(find N and M)

$$\text{To find } N \rightarrow \left( \frac{\partial t_{\text{total}}}{\partial N} = 0 \right)$$

$$N = \sqrt{\frac{R_{\text{int}} \cdot C_{\text{int}} \cdot L^2 / 2}{R_{\text{eqn}} (C_J + C_G) (1+\beta)}} = \sqrt{\frac{t_{\text{wire}}}{f_0 I}}$$

To find  $M$ .

$$\frac{\partial \tau_{total}}{\partial M} = 0 \Rightarrow M = \sqrt{\frac{R_{reg} \cdot C_{int}}{C_a (1+\beta) R_{int}}}$$

Ex. 10.4

Do Ex. 10.3 but use buffer insertion approach.

$$R_{int} = 54 \text{ m}\Omega/\mu\text{m}, C_{int} = 0.1 \text{ fF}/\mu\text{m}, L = 20,000 \mu\text{m}$$


$$R_{reg} = 12.5 \text{ k}\Omega/\square, C_a = 2 \text{ fF}/\mu\text{m}, C_{eff} = 1 \text{ fF}/\mu\text{m}$$

$$W_n = 0.2 \text{ and } \beta = 2 \rightarrow W_p = 0.4 \mu\text{m}.$$

$$N = \sqrt{\frac{\tau_{wire}}{F_01}} = 6.9 \rightarrow \underline{7}$$


$$M = 139 \rightarrow \underline{140}$$
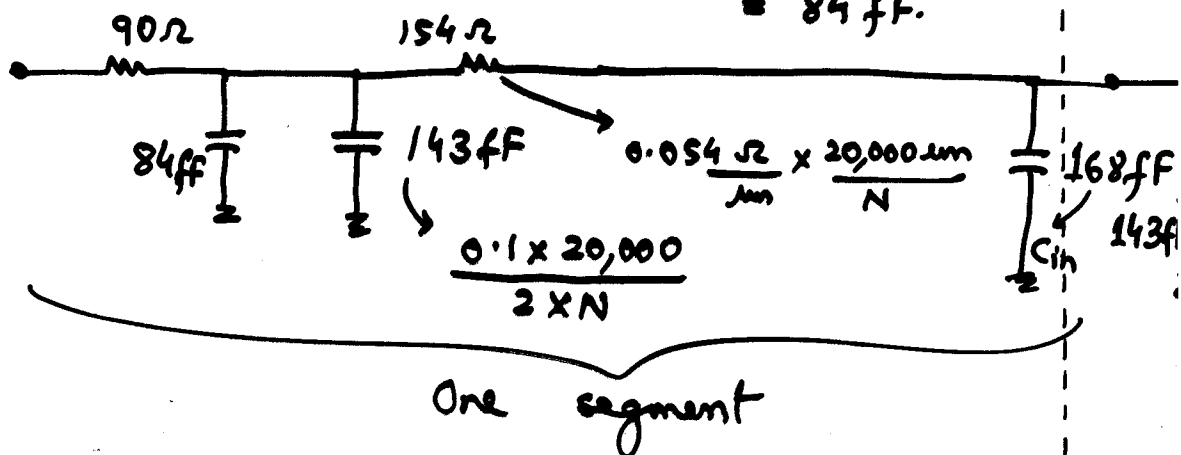
$$R_{eff} = \frac{12.5 \text{ k}\Omega}{140} = 90 \Omega, C_{self} = C_{eff} (2W + W) 140 = 84 \text{ fF}.$$



$$\begin{aligned} \text{Total delay} &= 7 \times \left[ 90 (143 \text{ fF} + 84 \text{ fF}) + \left( \frac{90}{154} \right) (168 \text{ fF} + 143 \text{ fF}) \right] \\ &= \underline{0.67 \text{ ns}} \quad (\text{with no buffers, delay} = 1.3 \text{ ns}) \end{aligned}$$

## Interconnect coupling capacitance

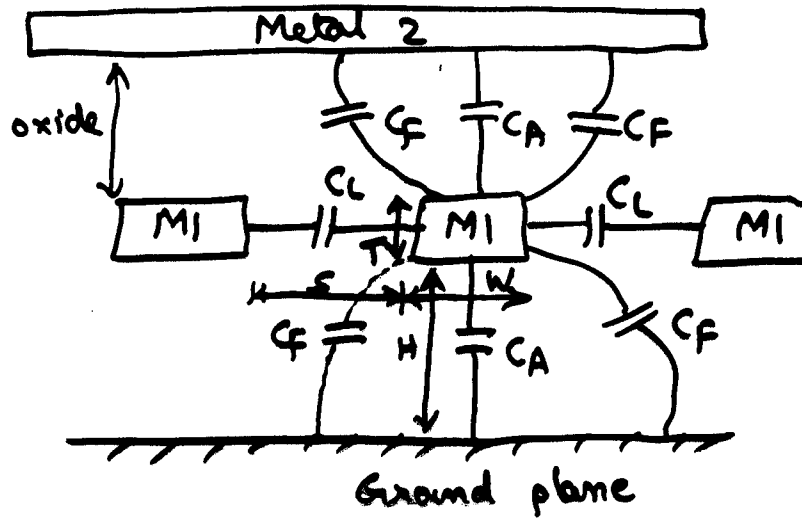

### Types:

- 1) Vertical. ( $C_A$ )  $\rightarrow \epsilon_0 \times \frac{W}{H} = 4 \epsilon_0 \frac{W}{H} \approx 0.035 \frac{W}{H} \text{ fF}/\mu\text{m}$
- 2) Lateral. ( $C_L$ )  $\rightarrow \epsilon_0 \times \frac{T}{S} = 0.035 \frac{T}{S} \text{ fF}/\mu\text{m}$ .
- 3) Fringing. ( $C_F$ )  $\rightarrow \epsilon_0 \ln \left( 1 + \frac{T}{H} \right) \text{ fF}/\mu\text{m}$ .